

NOVEMBER, 1928

25 CENTS

RADIO

(REG. U. S. PATENT OFF.)



A MAGAZINE OF NATIONAL CIRCULATION / COVERING THE ENTIRE FIELD

MAGNAVOX "Dynamic" SPEAKERS



"MAC," leader of the famous
broadcasting "Haywire Orchestra"

The Aristocrat

Beautiful butt burl walnut
cabinet finished in two tones.
For A-Battery Operation . . . \$60
For AC Operation \$70



The Beverly

Gracefully proportioned cabinet
finished in light mahogany.
For A-Battery Operation . . . \$50
For AC Operation \$60

Other floor and table models up to \$175
Units only; DC \$30; AC \$40.



"FIRST
SPEAKER
FIRST
DYNAMIC"

DYNAMIC


Magnavox Dynamic reproduction
is infinitely finer . . . richer, fuller, more
realistic . . . Those who wince at distorted
music or who must strain to hear other
speakers welcome the beauty and generous
volume of Magnavox. That's why fourteen
leading radio set manufacturers have
chosen it for built-in equipment.

THE MAGNAVOX COMPANY

Oakland, California

Chicago, Illinois

PEP UP YOUR SET!

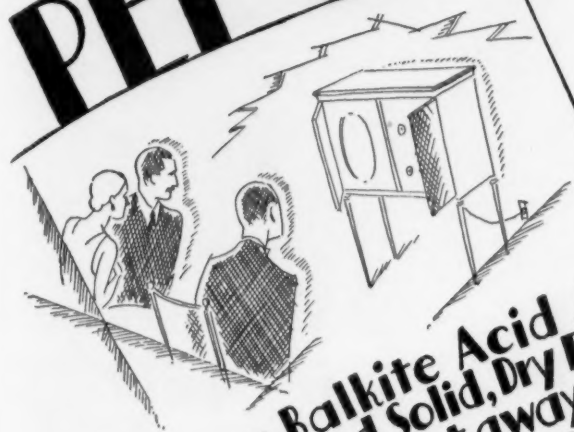

Replace your Balkite Acid Jar with the Authorized Solid, Dry ELKON Replacement Unit... Get away from Acids, Water, Corrosion, Trouble...



BUY ELKON—The Authorized Replacement Unit
Throw away the acid jar! No more fuss, mess, trouble. Simply remove the Acid Jar and snap in the Elkon Replacement Unit—Solid—dry—self healing—no attention or adjustments, and forget it for 5000 hours.

The Elkon Replacement Units and those made by the Famous Steel Products Company containing the Elkon Dry Rectifier are the only ones authorized for replacing the acid jars in Balkite Power Units.
With the Elkon Self-Healing Replacement Rectifiers, your type K will charge at the rate of .8 ampere, type N at the rate of 1 ampere. The charging rate of type J the large charger, is raised 20%. Increased efficiency, too! Why not see your dealer today!

ELKON, INC.
Port Chester, N. Y.
Division of P. R. Mallory & Co., Inc.



This is just one of the many reasons why Elkon Replacement Units are authorized by Famous Steel—Accurate, careful testing of every Rectifier.



Perhaps you need a New Elkon Rectifier

If your set hasn't the same pep and kick it did when you first installed your "A" Eliminator, you need a new Rectifier in the "A" Eliminator. And you are lucky if you have a Majestic, Elkon, Knapp, Fada, Sentinel, Webster, Metro and many others for then you can slip the old rectifier off, and put in a new Elkon Replacement Rectifier in less time than it takes to read this. And the old eliminator is as good as it ever was! Buy one today from your dealer.

If your trickle charger isn't keeping the battery up as well as it did when you bought it—buy a set of Elkon replacement rectifiers and it will be as good as it ever was. Elkon Type V-4 replacement Units can be placed in Acme, Elkon, National, Cleveland, Precision, Bernard. Today's a mighty good time to pep up the old charger—see your dealer.

Radio Department,
Elkon, Inc., Port Chester, N. Y.
261 Fox Island Road.
Send me complete information on Elkon Radio Products.
Name _____ Address _____

RADIO

Established 1917

Published Monthly by the Pacific Radio Publishing Co.

ARTHUR H. HALLORAN,

Editor

P. S. LUCAS,

Associate Editor

H. W. DICKOW,

Business Manager

A. I. RIVETT,

Draughtsman

FRANK C. JONES, Technical Adviser

Entered as second-class matter at Post Office at San Francisco, Calif.

Copyright 1928 by the Pacific Radio Publishing Co.

Address all communications to

PACIFIC RADIO PUBLISHING COMPANY

Pacific Building, San Francisco, California

VOL. X

NOVEMBER, 1928

No. 11

CONTENTS

RADIOTORIAL COMMENT.....17

SHORT-WAVE TRANSATLANTIC

RADIOTELEPHONE SERVICE.....19

By S. R. Winters

SIMPLIFIED REACTANCE

CALCULATIONS.....20

By Arthur Hobart

WHAT IS AN UNDERGROUND

ANTENNA?.....21

By G. M. Best

STANDARD FREQUENCY

TRANSMISSIONS.....22

ELECTRIC PHONOGRAPH PICK-

UP UNITS.....23

By Francis Churchill

RADIO PICTURE TRANSMISSION

AND RECEPTION.....25

By John P. Arnold

RADIO AIDS AIR RACES.....30

By Wallace S. Wiggins

BATTERY CHARGING WITH

A SYNC.....31

By G. F. Lampkin

A COMPLETE TUBE TESTING

SET.....33

By Clinton Osborne

THE MARSHALL SHORT-WAVE

RECEIVER.....34

By S. R. Winters

TECHNICAL BRIEFS.....37

THE COMMERCIAL BRASS-

POUNDER.....39

By P. S. Lucas

A PRACTICAL "B" ELIMINATOR

FOR SHIP USE.....39

By R. M. Hughes

AN ALL-SHORT-WAVE

RECEIVER.....41

By A. Binneweg, Jr.

A SELECTIVE SHORT-WAVE

RECEIVER.....42

By R. Wm. Tanner

INSIDE STORIES OF FACTORY-

BUILT RECEIVERS.....43

FORECAST FOR DECEMBER ISSUE

J. Garrick Eisenberg has a helpful article on "Some Service Considerations." G. F. Lampkin describes the construction of a crystal-controlled transmitter. "Melting Precious Metals by Radio," is illustrated and described in detail. John P. Arnold has some more interesting information on radio transmission and reception of pictures. Circuit diagrams and descriptions are given of several new a.c. factory-built receivers. Articles necessarily omitted from the November issue, but definitely scheduled for December are "A Short-Wave Superheterodyne," by R. Wm. Tanner; "Impedance of R. F. Chokes," by Glenn L. Browning; and "Experimenting with the Grid Leak," by L. W. Hatry. In "Technical Briefs," will be found a circuit for adapting a 45 k.c. superheterodyne to the use of a.c. tubes. Frank C. Jones, who is better known as Francis Churchill, discusses the volume control methods used in a.c. receivers.

"You Can Forget the Condensers—If They Are DUBILIER'S"

Type PL 1120 especially designed for the Thordarson types R-480 and R-280 Power Compacts, used with 171 type tubes and the 280 type tube Rectifier or the Elkon E-80 metallic Rectifier. Price \$15.50



There
is

No Substitute for Quality

No amount of lurid claims by nimble-penned advertising writers will take the place of quality in the final analysis—the operation in your power supply.

Ever since the advent of Radio, Dubilier has been the manufacturers' standard—and the set-builders' stand-by. Built in every Dubilier Condenser is a factor of safety which is your safeguard for years of service without failure.

Dubilier Light Socket Aerial — "A Moulded Bakelite Product"

Bring in programs with a minimum of interference. Do away with the unsightly and trouble causing outside aerial and lightning arrester. Simply attach to the set and plug into the nearest light socket. Uses no current. Sold by all good dealers on a 5 day, money-back basis. Price \$1.50.

Write to Dept. 20 for free catalog



Dubilier
CONDENSER CORPORATION

10 East
43rd Street



New York
City

Reg. U.S. Pat. Off.

Six Issues for \$1.00

SAVE money. Get the next 6 issues of "RADIO" for one dollar—fifty cents less than they cost if purchased from a news dealer. The next six issues of "RADIO" will be better than ever. Let us mail the magazine to your address, starting with the November issue, out on October 25th.

Mail coupon now. Attach a dollar bill, check, money order or \$1.00 in stamps and mail NOW.

Name.....

Street and No.....

City and State.....

Tell them you saw it in RADIO

**164
PAGES
of RADIO
VALUES**

A NEW CATALOG JUST OFF THE PRESS




Wholesale Prices

This big new catalog heralds a new era in radio. Never before have you been offered such variety—**such quality**—such sterling value in radio as you are now offered in this large new catalog. In it, **wholesale prices** are not a myth—but *actual* reality. You will marvel that such merchandise, comprising everything that is **new and worthwhile** in radio can be offered at such prices. Here you will find high quality that is not high priced. If you are interested in radio you cannot afford to be without the **Allied Catalog**.

SET BUILDERS!

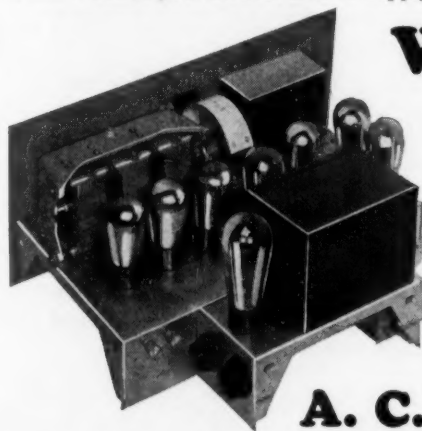Set Builders, Amateurs and so called "Hams" will delight in the *unusual variety*—and **remarkable values** that are offered in standard kits and parts. Tremendous stocks—**real organization**—prompt shipping service all combine to make Allied your ideal source of supply.



A. C.

ELECTRIC SETS

Allied offers you a new—complete line of A-C Receivers, available in either chassis form or in a wide variety of beautiful console models. Prices range from \$32.95 to \$199.00. Dollar for dollar they stand out as one of the season's leading receivers. Engineered to unusual perfection they offer you features found only in the highest priced sets.

YOU MEN Who Buy RADIO!

By making your problems *our* problems, we know the service you require—and to render you such service the entire Allied organization is dedicated—to give you the service you have a right to expect. Tremendous stocks, remarkable values and a real desire to serve, all combine to make Allied your ideal source of supply.

RADIO DEALERS!

The live radio dealer—the man who keeps pace with the rapid advance of radio will find much of **real interest** in the Allied Catalog. New A-C Sets, D-C Sets, Dynamic and Magnetic Speakers, television equipment, in fact **everything** that an impatient radio public is demanding.

What Allied offers you!

Allied Service will prove a revelation to you in what radio service can really be. Allied Executives backed by years of training in radio are practical men. They know radio. Their vast experience has built up around them an organization trained to serve. Months of effort have built up here a tremendous reserve of stock that makes for prompt shipments; and this stock is new stock comprising the seasons pick of such prominent manufacturers as Silver-Marshall, Tyrman, Aero, Hammerlund-Roberts, etc.

You Profit When You Buy Right


Buying right is half the battle. From the small set builder to the large dealer, your success depends upon gauging the public pulse of radio and in **buying right**. Everything that is new in radio—the items the radio public is now demanding are here, ready for your call. Write now—the catalog is **free** for the asking.

Write for Catalog Now


Allied Radio

CORPORATION

711 W. LAKE ST. Dept. E-2 CHICAGO, ILL.

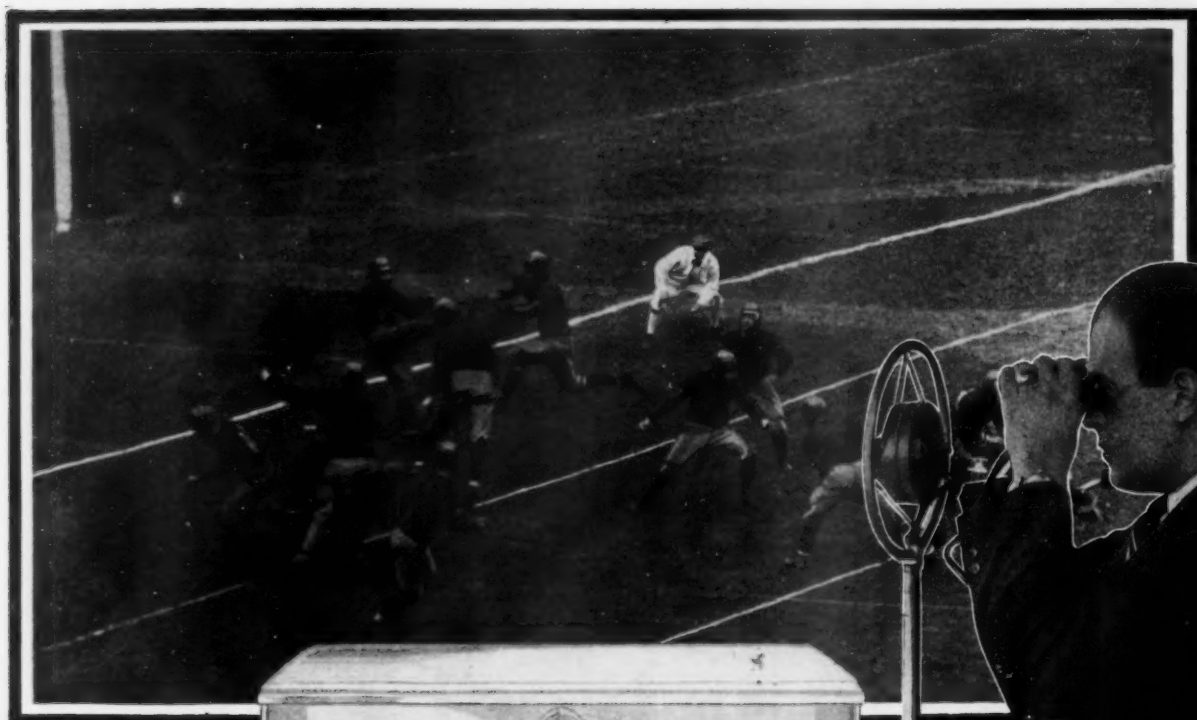

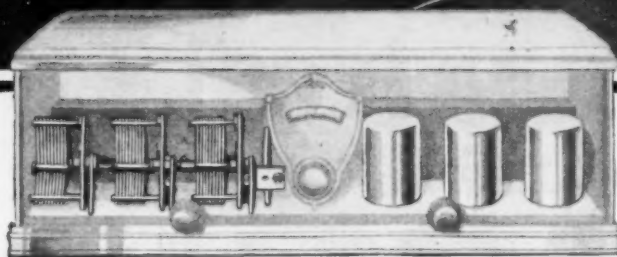The broadcast of the Army-Navy game last year was enjoyed by hundreds of thousands of fans all over the country.



Phillips Carlin broadcasting at one of the big football games.

The Big Game Comes Over-- BETTER--CLEARER

MILLIONS of enthusiastic football fans are listening this fall to the play by play broadcasts of America's greatest games. They are experiencing almost as keen enjoyment as if they were sitting in the stands. The voice of the announcer comes to them clearly and distinctly because their receiving sets are Aluminum equipped.

Leading radio manufacturers are using Aluminum extensively for shielding, for condenser blades and frames, for chasses, sub-panels, front panels and for many other parts—because Aluminum so ideally meets the varied conditions that radio design presents.

It combines remarkable shielding properties, high electrical conductivity, great strength and extreme lightness.

Examine the set you contemplate buying. If it is Aluminum equipped you may rest assured that the manufacturer has done everything in his power to give you the finest possible reception.

And if you are building a receiving set use Aluminum for finest results.

We will gladly send you the booklet, "Aluminum For Radio," which explains the varied radio uses to which Aluminum is adapted.

ALUMINUM COMPANY OF AMERICA

ALUMINUM IN EVERY COMMERCIAL FORM

2463 Oliver Building
Pittsburgh, Pa.



Offices in 19 Principal
American Cities

ALUMINUM

The mark of Quality in Radio



In the Sets Designed by Leading Engineers

Faradon Capacitors are specified as standard equipment where electrostatic condenser long life and durability is essential.

Faradon Capacitor marks quality. Keep this in mind when considering a new set, kit or replacement parts.

WIRELESS SPECIALTY APPARATUS CO.

Jamaica Plain, Boston, Mass., U. S. A.

Established 1907

Faradon

Electrostatic Condensers for All Purposes

2202

Tell them you saw it in RADIO

5



Here is a Real DYNAMIC Speaker Amplifier



Nothing else like it on the market

Remler Audio Transformers are Different Because They are Designed for Dynamic Speakers

NO HUM from this super power amplifier and *B* eliminator—even with the husky "250" power tube. Remler has so thoroughly engineered this power amplifier that the hum is eliminated. By scientific placing of parts and by skillful engineering Remler makes it so simple for you to assemble this amplifier that you are assured in advance of complete success. The new Remler audio transformer in the last stage—designed especially for the dynamic loud speaker and the new Remler output transformer—the only one of its kind available—allows you to get the most out of a dynamic speaker for the FIRST time. There is no

other output transformer like it on the market. Nothing just as good. It's a brute in size and a sure-fire performer. It delivers better and purer tonal qualities to the loud speaker than any other known amplifying device. You will marvel at the fidelity of reproduction. You have never heard anything like it before. Only Remler gives you this modern up to date equipment. This amplifier is known as the No. 950. The metal base goes with the kit. Everything is included—even the screws, nuts, wire and a simple diagram of connections.

Price for All Parts—Less Tubes, \$114.00

The New REMLER

29


A RECEIVER that looks as good as it works. Finished in beautiful lacquered copper. Screen grid amplifier unit with individual compartment shields. The entire unit is assembled, wired and laboratory matched and balanced in the Remler factory. Clean cutting 10 KC. selectivity. The new Remler audio transformer gives reproduction such as you have long waited for.

Price for Complete Kit....\$131.25

Set Builders—Dealers:

ORDER your Remler equipment from us. We make prompt deliveries anywhere. Out of town set builders and dealers can wire us for immediate shipment. Express or parcel post delivery to out of town customers. Over-the-counter deliveries to local trade. We carry a complete stock of the best known national lines. Get your tubes, batteries, speakers, eliminators and other supplies from us. Let us convince you that our service is better than ordinary. Usual discounts allowed to set builders and dealers.

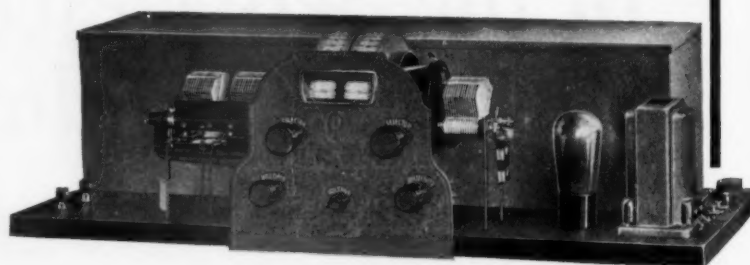UNITED RADIO SUPPLIES CO.
1062A Howard Street, San Francisco, Calif.



A Professional Job

HERE is a receiver for the most discriminating fan. It can be assembled in a few hours. Simple, explicit wiring charts and instructions make it a pleasure to assemble this new kit—the best of any we have seen this season. Metal chassis with all holes punched. Beautiful escutcheon plate. The illustration fails to do justice to this new "29" Remler SUPER. Acknowledged by engineers as the finest thing in radio for the season.

THIS COUPON SAVES TIME

UNITED RADIO SUPPLIES CO.
1062A Howard St., San Francisco, Calif.

Per your ad in "RADIO" send me at once the following new REMLER items, for which remittance of \$50.00 is enclosed, balance to be paid by me C.O.D.

Name.....

Street and No.....

City and State.....

DESIGNED
TO RENDER
UTMOST IN
SERVICE

FROST-RADIO

PRICED TO
GIVE YOU
UTMOST IN
VALUE

A Complete Line That Was Built
For Your Specific Requirements



Frost Volume Control

Gives complete, stepless and wonderfully smooth control of volume and oscillation. Wearproof roller contact arm, Bakelite case and dust cover. \$2.00 and \$2.25.



Frost Volume Control With D.C. Switch

Equipped with sturdy German silver switch mounted on Bakelite panel, and with switch points fitted with sterling silver contacts, this Volume Control gives quick operation, positive-locking off position and saves space. For battery operated sets. \$2.25.



Frost Gem Rheostats

Made to deliver a service that is not usually expected from little rheostats like these. Mighty good little rheostats, taking up little space and supplied either plain or with D.C. switch. Easy to solder to. Plain, 75c. With switch, \$1.00.




Frost Bakelite Rheostats

Long the standard air-cooled Bakelite Rheostat, as well as the original of this type. Resistance wire is wound on die cut Bakelite strip over moulded Bakelite frame. Wide choice of resistances. \$1.25 and \$2.50.



Frost Bakelite Rheostats with D.C. Switch

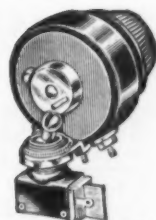Cleverly mounted German silver D.C. battery switch is firmly attached to Bakelite panel on back of rheostat, affording quick on and off control of filament current. 2 to 75 ohms. \$1.35.



Frost Volume Control With A.C. Switch

We equip our famous Volume Control with approved A.C. Snap Switch tested to carry 250 volts at 3 amperes, so that both switch and volume control may be handled by single knob. \$2.75 and \$3.00.



Frost Gem Volume Control

Identical with our standard size Volume Control units except in size. Gem units are only 1 1/2 in. in diameter, and 3/4 in. thick. Great space savers. \$2.25 and \$2.50.



Frost Hum Balancer

Simply turn the slotted head shaft with screw driver to regulate. Smooths the ripple out of A.C. current. Precision built. \$1.00.



Frost Convenience Outlets

Fit std. outlet box. Brush brass or Bakelite plates. \$1.00 to \$3.00.




Frost Moulded Mica Condensers

Cannot be affected by moisture or climate. Moulded Bakelite with finest mica dielectric. Easy to attach. 45c. to 90c.




Frost Approved A.C. Switch

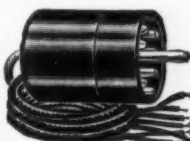Single hole mount 110 volt A.C. Snap Switch. Tested to 250 volts, 3 amps. Underwriters' approved. 75c.



Frost All-Bakelite Cable Plug

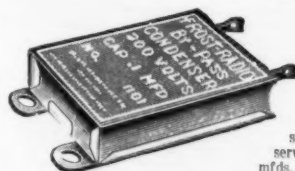Terminals cannot work loose even when overheated. Color code moulded into Bakelite. Best quality cable, with colored rubber insulation on wires. Has 5 ft. seven strand braid covered cable. Plug and cord only, \$2.25. Baseboard or sub-panel socket, 75c.



Frost By-Pass Condensers

Made from finest materials, thoroughly seasoned, vacuum impregnated and hermetically sealed. Accurate capacities and conservative voltage ratings. .1 to 2 mfd. 80c. to \$2.00.




Frost Fixed Resistances

Die cut flexible Bakelite strip holds windings firmly in place. Terminals are staked into Bakelite. .4 to 1000 ohms. Also as center tapped resistances, 6 to 64 ohms. 15c. to 50c.

Frost Push-Back Hookup Wire

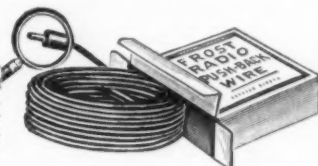Slide back the braid for soldering, then slip braid back over soldered joint. No. 18 double cotton covered, impregnated wire, tinned. 50 ft. roll, 80c.



Mail Coupon Below For Our Complete 16 Page Catalog

HERBERT H. FROST, INC.

Main Office and Factory: ELKHART, IND.
New York City CHICAGO San Francisco

HERE'S A BOOK THAT
YOU SHOULD SEND
FOR TODAY

It costs but little—10c brings it to your door—and contains a vast amount of valuable information about rheostats, volume controls, switches, jacks, plugs, condensers, circuits, etc. It's a book every fan should have. Fill out and mail coupon today for your copy.

The
FROST-RADIO
1928 Catalog
A handbook of
useful information

HERBERT H. FROST, INC.

160 North La Salle Street, Chicago

Send me your new Frost Data Book, containing valuable radio information and facts about your complete line of parts. I enclose 10c.

My Name

Street Address


City

State


(Are you a professional set builder?.....)

Frost Heavy Duty Filter Condensers

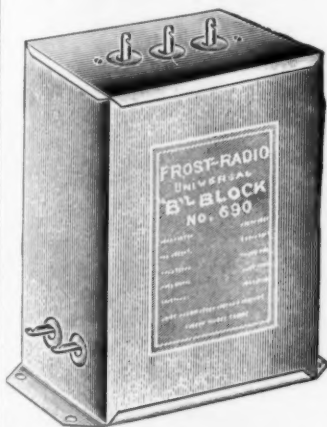We use only finest quality linen paper and highest grade foils in building these Filter Condensers. Conservative ratings. Designed to give longest service with entire freedom from trouble. .5 to 2 mfd. \$1.40 to \$7.00.



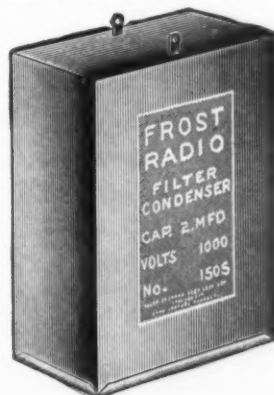Every particle of material used is of tested quality. Entire condenser enclosed in hermetically sealed cases after vacuum impregnation. Gold bronze lacquer finish; tinned terminals. \$18.00.



Tell them you saw it in RADIO

HFL

The Marvelous New Screen Grid

LIST PRICE
\$195.00


ISOTONE

radio
phonograph

America's Finest Custom Built Receiver

33 Modern Improvements

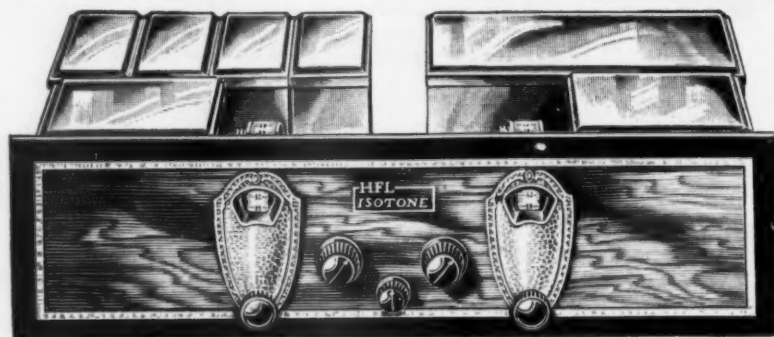1. ABSOLUTE ONE SPOT OPERATION, 450 KILOCYCLES
 2. PERFECT PHONOGRAPH RECORD REPRODUCTION
 3. OPTIONAL LOOP OR ANTENNA OPERATION
 4. PERFECT 8 KILOCYCLE SELECTIVITY
 5. EXTREME SENSITIVITY, UNLIMITED RANGE
 6. A.C. POWER SUPPLY OR BATTERY OPERATION
 7. THREE STAGE SCREENED GRID AMPLIFIER
 8. EXQUISITE TONE QUALITY FIVE POWER TUBES
 9. COMPLETE CONSTRUCTION IN ONE HOUR
 10. NEW SIGNAL STATIC BALANCE CONTROL
 11. MANUALLY TUNED R.F. AMPLIFIER STAGES
 12. THREE STAGE PUSH PULL AUDIO AMPLIFIER
 13. SPECIAL AUDIO FREQUENCY FILTER
 14. AUTOMATIC TUBE BALLASTING CONTROL
 15. MEASURED GAIN OF 65 PER STAGE
 16. OPERATES ALL DYNAMIC LOUD SPEAKERS
 17. DUAL PHONO RADIO VOLUME CONTROL
 18. LABORATORY ASSEMBLED AND MATCHED UNITS
 19. BUILT IN MICROPHONE TRANSFORMER
 20. ABSOLUTE STABILITY—CANNOT SQUEAL OR HOWL
 21. CONSECUTIVE NUMERICAL DIALING
 22. BEAUTIFUL GOLD DIALS—WALNUT PANEL AND KNOBS
 23. COMPLETE INTER UNIT SHIELDING
 24. VELVET SMOOTH—LINE DRIVEN DIALS
 25. AUTOMATIC TUBE DISCONNECTING SWITCH
 26. COMPLETELY SHIELDED—INVISIBLE WIRING
 27. CADMIUM PLATED STEEL SUPPORTING BASES
 28. PYRALIN DIFFUSED DIAL ILLUMINATION
 29. BUREAU OF STANDARD SHIELDING 24 GAUGE
 30. NEW TYPE LOUD SPEAKER IMPEDANCE
 31. SPRING SUSPENDED TUBE SOCKETS
 32. SPECIALLY DESIGNED TANK CONDENSERS
 33. NEW MIXER BALANCING PADDER
- AND MANY OTHER MODERN IMPROVEMENTS



Unlimited Range. This excellent instrument employs practically every new engineering feature known to radio science. The range of the Isotone is almost unlimited. The three-stage screened grid amplifier having the unusually high gain of sixty-five per stage can be hand tuned by the operator which results in a perfectly balanced instrument. The 450 kilocycle amplifier allows absolute one spot tuning.

Perfect Selectivity. Actual laboratory tests have shown that an Isotone can be tuned so that it will select an eight kilocycle band. This is undoubtedly the highest attainment in selectivity which has been obtained up to this time. Local station interference will never trouble the owner of an Isotone.

Exquisite Tone Quality. Five power tubes are used in the receiver which are responsible for the unsurpassed tonal quality of the instrument. An automatic tube ballasting system eliminates all voltage surges and phonograph records can be played through the three-stage push pull amplifier by simply throwing the control knob on the front of the panel. The instrument operates perfectly with a standard 180 volt B unit and a battery or with the new Isotonic model 5 ABC power supply.

Easy to Construct. The Isotone can be completely constructed and wired by anyone in less than one hour. The factory assembled and wired Isotonic units which make up the instrument are individually laboratory tested and are unconditionally guaranteed to be mechanically and electrically perfect. The Isotone kit comes absolutely complete with all instructions. Nothing else to buy. Requires 3 CX322, 3 CX312A, 2 CX371A, 2 CX301A tubes.

Isotonic Screened Grid Amplifier

Operating frequency 450 kilocycles allowing absolute one spot operation. Extremely sensitive, having a measured gain of 65 per stage under actual operating conditions. Absolutely stable, cannot squeal or howl. Arranged for sub panel mounting and sold completely assembled and wired. Overall size 11 1/2" long, 5 1/4" wide, 6 1/2" high. Requires 3 UX222 and 1 UX112A tubes. Price

\$60

HFL Audio Amplifier

Three stage push pull, with built in microphone transformer and audio filter. Operates all dynamic speakers. All instruments and wiring perfectly shielded. Arranged for sub panel mounting and sold separately completely assembled and wired. Overall dimensions 11 1/2" long, 5 1/4" wide, 6 1/2" high. Uses 2 UX112A and 2 UX171A tubes. Price


\$55

HFL ABC Power Unit


This perfect device was designed especially for the Model 10 Isotone. It is absolutely free of A.C. hum, voltage surges and motor boating. Oversize condenser sections, having an unusually high breakdown rating allowing perfect low note reproduction in the receiver. The Model 5 supplies A voltage 6 volts at 2 1/2 amperes—Plate voltages 45-90-135 and 180 and C Biasing voltages of 40 and variable 0 to 15 volts. Mounted on a satin finished Cadmium plated steel base with steel cover. Unconditionally guaranteed against breakdowns and to operate perfectly with the Model 10 Isotone Receiver. Size 11" long, 10" wide, 8 1/4" high. Requires 1 UX 280 tube for operation. Price

\$95

List Price, Less Tubes.....**\$195.00**

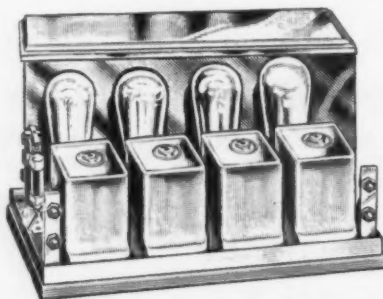

HFL Audio Amplifier \$55

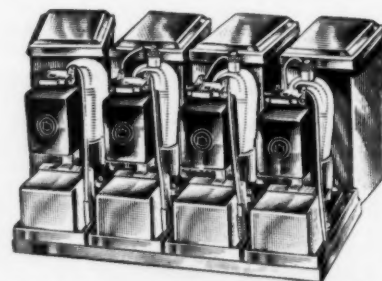

HFL Screen Grid Unit \$60

Immediate Deliveries

8 Hour Mail Order Service

Radio Dealers Supply Service

Wholesale Division of

OFFENBACH
ELECTRIC COMPANY
"The House of a Million Radio Parts"

1452 Market Street San Francisco, Calif.



HFL
ABC
Power
Supply
Model 5
\$95.00



HFL
AUDIO
TRANSFORMER

HFL

NEVER before has any receiver possessed such selectivity and unlimited power. Imagine perfect separations on every wave channel. Absolute 10 kilocycle splits—right alongside of the most powerful locals in the country.

You can choose your station with an Isotone and *you can get that station*. You can get it clear and you can get it without the annoying overlapping swishes that ordinarily ruin long distance reception.

The HFL Isotone is the supreme radio achievement. We believe that no other receiver in the country can show an actual radio frequency gain of 65 per stage consistent with absolute 10 kilocycle band selection.

Nothing has been sacrificed to obtain this unprecedented efficiency. The instrument is a beauty to behold. The three-stage push-pull audio amplifier produces tone quality that is a revelation. There is a choice of radio or phonograph reproduction. A master control switch—automatic ballasting systems—hand-tuned filter transformers—these and over 25 other new features play their part in making the Isotone the greatest radio receiver of all time.

Write to the factory for complete information and an eight-page booklet giving circuits and all technical data.

Can be Constructed by Anyone

There is nothing complicated about the construction of an ISOTONE. Each of the three units is assembled, wired and laboratory tested at our factory. All you have to do in order to reproduce these wonderful results for yourself is to take a standard kit of ISOTONE parts and assemble the instrument with a few nuts, bolts and only ten wires. There is nothing to go wrong. Each piece fits together with absolute precision, and in less than an hour you can realize what is acclaimed by women as the most beautiful receiver of the day—and admitted, beyond a question of doubt, by radio engineers as the most efficient radio phonograph ever designed.

HIGH FREQUENCY LABORATORIES

Office R. 28 N. Sheldon St.
CHICAGO, ILL.

FREE

Circuit
Diagram
And All
Information




Model 10 ISOTONE

70

Stations
in one evening

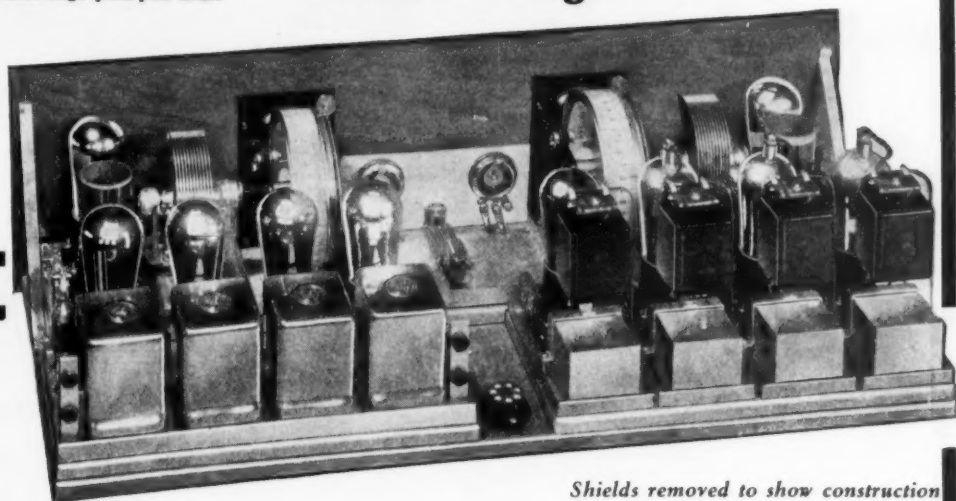An amazing demonstration
of ultra selectivity and extreme
distance range.



Shields removed to show construction

Absolute Guarantee

Every ISOTONE kit and each ISOTONIC unit is fully guaranteed. All H. F. L. items must be mechanically and electrically perfect. Each instrument must test up to the standard set by our laboratories. Any unit that does not operate perfectly will be immediately replaced at no charge. No arguments—no lengthy correspondence—your ISOTONE must be right or we will make it right. Our guarantee gives you absolute protection. **BUILD YOUR ISOTONE NOW** and have the finest receiver in your neighborhood. Send for full particulars **TODAY**.

The Coupon Brings Complete Information

HIGH FREQUENCY LABORATORIES
Office R, 28 North Sheldon Street,
Chicago, Illinois.

Gentlemen,—Without obligation, please send complete information on the ISOTONE receiver and the ISOTONIC A. C. power supply.

Name


Address

City..... State.....

(Please print plainly)

Tell them you saw it in RADIO

OUT-SELLING ALL

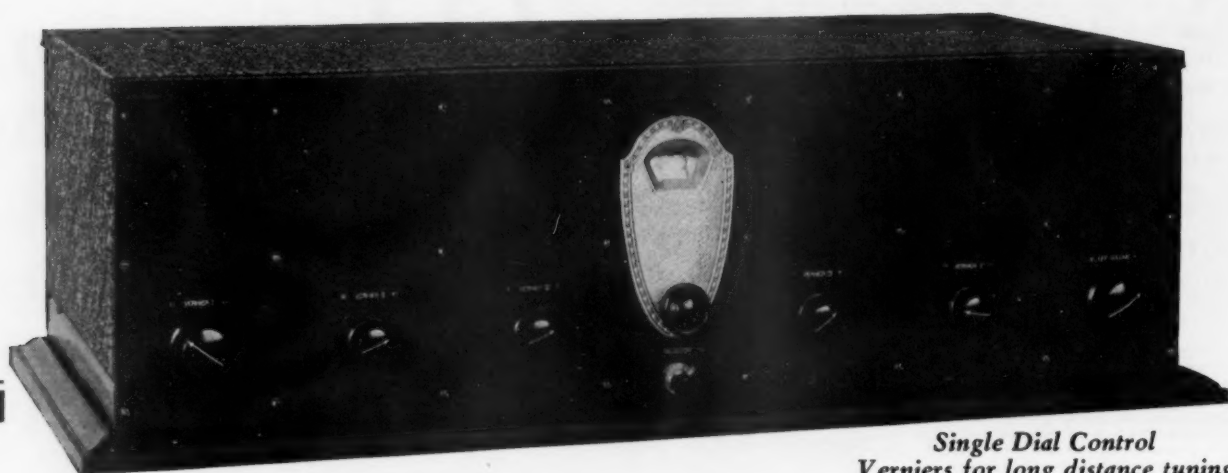

Single Dial Control
Verniers for long distance tuning

"De Luxe Model" SARGENT-RAYMENT SEVEN

Uses Four Screen Grid Tubes, Detector, and Two Audio

A Station for Every Dial Degree

THAT is the average performance of the Sargent-Rayment Seven over the entire dial. Tuning from slightly over 200 meters up to 550 meters, this receiver will, under average night-time conditions, receive 100 stations per evening.

The outstanding performance of this receiver is due to very careful design throughout. Four stages of screen grid tube amplification are used. Each stage is completely isolated by heavy aluminum shielding. Lap Shield joints are used to insure against any possibility of having the slightest leakage from stage to stage. Each screen grid, plate and filament wire is by-passed and nine radio frequency chokes are used to prevent inter-coupling. As a result, the set is not critical to operate and does not oscillate at any wavelength. Even with the full power turned on at 200 meters the receiver is fully stable.

THE ANTENNA CIRCUIT

An entirely new type of antenna circuit is used. This input circuit at once assures fine selectivity and good sensitivity, and at the same time it is so connected that antenna capacity does not affect the setting of the gang condenser. Thus, although the antenna is sharply tuned, it is not necessary to compensate for changes in wavelength. This is a special feature released for the first time in this set.

The full power of four screen grid tubes gives a degree of sensitivity that has never before been attained in anything that has been placed on the radio market. No suppressors or other counteracting devices are used to prevent oscillation, so that the full amplification of each tube becomes useful. As a result, the receiver will produce a louder signal on a distant station than any other set that can be put up against it, and the selectivity, which is 10 kilocycle in most cases, enables the owner to get long distance reception during the early evening hours when all the local stations are on.

A Guarantee by the Designers

Some very broad claims have been made in our advertising of the Sargent-Rayment Seven. Were it not for the fact that this set is unique in design these claims could not rightly be made. The Sargent-Rayment Seven has been thoroughly tested under the most adverse conditions and is unconditionally guaranteed to do everything claimed in our advertising. In case anyone desiring to purchase one of these sets is in doubt about this point, we will be glad to arrange so that that person can obtain the set on a ten day money back trial basis.


We are perfectly willing to stake our professional reputations as radio designers on this circuit and will leave it to the judgment of the radio fans at the end of the season whether or not any misleading statements have been made.

(Signed) E. M. SARGENT, L. C. RAYMENT

Seven Outstanding Features

- 1 Ten kilocycle selectivity all over the wave band.
- 2 More power, more amplification, more sensitivity than ever before available in any receiver.
- 3 All present distance records smashed. Sets a new standard.
- 4 Efficient all over the wave band. Plenty of power on the long waves.
- 5 Tone quality unsurpassed. Uses the latest audio transformers. 210 or 250 tube can be used in last stage if desired.
- 6 Tuning controlled by handsome, illuminated revolving drum. Only one control for master selector. Fine tuning verniers available for use when wanted.
- 7 Requires no cabinet. Finished in grained aluminum with black and white trimmings, or in brown, crackle, crystalline lacquer.

THE OTHER KITS!

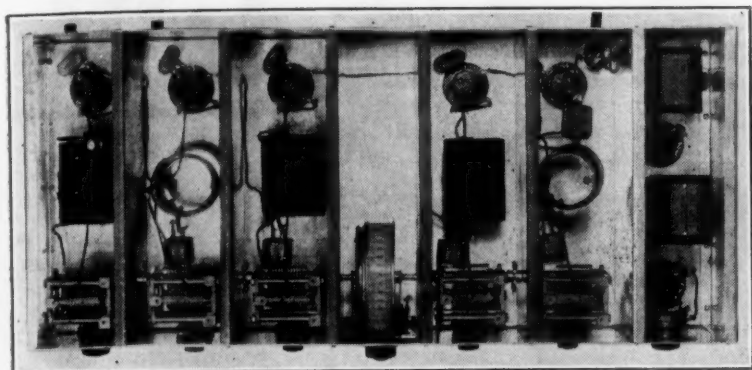

"Built Like a Battleship"

NOTE THE CONSTRUCTION

The above illustrates a top view of the receiver with the cover removed, giving an idea of how substantially this set is built. It shows the complete isolation of each radio frequency stage, the single drum control on gang condensers and the spacing and angling of the coils to prevent feed back. This is a triumph in radio set construction and at the Radio Shows at which it has been exhibited it has attracted widespread attention and comment.

THE AUDIO SYSTEM

The audio system employed in the Sargent-Rayment Seven is noted for its clearness of tone. The small-sized Clough transformers Nos. 255, 256 and 251 have been purposely selected because they do not over-emphasize the base notes at the expense of the high ones. More powerful transformers could have been selected, but as the set contains plenty of radio frequency power a distinct gain was made by choosing the less powerful but clearer small transformers.

WHAT FINISH DO YOU LIKE?

The Sargent-Rayment Seven is supplied in two finishes. For the dyed-in-the-wool radio fan there is a standard grained aluminum finish, while for those who prefer a darker set which will better harmonize with living room furnishings we are prepared to supply the usual brown, crackle, crystalline finish. The set can be obtained either built up or in kit form, with finish desired at the prices given below. The models are identical in every respect except for the finish.

The De Luxe model is put out exclusively by Radio Constructors Corporation and can only be bought from us or from jobbers listed on this page. All parts are manufactured by Silver-Marshall and the De Luxe Finish is applied by us.

We especially recommend this model. It is unexcelled in appearance and harmonizes with all furnishings.

PRICES—FOR THE COMPLETE KIT

The SM-710 Sargent-Rayment Seven Kit is complete in every respect. All parts are inspected at the Silver-Marshall factory for both electrical and mechanical defects and are fully guaranteed by both Silver-Marshall and by Radio Constructors Corporation to be in first-class condition. Everything is carefully packed to withstand shipment. Complete instructions for assembling and wiring the kit are included. These instructions are so explicit and so well illustrated that the novice will have no difficulty in following them.

All hardware, screws, nuts, washers, brackets—everything necessary to build the set—is included. There is nothing additional to be bought. The kit includes even the "cabinet."

No. 710 Standard Model, Grained Aluminum Finish, Code Word "Mercury".....\$130.00
No. 810 De Luxe Model, Brown, Crackle Crystalline Finish, Code Word "Venus".....\$140.00

FOR THE BUILT-UP SET

The completely built, wired, and tested Sargent-Rayment Seven receiver is carefully packed in a specially cushioned packing case. It exceeds the parcel post size limits and hence must be shipped by express. Full instructions for connecting the set to the power supply and operating it are included.

No. 711 Standard Model, Code Word "Neptune".....\$150.00
No. 811 De Luxe Model, Code Word "Jupiter".....\$160.00

IMMEDIATE DELIVERY

RADIO CONSTRUCTORS CORPORATION

357 Twelfth Street

Oakland, Calif.

Dealers

These jobbers can supply you with either the kit or built-up set

WASHINGTON

WEDEL CO.,
520 Second Ave., Seattle, Wash.
HARPER-MEGGEE, Inc.,
4th at Blanchard St., Seattle, Wash.
INLAND RADIO CO.,
922 West First, Spokane, Wash.
HARPER MEGGEE & CO., INC.,
South 214 Howard St., Spokane, Wash.

OREGON

STUBBS ELECTRIC CO.,
75 6th St., Portland, Ore.
UNIVERSAL SPECIALTIES CO.,
40 N. Ninth St., Portland, Ore.

SOUTHERN CALIFORNIA

HERBERT H. HORN CO.,
1629 S. Hill St., Los Angeles, Calif.
C. C. LAWTON,
1125 Wall St., Los Angeles, Calif.
RADIO SUPPLY CO.,
912 S. Broadway, Los Angeles, Calif.
RADIO MFRS. SUPPLY CO.,
1000 S. Broadway, Los Angeles, Calif.
RADIO MFRS. SUPPLY CO.,
Long Beach, Calif.

MODERN ELECTRIC CO.,
308 West Center St., Anaheim, Calif.
SUNSET ELECTRIC CO.,
1141 1st St., San Diego, Calif.
WILLIAMS AND KLENTZ,
409 5th St., Santa Ana, Calif.

NORTHERN CALIFORNIA

ELECTRIC SUPPLY CO.,
370 11th St., Oakland, Calif.
ELECTRIC SUPPLY CO.,
Room 250, Chronicle Bldg., San Francisco.
COAST RADIO SUPPLY CO.,
648 Howard St., San Francisco, Calif.
GILSON ELEC. SUPPLY CO.,
1106 Madison St., Oakland, Calif.
KIMBALL-UPSON CO.,
607 K St., Sacramento, Calif.
OFFENBACH ELECTRIC CO.,
1452 Market St., San Francisco, Calif.
PACIFIC RADIO SALES CO.,
357 Twelfth St., Oakland, Calif.

COLORADO

VREELAND RADIO CORP.,
1639 Tremont St., Denver, Colo.

NEW MEXICO

PACKARD SERVICE STATION,
417 West Gold Ave., Albuquerque, N. M.

UTAH

INTERMOUNTAIN ELECTRIC CO.,
43 East 4th South, Salt Lake City, Utah.
LUND RADIO CO.,
Fairview, Utah.

NEVADA

RENO MOTOR SUPPLY CO.,
Reno, Nevada.

DEALERS—SET BUILDERS

Get established now in your community as headquarters for the Sargent-Rayment Seven. Fill in the attached coupon and send it to us for full information.

Radio Constructors Corporation,
357 Twelfth Street,
Oakland, Calif.

Please send me at once full details regarding the Sargent-Rayment Seven. I am a dealer or professional set builder and buy my supplies from the jobbers listed below.

Name.....

Address.....


City and State.....

Name of Jobber.....

Name of Jobber.....

\$130

FOR ALL PARTS & CABINET

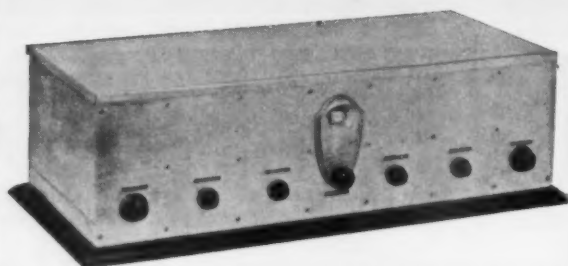

The cabinet goes with the kit at \$130.00. Aluminum, grained finish. Brown crackle lacquer finish \$10.00 additional.

\$150

FOR THE ASSEMBLED SET

The KIT

For those who want to build their own receiver we offer the Sargent-Rayment Seven Kit, complete with aluminum cabinet, as illustrated, for the surprisingly low price of \$130.00. The kit forms its own cabinet when assembled and gives the set a beautiful appearance. If you don't like the aluminum cabinet as pictured on this page, we can supply a "De Luxe" cabinet—the same cabinet exactly as shown excepting that a coating of dark brown crystalline is applied to the aluminum, giving the set the appearance of the factory sets now on the market with crystalline finishes. This finish costs you \$10.00 extra. All parts for this kit are guaranteed. Complete wiring diagrams and instructions for assembly go with each kit. You can't go wrong. Immediate deliveries guaranteed. Positively no delays.

Sargent-Rayment Receiver Out-performs All Others

OUTSELLING everything in the kit field, the new Sargent-Rayment 7 is piling up sales records that exceeded our fondest expectations. No wonder—there is nothing to compare with it for DX range—selectivity—tone and simplicity. A single dial control set. Verniers needed for extreme long distance reception only. We predict that this receiver will sell in larger quantities than all other kits combined. It is our leader. We always have a stock on hand—kits and completely built and wired receivers, ready to operate. Shipments made on same day your order reaches us. Positively no delays.

64 Clear Channels

On November 11th the new wave allocations were made effective. For the first time in years the DX fan can now get his money's worth out of a DX receiver. You can choose from six Eastern stations nightly, if you live on the Pacific Coast—and from six Western stations nightly if you live in the East—and be assured of no interference within 10 kilocycles or more. All told, there are 64 channels throughout the United States that are fairly clear of interference and heterodynes. Cash in on the greatest DX season in radio. Get your 10 KC Sargent-Rayment receiver right now and get in on the sport. Why be content to listen to a separate local station when the Sargent-Rayment receiver enables you to bring in 100 stations during an evening? Stations 1000 miles away pound through like locals. The tone quality is SUPERB.

The SET

Completely assembled, wired and tested on the air for extreme long distance reception. Perfectly balanced for 10 KC selectivity and thoroughly inspected by competent engineers who specialize solely on the construction of this set. When a completely wired Sargent Receiver leaves our establishment you have three guarantees to protect you—one from the inventors, another from the constructors and a final guarantee by ourselves. The completely assembled job sells for \$150.00 in the aluminum satin finished cabinet, as pictured. The De Luxe finish (brown crystalline) costs \$10.00 extra. Both models are in stock for shipment on the same day your order reaches us. Send \$40.00 today—balance c.o.d.—get our special discounts to dealers and set builders. Order now!

A. C. OPERATION WITHOUT HUM

RECENT developments in power units makes it possible for us to offer you the new Knapp Dry A Power Supply, a guaranteed power unit which has been given a thorough test and is positively unequalled for reliability and sure-fire performance. No hum whatsoever. This Knapp A Power unit and a good B eliminator will make your Sargent-Rayment receiver an AC operated instrument free from annoying AC hum. You will get better tone quality—longer life from tubes and nothing to worry about. Price for the Knapp "A" is \$37.50. Immediate shipment from stock. No delays. We guarantee this power unit without reserve. There is no satisfactory substitute for it.

Immediate Deliveries. 4-Hour Mail Order Service

SET BUILDERS AND DEALERS—

ORDER DIRECT FROM

Radio Dealers Supply Service

Wholesale Division of



"The House of a Million Radio Parts"

1452 Market Street San Francisco, California

RADIO DEALERS SUPPLY SERVICE

Wholesale Division of
OFFENBACH ELECTRIC COMPANY
1452 Market Street,
San Francisco, Calif.
Send me

☒ SM-710 Sargent-Rayment Kit, unwired,
List \$130.00.

☒ SM-710 Sargent-Rayment Set, completely,
wired, List \$150.00.

Brown Crystalline Finish—\$10.00 Extra

for which I attach a deposit of \$40.00, the balance to be paid for C. O. D. upon receipt of shipment.

Name.....

Street and Number.....

City.....State.....

Send the coupon now for your Sargent-Rayment Seven kit, or completely wired receiver. Telegraph orders promptly filled. Mail order service to all parts of the world. All tubes and accessories can be purchased from us at regular dealer discounts.

~~THEY'RE THERE~~ IN THE WORLD'S FINEST RECEIVERS

STANDING guard at the door of tone, Thordarson audio and power transformers do their part in making real musical instruments of hundreds of thousands of radio receivers annually.

Leading receiver manufacturers are well aware of the important relationship between the choice of transformers and the musical characteristics of their instruments. No wonder, then, that the majority of manufacturers of quality radio receivers have turned to Thordarson as the logical transformer source.

When buying your receiver, insist on Thordarson amplification and power supply. The set manufacturer who uses Thordarson transformers can be depended upon to have the balance of his receiver in keeping with this high standard of performance.

Custom set builders will find Thordarson transformers to meet every radio need at their nearest parts dealer.

THORDARSON RADIO TRANSFORMERS

SUPREME IN MUSICAL PERFORMANCE

Tell them you saw it in RADIO

*New Jensen
Model 6 Cabinet*

In size and appearance the new Model 6 Jensen Cabinet is ideally suited for use in the most artistically furnished living room or music room.

Jensen Dynamic Speakers are made in types to operate with 110 volt A. C. house current, 6 volt storage battery, "A" eliminator or trickle charger, 110 volt D. C. house current and 90 to 180 volt D. C. current as provided by many of the late model radio sets. The sensitivity of the instruments is the same in any case.



Jensen Dynamics Will Build Sales For You

SHREWD dealers know that radio sets sell best when they sound best. These dealers are increasing their set sales and dynamic speaker sales every day by using Jensen Dynamics for demonstration. It is Jensen reproduction "true as the original" which provides this distinct selling advantage. It is the absolutely true,

dependable reproduction of the entire musical scale which accounts for the vast public preference for Jensen tone quality. And the new distinctive cabinets in which

Jensen units are enclosed is the final feature which clinches sales. Console cabinets sell better too when they are Jensen equipped.

All types of Jensen Dynamic Speakers are now ready for delivery to the trade. Dealers, jobbers and manufacturers are invited to write for particulars and an immediate source of supply.


Jensen Radio Manufacturing Co.

212 9th Street, OAKLAND, CALIF.

338 N. Kedzie Avenue, CHICAGO, ILL.

JENSEN PATENTS ALLOWED AND PENDING
Licensed under Lektophone and Magnavox

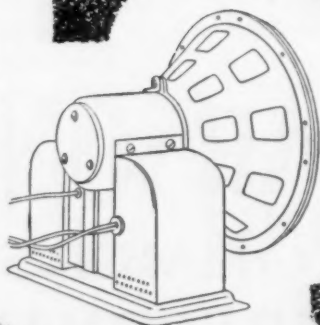Jensen Dynamic Speaker Units may be quickly and easily installed in radio or phonograph console cabinets. They may be operated with the same current supply as used for the radio receiver or electric phonograph. Prices for the Units for console cabinet installation range from \$40.00 to \$55.00.





Bring the games to the crowd—and they'll welcome your message.



MIK 1
List Price \$135.00
Without Tubes



PAM 16 or 17
List Price \$125.00
Without Tubes

Where Crowds Assemble--Use the Voice of a Samson

YOU can reproduce with great volume any radio music on the air or recreate the best recorded music by using a PAM 16 or 17. For the radio music connect PAM to detector tube of any radio set or to a tuning unit, and for recorded music connect it to a magnetic phonograph pick up.

You can make announcements before, during or after the game if you use a Samson MIK 1 (a 2-stage entirely AC operated microphone input amplifier) which uses the same high grade transformers we have supplied many of this country's better broadcast stations.

For even greater volume use the PAM 19 or 20 which has approximately $2\frac{1}{2}$ times the undistorted output of the PAM 16 or 17.

Send for illustrated bulletin RB1 describing these units and other items showing why "PAM AMPLIFIERS are a Sound Investment."

Main Office: Canton, Mass.
Manufacturers Since 1882

Samson Electric Co.
MEMBER
RMA

Factories at Canton
and Watertown, Mass.


Tell them you saw it in RADIO

SIMPLIFYING POWER PLANT CONSTRUCTION

TRUVOLT DIVIDER



A Universal Voltage Separator

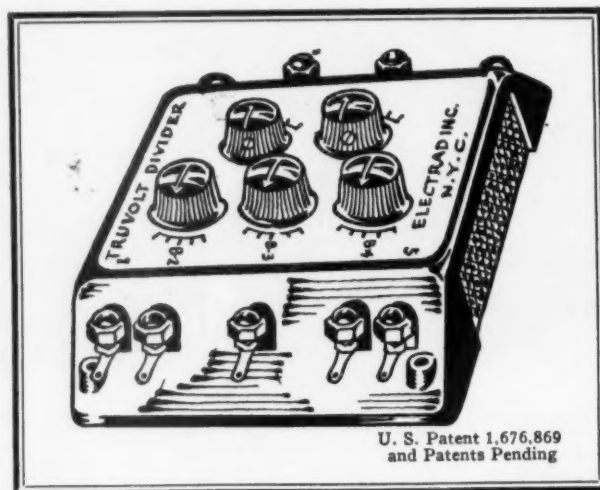

U. S. Patent 1,676,869
and Patents Pending

THE Truvolt Divider offers the radio engineer or builder of eliminators for the first time a complete wire wound resistance unit so arranged with five adjustable contacts that all required voltages may be obtained with any set or eliminator combination.

This device removes the guesswork and saves time and trouble in constructing an

eliminator. By dividing the filter voltage into usable values, it eliminates the necessity of mathematical calculations. It does away with a great deal of wiring and the need of regulator tubes.

The Truvolt Divider is not only flexible to all receiver current conditions, but it is possible, because of its inherent design, to calibrate the adjustable contacts. By the use of tables or graphs, the Divider may be adjusted to give the desired voltages without the use of a high resistance voltmeter.

Case made of genuine bakelite. Can be mounted on baseboard or sub-panel, or used as the front panel of a metal cabinet, at the same time providing binding posts for all B and C Voltages. PRICE \$12.50.

Electrad specializes in a full line of Controls for all Radio Purposes, including Television.

Write for Free Truvolt Divider Booklet giving Full Information.

FILL OUT
AND MAIL
THIS
COUPON

ELECTRAD, INC., Dept. H-11, 175 Varick Street, New York, N. Y.
Please send me descriptive circulars on the following products and put me on your
mailing list for similar literature. _____
"General Circular" _____
"Royalty Variable Resistors" _____
"Electrad Control Manual" _____
"What B Eliminator Shall I Build?" _____
I am particularly interested in _____
Name _____
Address _____
ELECTRAD, INC., Pacific
Coast Office, 905 Mission
San Francisco,
California

ELECTRAD Inc

OCT 22 1928

© CIB 3265

RADIO

VOLUME X

NOVEMBER, 1928

No. 11

Radiatorial Comment

POLITICAL speeches may simultaneously be either the most or the least obnoxious kind of radio advertising—depending upon the political beliefs of the listener.

When a man ceases to criticize the radio conditions in his locality, he has lost his interest in radio. Then there is really something the matter with it.

Radio applause cards, once as numberless as the buffalos of the great plains, are now as nearly extinct. Advertising is killing them.

Good radio humor is the best of the twice-told tales. For if it "gets over" from a radio studio it will register where the teller is present. And it is always clean.

Television will soon add "synchronize" to the slang dictionary. Its meaning requires no definition, as applied to an individual, for anyone who has watched or manipulated a receiver screen.

* * *

A RADIO operator has always been judged largely upon his proficiency in sending and receiving code. Wire telegraph operators were once valued likewise. So also was a bookkeeper gauged on his ability to add, and a typesetter by his speed and accuracy as a hand compositor. But nowadays type is set on a linotype machine, adding is done with an adding machine, and telegraph messages are sent and received by means of machine printers. Eventually, also, the great bulk of radio traffic will be sent by photoradio.

In each of these cases the operator has graduated to higher duties which require more technical knowledge and which command higher pay. The world is rapidly approaching the point where it will be difficult to find men to cope with the modern machines which are being created. Radio, in particular, is a new field and is destined to great progress. The radio operator

who keeps in step with this progress is also destined to a great future.

* * *

AN SOS is a signal for a broadcast station to cease transmitting. No matter how trivial or how important its program, whether a jazz request number or an address by the President of the United States, it must give way to the distress call. This was absolutely necessary to prevent interference in the old days of spark transmitters. But with the use of continuous waves from vacuum tube transmitters it is as needless as a hitching post for automobiles. No broadcast station on 545 meters or under need cause any interference on 600 meters. The portion of this law which requires a broadcast station to maintain continuous watch on 600 meters is virtually a dead letter. In view of the progress which has been made since the law was passed, it should now be wiped off the statute books. Aside from the unnecessary annoyance that it may cause broadcast listeners it may cause a direct financial loss to a station which is broadcasting a sponsored program.

* * *

THE subject uppermost in broadcast discussion today is the probable effect of the Federal Radio Commission's order that nine-tenths of the stations change their wavelengths on Armistice Day. At first glance it might appear that in this new deal just as much satisfaction would have been created by dealing five hands, one to each zone, from a well-shuffled deck of cards.

Yet a little analysis shows that the deck has been carefully stacked in an endeavor to improve reception conditions for the listener. So, aside from the temporary inconvenience of changing the logs or dial markings of most of the stations ordinarily heard, the average listener will probably hear his favorite stations to better advantage than he did last winter.

To understand the plan upon which the new allocations are based, it is necessary to know that there are ninety-six channels or highways in the broadcast spectrum between 550 and 1500 kilocycles. Each of these channels is ten kilocycles wide, the modulating or sound frequencies extending for five kilocycles on both sides of the station's carrier frequency. Incidentally, since the station frequencies are designated in multiples of ten so as to give this ten kilocycle separation, it is more convenient and less confusing to omit the final cipher and to designate the channels by numbers from 55 to 150, corresponding to 550 to 1500 kilocycles.

Naturally a collision occurs whenever two or more stations are radiating energy into the same channel at the same time. If the stations are very powerful and are not given sufficient geographical separation, these collisions or heterodynes will be heard as a high-pitched singing note, especially where the receiver is located between the interfering stations.

Of the ninety-six channels, six are assigned exclusively to Canada, leaving ninety channels for the use of six hundred and twenty-four stations in the United States and Alaska, an average of nearly seven stations per channel.

Heretofore, no station has occupied a clear channel unless the other stations assigned to its wavelength were not broadcasting. For instance, due to the difference in time, some Pacific Coast stations could be heard without heterodyning only after their Eastern channel-sharers had shut down. But as a general rule no station was free from a heterodyne whistle during some period of its operation. What could the Commission do to remedy the trouble?

* * *

THERE were two answers to the problem of preventing collisions on the radio highways: one to reduce the number of stations which employ them, and the other to reduce the time that some of the stations operate, thus allowing two or more stations to use the same channel during different periods, much as a thrifty landlord used one set of beds to accommodate three shifts of miners in the early days of the gold rushes. The Radio Commission adopted the latter plan.

Forty channels were cleared, eight in each zone. One-fourth of these were assigned ex-

clusively for the use of single stations. On the other three-fourths, two or more stations are limited in time so that they do not operate simultaneously. Most of them are high-power stations. Consequently, during the night hours, there should be little or no interference on nearly one-half the dial. According to the Commission's original order the clear channels are Nos. 64 to 87 inclusive (excepting 78) and channels 97 to 119 inclusive (excepting 101 and 112). Subsequent allocations may slightly change these figures. This should revive interest in long distance reception on these channels.

Of the remaining fifty channels, four are assigned for simultaneous use in not less than two zones, thirty-five for not more than three zones, five for all zones for stations whose power does not exceed 1000 watts, and six for all zones for power not over 100 watts. The last two classifications cover 317 stations. Thus more than half the number of stations are accommodated on eleven channels and nearly a fourth of them are found on three local service channels, number 120 with 52, 121 with 45, and 131 with 51 stations.

These allocations, as well as this interpretation thereof, are somewhat tentative and many of them will be changed, if the number of protests is any criterion. But zone assignments of power and particular frequencies cannot be greatly altered because of the interdependence of the entire set-up.

* * *

ANOTHER revolutionary order which will be bitterly opposed by the stations, and as heartily approved by the majority of listeners, is that prohibiting the broadcasting of chain programs from more than one station for more than one hour a day where the chain stations are within three hundred miles of each other.

So the eleventh of November will probably mark the beginning of the end of much of the interference that the listener has endured for many months. But in the meantime active hostilities are in progress between station and station and between stations and the Commission. Many stations and communities are up in arms against what they consider unjust discrimination. Consequently, even if Armistice Day brings an armistice in this radio warfare, it will leave many hard feelings to be softened by subsequent peace negotiations.

The Short-Wave Trans-Atlantic Radiophone

By S. R. WINTERS


A REGULAR radiotelephone service on short waves between the United States and England is soon to be in effect. This is a departure in that two-way communication is to be attempted on short waves, instead of the long waves by means of which the service was introduced. The Bell Telephone Laboratories, Inc., recently erected buildings and installed short-wave receiving equipment at Netcong, New Jersey, and the British Postoffice has completed a short-wave transmitting station in Scotland.

The radiotelephone calls between this country and Great Britain now average 30 a day, and occasionally the number of international radio conversations may reach 60 within twenty-four hours. To accommodate this increasing traffic as well as to determine the suitability of short waves for regular, dependable long-distance communication, the duplex, two-way system has been constructed in the two respective countries. Until quite recently England had no short-wave transmitting station for communication with the United States. The new short-wave receiving station at Netcong, New Jersey, is a mate for the recently built English high-frequency transmitting station.

The use of a radiotelephone for dependable communication over a distance exceeding 3000 miles requires the application of three pairs of short wavelengths. The vagaries of short waves are such as to require different frequencies for effective operation at varying periods of the day and night. For

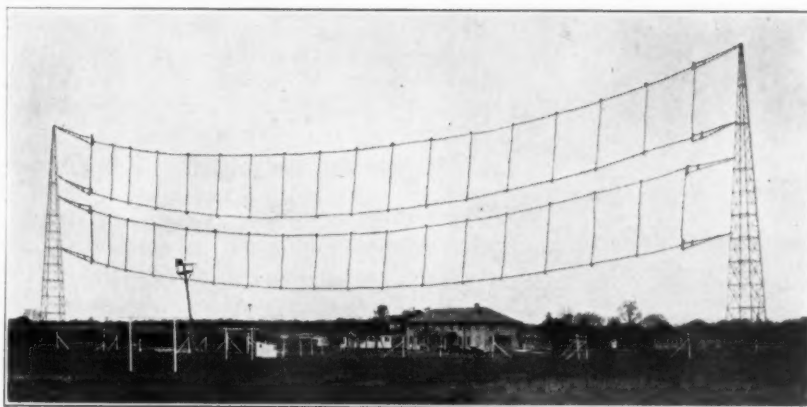example, in the two-way trans-Atlantic radiotelephone service one wavelength will be used during daylight hours, a different wavelength will be employed for night service, and still a third wave channel of a frequency at variance with the other two will be necessary for effective communication when a portion of the signal path is shrouded in dark-

sideband transmission and working both ways on one wavelength are not now practicable commercially on short waves, contend engineers of the Bell System. The voice-operated devices, however, are employed in connection with two slightly different wavelengths, one of which is used for eastbound speech and the other for westbound conversation.




Short-Wave Telephone Transmitting Station at Deal, N. J.

ness and the other part illuminated by daylight.

In this particular, the short-wave service differs essentially from that of long-wave trans-Atlantic radiotelephone communication. At present, in the use of long wavelengths, two-way operation is effected on a single wavelength by means of the single-sideband method of transmission and voice-operated relays. This arrangement permits of telephone currents traveling in but one direction on the circuit at any given moment. Single-

The short-wave transmitting station of the Bell Telephone Laboratories is located at Deal, New Jersey—occupying the grounds and housed in the building originally dedicated to the innovation of exchanging radiotelephone communications between shore and ship stations, about ten years ago. This is fitting that the same location should mark the inauguration of two such signal achievements in the art of radiotelephony. The ship-to-shore experiments were conducted from 1919 to 1922. Quite recently, a marine-service company in California inaugurated a regular radiotelephone service hourly between the Los Angeles harbor and a fleet of steamers and tugboats operating in the southern California waters.

The New Jersey short-wave transmitter for trans-Atlantic communication is subject to quartz-crystal control, a thin slab of this mineral—encased in a constant temperature cabinet—governs the transmitting frequency or wavelength with remarkable precision. The shifting from one wavelength to another in the variable frequency operating schedule is effected in less than ten minutes. This change in operating wavelengths merely requires the substitution of one slab of quartz crystal for another of different thickness and the insertion of different inductance units in the output circuits of the high-frequency amplifier. These changes in operating conditions are not only dictated by variations in day and night periods but by seasonal de-

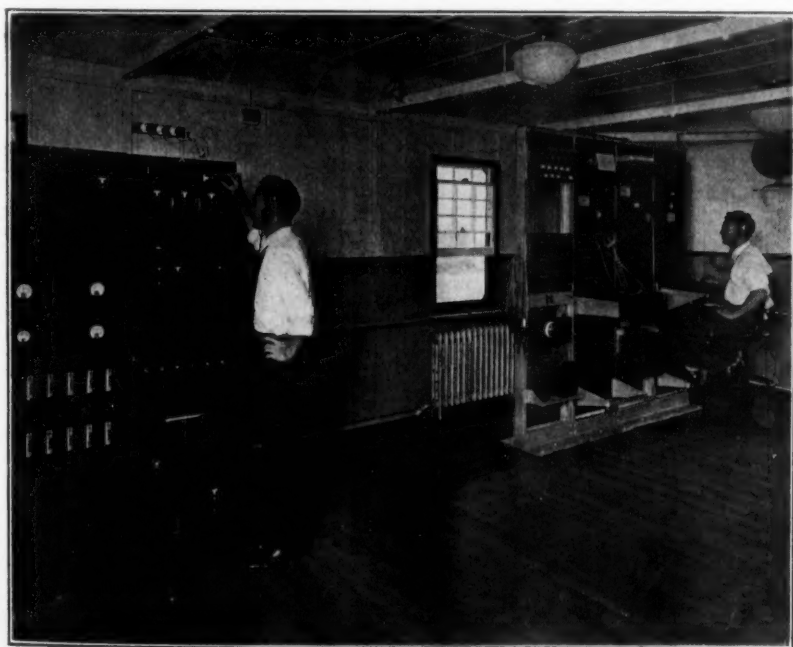

Short-Wave Receiving Station at Netcong, N. J.

mands—the change from summer to winter or vice versa, for example.

The short-wave receiving station at Netcong, New Jersey, is an absolutely new link in the radio and telephone communication chains of the Bell System—the buildings having been recently erected and the equipment newly installed. Both stations are linked by land wires with communication headquarters



Transmitting Equipment

of the Bell Telephone Laboratories at 24 Walker Street, New York City. At this point, the two one-way circuits converge and are thus transformed into a two-way circuit for connection through the long-distance switchboard to the lines of the Bell System.

This new undertaking of establishing two-way radio communication between America and England on short-waves



Speech-Input Monitoring Panel at Transmitting Station

should further contribute to our knowledge of a band of frequencies which radio amateurs discovered as having great intrinsic value. Already, the one-way trans-Atlantic communication has disclosed that static or atmospheric disturbances discriminate against long waves

SIMPLIFIED FORMULAS FOR REACTANCE

By ARTHUR HOBART

A DELIGHTFUL simplification can be made in radio's most fundamental equation, which says that the total reactance of a series circuit is equal to the difference between the inductive reactance and the capacitive reactance.

It is ordinarily expressed as $X = \omega L - 1/\omega C$, where X is the reactance in ohms, ω is $2\pi f$, f being the frequency in cycles per second, L is the inductance of the coil and C the capacity of the condenser. The circuit is resonant when $\omega L = 1/\omega C$, the reactance then being zero and the impedance to the flow of an alternating current being equal solely to the resistance of the circuit.

But the prodigious labor involved in calculating a resonance curve with this formula may be greatly lessened by simplifying it to meet the conditions found in practice. As the circuit conditions are constant when it has been tuned to resonance for a given frequency, the only variable is the non-resonant frequency, for which the impedance is to be found.

Thus it is common practice to use a 170 microhenry coil with a .0005 microfarad condenser to cover the broadcast band from 550 to 1500 kilocycles. A frequent problem is to determine the proportionate interference that may be caused by a carrier wave in a channel close to that to which the circuit is tuned. The reactance to the tuned frequency is zero and that to the interfering frequency is approximately $X = 4\pi Ld$ when d is the difference in megacycles between the two frequencies and L is expressed in microhenries.

The value of this approximation can best be illustrated by a typical problem. Assume that a circuit consisting of a 170 microhenry coil and a .0005 mfd. condenser is tuned to 1000 k.c., i.e. $X = 0$ at 1000 k.c. What is its reactance to 990 k.c.?

By the standard formula it is first necessary to find the LC value of the circuit, either from a published table or from the formula $LC = 1/(2\pi f)^2$, which in this case is .02532. From this find C as $.02532 \div 170 = .000149$ mfd. Then $X = 6.28 \times .990 \times 170 - 1 \div$

in favor of short waves for such long-distance service. Short waves, it has also been found, do not travel so nearly in a bee-line to their destination as do the long wavelengths. The exact path of short waves, however, remains to be defined and charted. Our knowledge of the skip effect and the fading of signals when employing short waves should be contributed to measurably by this regular radio service for spanning the Atlantic Ocean.

$$(6.28 \times .990 \times .000149) = 1057.4 - 1079.0 = 21.6 \text{ ohms.}$$

By the approximate formula $X = 4\pi \times 170 \times .01 = 21.4$ ohms, and how much easier it is to check the correctness of your work!

For a 5-ohm circuit tuned to 1000 k.c., the impedance is 5 ohms to 1000 k.c., and $\sqrt{5^2 + 21.4^2} = 22$ ohms to 990 k.c., or 4.4 times greater. So, for equal signal input, the 1000 k.c. signal is 4.4 stronger than the 990 k.c. signal at the circuit output, or the 990 k.c. signal is less than one-fourth as strong as the 1000 k.c. signal.

The method whereby this approximation, and also a very simple exact equation for reactance, may be derived is an interesting exercise. At the resonant frequency f_R , the inductive reactance is equal to the capacitive reactance, — $2\pi f_R L = 1/2\pi f_R C$, whence $LC = 1/(2\pi f_R)^2$ and $2\pi L = 1/(2\pi f_R^2 C)$. At any frequency f , $X = 2\pi f L - 1/2\pi f C =$

$$\frac{(2\pi f)^2 LC - 1}{2\pi f C} = \frac{(2\pi f)^2}{(2\pi f_R)^2} - 1 \frac{1}{2\pi f C}$$

$$= \frac{f^2 - f_R^2}{2\pi f_R^2 C f} = \frac{2\pi L(f^2 - f_R^2)}{f}$$

$$\text{Let } f = f_R \pm d, \quad f^2 = f_R^2 \pm 2f_R d + d^2, \quad f^2 - f_R^2 = \pm 2f_R d + d^2 = d(\pm 2f_R + d)$$

$$\text{So } X = 2\pi L d (\pm 2f_R + d) \text{ and if } d/f_R \text{ is small, } X = 4\pi L d.$$

As an example of the use of the exact formula, consider a circuit tuned to 1500 k.c., using a 170 microhenry coil. What is the reactance to 1510 and 1490 k.c.?

$$2\pi L = 6.2832 \times 170 = 1068.124, \quad d = \pm .01, \quad f_R = 1.5.$$

$$X = 1068.124 \times .01 \frac{(\pm 3 + .01)}{1.5 \pm .01}$$

$$= 10.68 \times 1.993 \text{ or } -10.68 \times 2.0066$$

So the reactance to 1510 k.c. is 21.28 ohms and to 1490 k.c. is 21.43 ohms. By the approximate method, $X = 21.4$ ohms for either case. The magnitude of the error introduced by this approximation is about $\pm d/2f_R$, which is negligible in most practical cases.

An equation of almost equal simplicity can be developed for a parallel or non-resonant circuit. Assuming that the losses due to resistance are small, and consequently neglecting R , the reactance X of a parallel circuit is $\omega L/(1 - \omega^2 LC)$. Adopting the same method and notation as in the case of series reactance, this can be successively reduced to

$$\frac{-2\pi L f_R^2}{d} \frac{1 \pm d/f_R}{(\pm 2 + d/f_R)} \text{ or}$$

$$\text{approximately } X = \frac{\mp \pi L f_R^2}{d}$$

This method is much simpler and easier than the usual method of finding susceptances and reactances and is just as accurate.

What Is an Underground Antenna?

By G. M. BEST

EACH radio season sees the advent of a crop of devices commonly advertised under the name of "underground antennas." To read the claims for such devices, as set forth in their published advertising and mail circulars, creates an expectation that they will give absolute freedom from static, power line interference, and other annoying noises usually present when a conventional type of antenna is used, and at the same time with no sacrifice of distance, selectivity or other impairment of operation of the receiving set.

As this seemed too good to be true, an investigation of the various devices of this type was made, with a view to determining their merits, if any, and also to obtain an accurate definition of an underground antenna as conceived by its inventors.

The principal patents covering underground antennas were granted to James Harris Rogers of Hyattsville, Md., in 1919 and 1920, and we understand that these patents have been sold by Mr. Rogers to other interests. A study of the patent papers discloses some very interesting data, and in Fig. 1, a re-

grounded. Many variations of this method are covered by the patents, including such an arrangement as is shown in Fig. 2, in which equal lengths of buried, shielded wire are placed on each side of the coupling inductance, and no ground connection whatsoever is used.

his opinion they are not comparable in efficiency with the elevated antenna or the underground antenna when buried substantially parallel with the surface of the earth.

Again thanking you for your esteemed letter, I beg to remain,

Very truly yours,
(Signed) JAS. C. ROGERS.

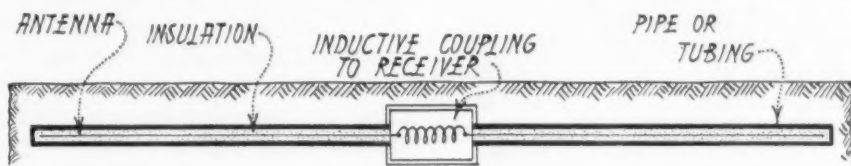


Fig. 2. Underground Antenna of Equal Sections

Other variations place the shielded cable on top of the ground but in contact therewith; place the cable on supports so that it is elevated a few inches above the earth; and several of the arrangements include grounding of the far end of the buried cable instead of insulating it as is done in Figs. 1 and 2.

Dr. Rogers developed his various underground systems before and during the World War, his first application for patents being made on May 2, 1917, and to him should go the credit for the

Having thus received confirmation of our opinion from the man best informed on the subject, a further investigation was made as to the nature of the various devices being sold, and the results obtained with them when used with an average broadcast receiver.

Practically all of them consist of a metal container, usually sealed and made of brass or copper, to which is connected a length of lead-in wire. In one or two specimens, the container was filled with a mixture of charcoal and common salt, the assumption apparently being that after the device had been buried for some time, the moisture in the soil would penetrate the container and make a better contact between the lead-in and ground. Some of the patent grounds which do not claim to be underground antennas have various combinations of chemicals, chiefly copper sulphate, which when combined with moist soil is supposed to provide an exceptionally good ground. This phase of ground connections is covered in detail in an article by Heckert Parker in August, 1928 RADIO.

All of these devices have ordinary rubber and cotton covered lead-in wire, and the accompanying instructions direct the buyer to install it directly outside the wall of the house, under the window through which the lead-in wire is to be brought. From our own experience, when used with a broadcast receiver having an average degree of sensitivity, the results were so poor as to make the set useless except for local stations.

Experiments with a real Rogers antenna, similar to Fig. 1, using a sensitive superheterodyne, showed that a range of 500 miles at night, in the winter, might be expected, with loud speaker volume, from stations having a power of at least 1000 watts. The static level was very much lower than when using an elevated antenna, 40 ft. above the ground, and 80 ft. long. Although the

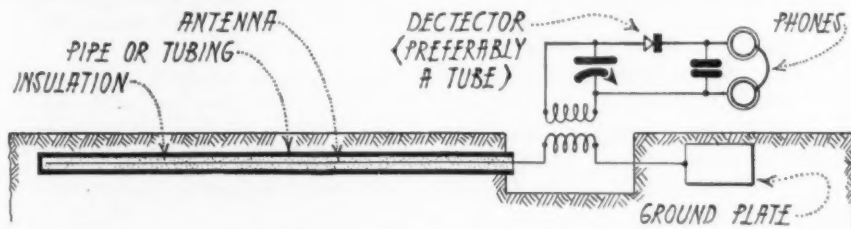


Fig. 1. Rogers Underground Antenna

production of one of the many types of antenna systems covered by Mr. Roger's patents is shown, as a typical example.

The principal claim covering this type of antenna defines the antenna as "A radio signaling system comprising an antenna extending horizontally substantially parallel to the surface of the earth and insulated therefrom, a metallic covering inclosing said antenna but insulated therefrom and in intimate contact with the earth substantially throughout its length, signal instruments associated with said antenna, and a balancing connection on the opposite side of said instruments."

Referring to Fig. 1 it is obvious that the underground antenna consists of an indeterminate length of insulated wire enclosed in a metal sheath such as a lead cable, buried sufficiently so that the sheath is in good electrical contact with the earth, and parallel to its surface, the lead-in being brought to one side of the coupling inductance of the receiver, the opposite end of which is

remarkable work which he did at a time when radio was in its infancy and the apparatus with which he had to work was necessarily of crude form. Being interested in knowing just what Mr. Rogers thought of the various so-called underground antennas being sold to the general public, a letter was addressed him on the subject, and the reply thereto is reproduced below:

ROGERS RADIO RESEARCH LABORATORY
Hyattsville, Maryland
August 22, 1928.

Editor, RADIO

Sir: My brother Dr. J. Harris Rogers, who is unwell, begs me to acknowledge receipt of your kind letter of August 10, and to thank you for the credit you propose to give him for his pioneer work in underground and underwater radio, in your valuable publication.

His attention has been called to various publications and advertisements of devices utilizing the underground principle and making exaggerated claims, for which he is in no way responsible, and which are misleading and unwarranted, and likewise unjust to himself and to the public.

Referring to the class of devices referred to in your letter, he is frank to say that in

volume on distant stations was much less with the underground antenna, a well-defined reduction of static to signal ratio was noted, and except for stations at distances of over 500 miles, the Rogers antenna was preferable.

However, when using the underground antenna with a 7-tube tuned r.f. set of well-known make, the results were much poorer than those obtained with the superheterodyne, due of course, to the lower degree of sensitivity in the tuned r.f. set. Stations 500 miles away which came in with good volume with the elevated antenna, could not be heard with the underground antenna, and this performance was made with the underground antenna arranged in such a manner as to receive the signals of the distant station to the best advantage. On local stations, however, the performance of the set was very satisfactory, and while the static level on the elevated antenna was so far down as to be barely noticeable, a difference could be detected when the underground antenna was used.

So much for the conventional buried wire in metal conduit. Several of the buried container antennas were then connected to the superheterodyne, and the results compared with those obtained with the Rogers system. Distant stations could not be heard, and only those locals which were within 6 or 7 miles of the receiver could be picked up with sufficient volume to give a satisfactory performance. In fact, with the superheterodyne, better results were obtained when a good water-pipe ground connection was used, with no antenna, than with the buried antenna. Hence, the conclusion was reached that if the lead-in from the buried antenna was cut off close to the ground, and only the lead-in used, better results would be had, and this proved to be the case. How much better it would be, then, for one to dig a small trench, say six inches deep, out through the back yard for a distance of fifty feet or more, and bury therein a length of lead covered wire, rather than to spend more money, and install what actually is nothing but a high resistance ground, with a small effective capacity thrown in.

It is necessary to give the devil his due, however, for one device proved to be quite satisfactory with sets such as the superheterodyne, and was the nearest to being an underground antenna of any of them. This device consisted of a sealed metal container, in which was coiled a roll of lead covered wire perhaps 60 ft. long. The wire passed through a hole in the container, and a 15 ft. piece was provided for the lead-in. Directions for installation called for burying the device in a vertical position, directly under the window through which the lead-in would pass, and did not call for any section of buried wire like the Rogers system.

The station log obtained with this antenna, using a superheterodyne, proved that a considerable amount of energy was being collected by the antenna, and that as compared with an elevated antenna, it was preferable except for the reception of extreme distance, in which case the elevated antenna was by far the best of the two. But the strangest part of the whole thing was that when the coil of wire was removed from the can, and laid out flat on the ground, the results were much better than when the coil was wound up and sealed within the buried container. "Why not eliminate the metal container then, dig a trench for the cable the same as for the Rogers system, and do a real job of it?" you might ask, but this would never do, for who would dare ask ten bucks for 75 ft. of lead covered wire? A copper-plated can filled with mystery looks ever so much more worth while to the average uninformed radio fan. Of course, digging the trench is a lot of bother, and conditions may be such that there is no room for a real Rogers antenna, which is the best argument the patent ground makers can bring forth.

A fair idea of how much money must be made on such devices can be gained by the writer's experience in answering a number of advertisements concerning them, for where the first quotation was list price, as advertised, subsequent follow-up letters gradually brought the price down until in one case the reduction amounted to nearly 70 per cent. It would be foolish to assume that they were not making a profit even at 70 per cent discount, so the reader can draw his own conclusions.

The moral of all this is that if you are satisfied with local reception, a short elevated antenna will give you the results you want with practically no static, except in the summer months, and unless the elevated antenna is impractical due to the location, the expense of a factory made underground antenna is not warranted. If you expect to receive distant stations, however, do not be disappointed if you meet with failure, for while you may find the static level very much lower than before, you will probably find the signal level has gone down in much the same proportion. So if you buy one, patronize the firm with the money-back guarantee and here's hoping you get your money back.

NEW SYSTEM FOR DETERMINING SHIP'S POSITION

A radio acoustic system for determining the position of a survey ship when it is beyond the visibility of shore objects has been developed by the U. S. Coast and Geodetic Survey. As described in the Survey's special publication No. 146, it consists essentially of a radio transmitter at each of two widely separated shore stations and a radio receiver on the ship.

Each transmitter automatically radiates a characteristic signal whenever a submerged microphone is disturbed by the explosion of a bomb close to the ship. This disturbance or noise is also instantaneously transmitted by a submerged microphone at the ship. At varying periods of time, depending upon the distance from the two shore stations, their radio signals are also received. As the speed of sound in water is definitely known, as are also the station locations, the ship's position may be quickly plotted on the survey map.

When the position of the ship is wanted, a small bomb is fired in the water alongside. The instant of the explosion is automatically recorded on a chronograph aboard the ship. The sound of the explosion disturbs the submerged microphones at the shore stations and their resulting characteristic radio signals are received and recorded on the ship's chronograph. The ship thus obtains the time of travel of sound in sea-water from her position to each of the known positions of the shore station microphones, and therefrom is figured the distances. This method has successfully been used with a ship 75 miles away from the shore stations.

RADIO SIGNAL TRANSMISSIONS OF STANDARD FREQUENCY, OCTOBER TO MARCH

The Bureau of Standards announces a new schedule of radio signals of standard frequencies, for use by the public in calibrating frequency standards and transmitting and receiving apparatus. This schedule includes many of the border frequencies between services as set forth in the allocation of the International Radio Convention of Washington which goes into effect January 1, 1929. The signals are transmitted from the Bureau's station WWV, Washington, D. C. They can be heard and utilized by stations equipped for continuous-wave reception at distances up to about 500 to 1000 miles from the transmitting station.

The transmissions are by continuous-wave radiotelegraphy. The signals have a slight modulation of high pitch which aids in their identification.

Information on how to receive and utilize the signals is given in Bureau of Standards Letter Circular No. 171, which may be obtained by applying to the Bureau of Standards, Washington, D. C. Even though only a few frequency points are received, persons can obtain as complete a frequency meter calibration as desired by the method of generator harmonics, information on which is given in the letter circular. The schedule of standard frequency signals is as follows:

RADIO SIGNAL TRANSMISSIONS OF STANDARD FREQUENCY Schedule of Frequencies in Kilocycles

Eastern Standard Time	Oct. 22	Nov. 20	Dec. 20	Jan. 21	Feb. 20	Mar. 20
10:00—10:08 P. M.	550	1500	4000	125	550	1500
10:12—10:20	600	1700	4200	150	600	1700
10:24—10:32	650	2250	4400	200	650	2250
10:36—10:44	800	2750	4700	250	800	2750
10:48—10:56	1000	2850	5000	300	1000	2850
11:00—11:08	1200	3200	5500	375	1200	3200
11:12—11:20	1400	3500	5700	450	1400	3500
11:24—11:32	1500	4000	6000	550	1500	4000

Electric Phonograph Pick-up Units

A Description of Their Methods of Operation and Suggestions for Improvement of Tone Quality

By FRANCIS CHURCHILL

WHILE many different phonograph pick-up units are available, but little information is given as to their proper use. An electric pick-up unit usually consists of a permanent magnet, a field coil and a moving armature. The armature is actuated either directly or through a link coupling, by the phonograph needle. The magnetic type is the most popular and seems to have the best frequency characteristic.

The frequency at which the needle moves across the groove of the record determines the pitch of the sound produced. The needle moves an armature, which in turn generates a voltage in the field coil, since it is cutting lines of force produced by the permanent magnet. This voltage is then applied to an audio frequency amplifier and loud speaker and is reproduced as sound.

As the design of the pick-up unit cannot be easily changed by the experimenter, the output frequency characteristics are not variable for a particular unit. That unit may not be very good on the low frequencies, or perhaps on the high frequencies, but by proper use it may be made to give satisfaction.

so that the pick-up unit works into, in effect, an infinite impedance, then a more uniform voltage output would be obtained for all frequencies. However, in such a case the primary of the first audio transformer would be across a variable impedance, depending upon the volume control setting, and so would not amplify uniformly.

Considering only the first transformer in the usual two-stage audio amplifier, the impedance across its primary should not be over 10,000 to 20,000 ohms. With impedances higher than this the low frequencies are lost, as also are generally the high frequencies. This means a peaked amplifier and poor tone quality. This is likely to happen at certain volume control settings if the resistance happens to be greater than 50,000 ohms. With this same arrangement at very low volume settings or at the highest settings, the primary of the audio transformer will be connected across a low impedance, which will improve the low frequency response and also the high end. This is undesirable, since changing the volume causes a change in quality.

A good way to get around this trouble is to connect the volume control as an ordinary variable resistance in shunt to the pick-up unit. With such a connection,

the maximum impedance across the transformer will be somewhat less than that of the pick-up unit, which means a fairly low impedance at any volume control setting. This is desirable because the characteristic of the first audio transformer stays the same, as does the complete amplifier.

Let's see what happens when such a low impedance is connected across the amplifier. Curve A in Fig. 3 is that of a popular type of audio transformer when connected across a detector tube having about 20,000 ohms plate impedance. Curve B shows the same transformer with a pick-up unit across it. Due to the lower impedance, the low frequency response is much better and the transformer is nearly perfect on the lower end. However, the upper end has an enormous peak. Tests on a number of makes of transformers showed the same effect with the peak ranging from 4,000 to 7,000 cycles. Such a peak would cause over-amplification of the higher frequencies and needle scratch.

All audio transformers have a certain amount of leakage reactance and the secondaries have distributed capacity and capacity to ground, as well as the input capacity of the vacuum tube across it. All of these capacities resonate with the leakage reactance in such a way as to

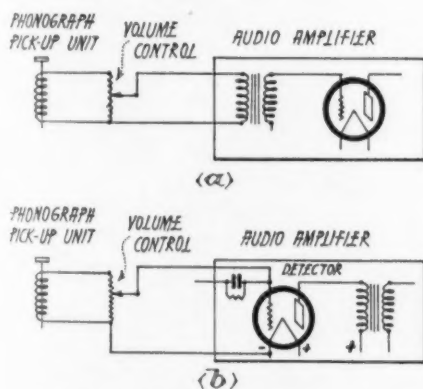


Fig. 1. Usual Methods of Connecting Pick-up Unit

Fig. 1 (a) and (b) show the usual methods of connecting a unit into the audio amplifier of a radio set. The ordinary pick-up unit has an impedance of about 1000 ohms at the low frequencies and may rise as high as 20,000 ohms at 5000 cycles, as shown in Fig. 2, whose curves were made with a standard impedance bridge and are typical.

When such a unit is connected as shown in Fig. 1 (a), the high frequencies may be lost if the volume control is of too low a value, since the load would then be equal to the pick-up or generator impedance at the lower frequencies. If the resistance is made high enough

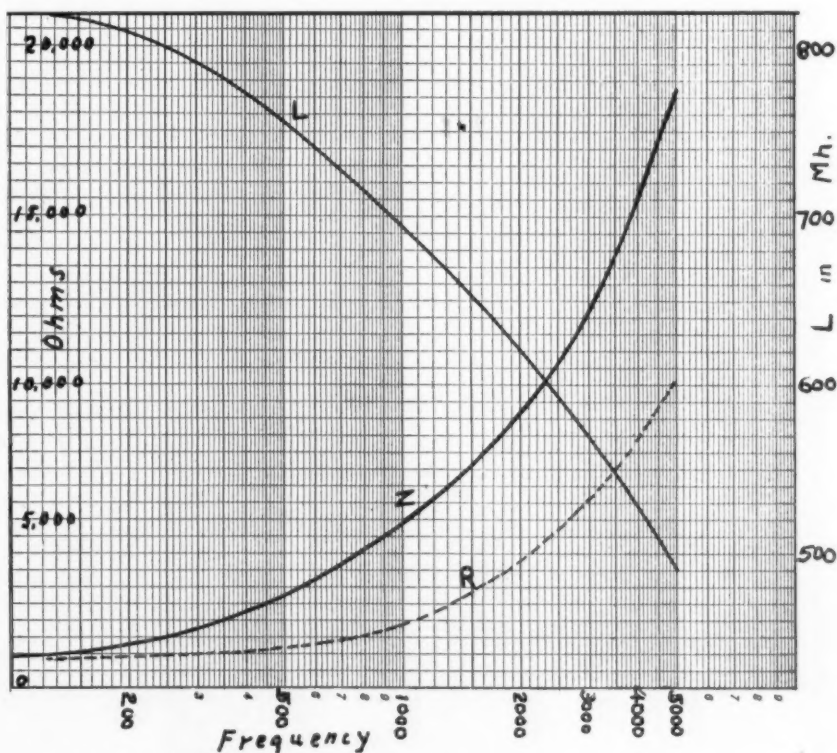


Fig. 2. Resistance, Inductance and Impedance Curves of Typical Pick-up Unit

cause a peak in the high frequency range. This leakage reactance can be increased by adding an external inductance in the primary circuit, which is exactly what we have done when connecting the pick-up unit across the primary. Naturally the lower the resistance in series with this resonant circuit effect, the higher will be the resultant peak. The pick-up unit has a fairly low resistance and so the curve B of Fig. 3 is obtained. There are two ways of overcoming this peak but first let us see whether it is desirable to eliminate it.

If the rest of the audio amplifier is not peaked on the high frequencies, such a peak in the first transformer can be put to good use. When the volume control resistance has a maximum value of say 10,000 ohms, the pick-up unit will not give a good high frequency response and the lower this value of resistance the poorer the response. Then the peak in the amplifier practically offsets the droop in output of the pick-up unit and so an excellent sound output is obtained over the whole range of frequencies.

Suppose that the amplifier has too high a peak or that the pick-up unit has naturally a greater output at high frequencies, then it would be desirable to eliminate this peak. This can be easily done in two ways; by inserting a 10,000 or 20,000 ohm resistance directly in series with the transformer primary, or by inserting a higher resistance in the grid return of the secondary.

The first scheme has the objection of causing a drop in the low frequencies as well as the highs, since the curve A will generally be obtained, but it has the ad-

vantage of being very simple to install, since it can be external to the radio receiver. The middle frequencies are not diminished, since even 20,000 ohms is only a very small portion of the transformer primary impedance at these middle frequencies.

The second scheme has the advantage of not affecting the low frequencies but does drop the higher ones. It has the disadvantage of having to be inserted in the audio amplifier and should not be used with a detector tube input, since the high frequencies would be practically lost.

Fig. 4 (a) and 4 (b) show the connections for these two schemes. In the latter,

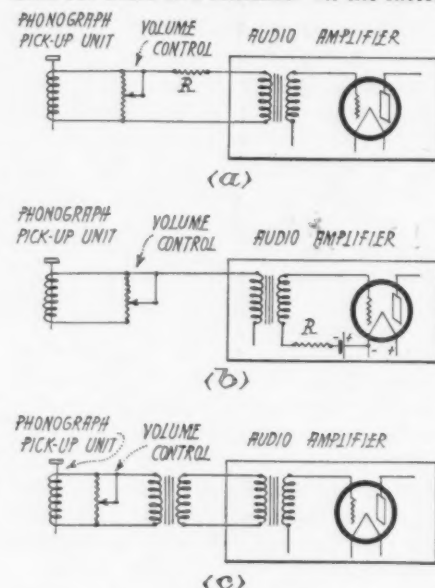


Fig. 4. Suggested Connections for Pick-up Unit. (In 4b the volume control resistance should be connected to ground.)

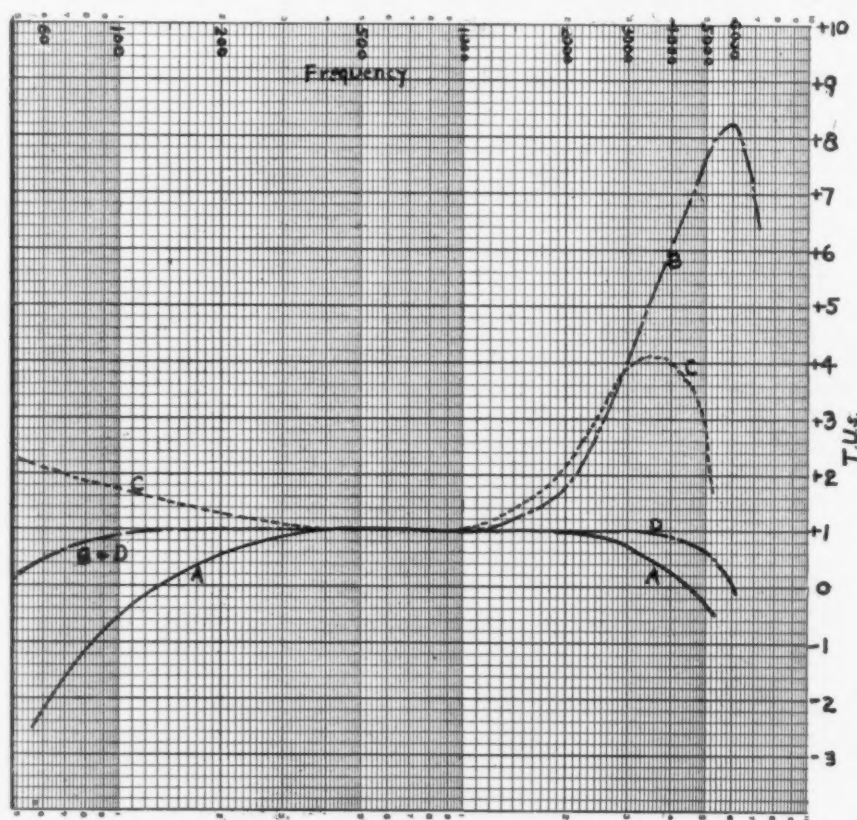


Fig. 3. Effect of Different Impedances on Audio Frequencies

the resistance R will vary between 50,000 ohms and 250,000 for different types of pick-up units and audio transformers. Its action is as follows: There is a capacity between the two windings of the transformer which is charged by the secondary induced voltage. The charging current flows to ground through this resistance R , causing an emf opposite to that of the secondary induced emf in its effect on the grid of the tube. Thus one voltage counteracts the other and so the hump on the high frequencies is reduced. At lower frequencies the charging current is less, due to the higher reactance and so the very low frequencies are unaffected.

Often the pick-up unit does not deliver enough voltage to properly operate the audio amplifier and loud speaker. When this occurs an intermediate impedance matching transformer may be used as shown in Fig. 4 (c) or the unit may be connected across the grid of the detector tube.

Curve C, Fig. 3 was obtained when such a transformer was used in conjunction with the first audio transformer. The rising low frequency response was obtained evidently from the effect of impedance matching at the very low frequencies, with a corresponding drop for all higher frequencies. Curve C does not show the voltage gain when using this step-up transformer but merely shows the frequency response with 1000 cycles per second as a reference.

Fig. 1b shows the method of connecting the pick-up unit and volume control into the grid of a detector tube. This can be most conveniently done by means of a flat adapter which will slip over the grid and negative filament prongs or cathode of an a.c. tube, after which the detector tube can be inserted in its socket. The volume control should be connected to ground and should be at least 50,000 ohms. A 500,000 ohm potentiometer would be more suitable and a more uniform frequency response would be obtained.

As stated before, the low frequency response with this last arrangement will not be as good as when the unit is connected directly across the audio transformer, but more gain will be obtained since the detector tube is used as an amplifier. There will be no high frequency peak, at least no more than when used for radio reception, but the pick-up unit will give more output at the high frequencies. Scratch filters may be used if the needle scratch is objectionable, though if the pick-up unit is used properly, such a filter is unnecessary.

Phonograph records are cut laterally. To prevent the cuts from cutting through to the next groove, the very low notes are undercut or in effect, attenuated. With a good dynamic speaker mounted in a large cabinet or baffleboard, the audio amplifier may be made to have a

(Continued on Page 47)

Radio Picture Transmission and Reception

Photoelectric Equipment and Methods for Visual Communication

By JOHN P. ARNOLD, *Departmental Editor*

SOME of the future possibilities of the electrical transmission of photographs were strikingly demonstrated when signals, emanating from radiophone apparatus installed in the cabin of an airplane, flying a mile above the city of Philadelphia on the afternoon of August 14, were picked up by Station WFI in that city and rebroadcast for radio listeners who were equipped with picture receiving apparatus.

Due to the vibration of a wind-driven generator which supplied the power for the radio transmitter, the results were not highly satisfactory as far as the quality of the received pictures was concerned. But the demonstration itself, probably the first in the history of photo-telegraphy, marked an epoch in the application of still picture transmission to modern problems such as the dissemination of military information to numerous points along a battle front, the location of forest fires by aerial patrols, and the transmission of photographs of impor-

tant events while an airplane is in flight. mum input of 75 watts, was mounted in the cockpit. A 65-ft. "fish line" antenna was used.

The flight over the central section of the city required more than an hour.



Reproduction of Received Radio Picture of Colonel Lindbergh

Half an hour was needed for the plane to gain the high altitude necessary to throttle down the engine so that it would not interfere with radio transmission. Photographs of Col. Lindbergh and Graham MacNamee, which had previously been converted to a "sound record" on a phonograph disc in accordance with the usual method employed in the Cooley system, were transmitted. Although this demonstration did not include the actual photographic operations of taking, developing and preparing the pictures for transmission aboard the plane, there would be no difficulties in carrying out these steps on an airplane especially equipped for this work.

The airplane was piloted by Robert P. Hewitt, assisted by John Busher, and the broadcasting apparatus was operated by John J. Leitch, Federal Radio Inspector of the Third District.

The picture signals were received on a short-wave receiving set on the roof of Station WFI and rebroadcast on that station's regular wavelength.

Essentially the system of transmission consists in converting the light and shade of a photograph into audio-frequency impulses which are received on a conventional radio receiver and converted to light impulses by a three-tube amplifier-oscillator circuit. This apparatus con-

verts the audio-frequencies, which would ordinarily be fed into a loudspeaker in speech reception, into ultra-violet light variations radiated from a needle-point stylus. The light impressions are recorded on sensitive photographic paper, producing a positive reproduction of the transmitted pictures. It requires but three minutes to make a 4 x 5 picture consisting of 100,000 image impressions.

A REVOLUTIONARY LIGHT-SENSITIVE CELL

READERS of these columns have already been introduced to the well-known types of photoelectric cells; that is, those which employ the alkali metals or selenium as the light-sensitive material. Still another type is the photovoltaic cell which is an important development in photoelectric cell construction. It is quite likely that the recent perfection of this cell will solve some very troublesome problems in the field of visual communication and in the improvement of various sound recording and reproducing devices for which light-sensitive cells are commonly employed.

To go back a bit to the early period of photoelectric history. In 1873 Willoughby Smith observed a phenomenon which is now designated as the *photo-resistive* effect. In this case the substance changes (usually lowers) its electrical resistance when light falls upon its surface. The effect is observable in selenium, molybdenite, the metallic sulphides, oxides and various other crystalline forms. Selenium cells were the first to be used for practical engineering work; but their response is very slow.

The so-called true *photoelectric* effect, first noted by Hertz in 1887 and later more fully investigated by Hallwachs, refers to the emission of electrons from a metal or compound when illuminated. Stated in other words, a photoelectric body loses a negative charge due to the action of light. Potassium or the other alkali metals are usually employed for the construction of such cells.

The photovoltaic effect is a case where an electromotive force is generated between two metals in an electrolyte as the result of the action of light on one of the metals. The discovery of this effect extends back many years, probably before either the photo-resistive or photoelectric phenomena were observed. In any event, in 1878, Sabine designed the first practical photovoltaic cell, employing selenium deposited on an aluminum



Picture Transmitting Equipment in Plane

tant events while an airplane is in flight.

The experiment was undertaken jointly by the Philadelphia airport, Ludington Philadelphia Flying Service, Inc., Station WFI of the Strawbridge & Clothier Store and the Radiovision Corp. of New York. A Cooley "rayfoto" transmitter was installed in the cabin of a Fairchild monoplane. The short-wave radiotelephone equipment, having a maxi-

plate for this purpose. Cells of this type consist of two electrodes immersed in a liquid or electrolyte and, in operation, do not require the use of an external battery as is necessary in using selenium or potassium cells.

Although this particular effect was discovered many years ago and although various combinations of electrodes and



Photovoltaic Cell. (Radiovision Corp.)

electrolytes have been tried, satisfactory results were rarely achieved. It would be tedious to describe the reasons why the development of this type of cell was neglected all of these years; it will suffice to mention that the general belief is that fatigue precludes any successful results with them. As we learn more about the matter of fatigue, in regard to the photoelectric cell, it is conceded that the emission of electrons is an intrinsic property of the light-sensitive material, and that strong fatigue characteristics are often due to secondary causes which improved design is constantly eliminating.

Although it is too early to say that this is also true in the case of photovoltaic cells, nevertheless, careful laboratory tests, which would detect a delay in response of the order of hundredths of a

second, have failed to reveal any fatigue. Moreover, there are additional reasons for believing that these cells may be used for practically all applications which require a high frequency of response. The credit for the perfection of the photovoltaic cell is due to Samuel Wein, of the Radiovision Corporation, New York, who has also made other valuable contributions to the science of photoelectricity.

The construction of this cell may be studied by referring to the accompanying picture. Two metallic plates, rigidly supported and separated about $\frac{1}{2}$ in. from each other, are immersed in an electrolyte contained in a cylindrical glass bulb, $1\frac{1}{2}$ in. in diameter and about $4\frac{1}{2}$ in. long. The cell is fitted with a radio base and the electrodes are connected by wires to the prongs which correspond to the plate and grid of a radio tube.

By connecting a very sensitive meter in series with the electrodes, a large deflection will be noticed when one of the plates is illuminated. In direct sunlight, the writer has obtained deflections of $\frac{1}{2}$ milliamperes when the cell is exposed. When an opaque screen is interposed between the cell and light, the pointer of the meter immediately falls to zero. While such relatively small deflections may seem insignificant to the lay reader, it is enough to make the informed experimenter sit up and take notice, since such results are unusual in this type of cell.

This cell may be temporarily sensitized in the following manner. When the terminals of the cell are connected to a 45-volt battery for about 10 seconds, the battery then removed and a meter substituted, deflections of several milliamperes—in fact, three or four times the value before sensitizing—have been observed. The effect of this charging gradually diminishes and disappears in about an hour, but the charge can be renewed as often as desired. The makers of the cell are planning to insert an auxiliary electrode between the two metal plates, serving a purpose similar to that of the grid in a radio tube, by means of which a constant charge may be maintained indefinitely. However, it is not necessary for the cell to be charged, since its output is sufficient to operate sensitive relays directly.

Further characteristics of these cells may be gathered from the curves illustrating this article, and from the following facts which were taken from laboratory tests:

Current Output: In very feeble light the cells furnish a current of the order of 10^{-6} amperes.

Internal Resistance: The internal resistance of five cells measured at 1000 cycles in the conventional manner ranged from 15 to 52 ohms, with an average of 32 ohms.

Photovoltaic Potential: The voltage illumination curves (Fig. 1) indicate that the potentials are proportional to the incident illumination; the apparent deviations from this generalization are doubtless due mainly to the difficulty of measuring closely the distance of the illuminated plate from the source at

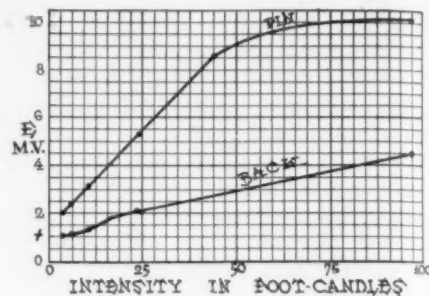


Fig. 1. Voltage-Illumination Curves for Photovoltaic Cell Whose Plates Are Designated as "Pin" and "Back"

high light values. At low intensities, between 10 and 20-foot candles, there is apparently a critical phenomenon, for nearly every plate exhibits a peculiar reaction as evidenced by change of curvature in the characteristic curve.

Spectral Sensitivity: A measure of the sensitivity of this type of cell to different spectral colors (Fig. 2) was obtained by means of Wratten light filters. The light source was a tungsten filament lamp with a concentrated filament supplied

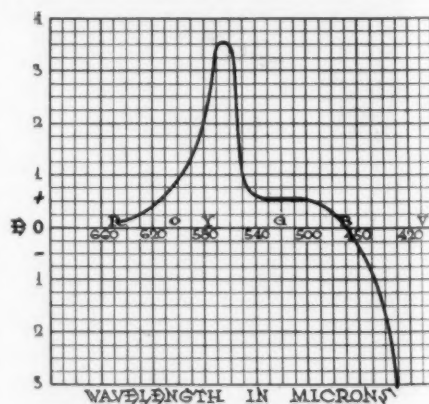


Fig. 2. Wavelength Sensitivity Curve

by a storage battery. The curve shown is purely qualitative as is any obtained by filters which pass a relatively wide band of frequencies. The cell shows a rather marked selective effect in the yellow. This rapidly decreases in the green and changes sign (positive to negative) in the blue. In the blue-violet the potential has reached an appreciable value of the opposite sign. The various spectral colors, red, orange, yellow, green, blue and violet are denoted by R, O, etc., in Fig. 2.

As has been previously noted the new photovoltaic cell may be employed for all the ordinary applications for which the other types of light-sensitive cells are used, with the additional advantage of not requiring external batteries.

A PHOTOELECTRIC AMPLIFIER

THE practical employment of photoelectric cells involves as a rule the amplification of the extremely minute photoelectric current. To accomplish this purpose the cell is connected to the input of a vacuum tube amplifier.

For delicate measuring work or for amplifiers designed for "still" picture transmission or television, steady sources of potential are required; the usual *A*, *B*, and *C* batteries and, in addition, a fourth or *D* battery, as it is sometimes called, may be used to charge the photoelectric cell. The use of a power tube in conjunction with the cell requires batteries of several hundred volts, depending on the types of cell and tube.

Where photoelectric cells are used to control power circuits through a relay or for other similar purposes, variations in the supply source are not particularly harmful and it is possible therefore to design amplifiers which have the advantages of greater convenience and lower cost. Circuits have been devised to operate directly from a.c. or d.c. power circuits, although these are not as satisfactory as the "eliminator" described here.

The circuits differ merely in the placing of the photoelectric cell and were described in a paper by Fox, Rood and Marburger in the *Journal of the Optical Society of America* for December, 1927. The specific purpose for which this apparatus was designed was to control a laboratory clock by photoelectric signals; but the amplifier itself is suitable for many other useful applications of photoelectric cells.

The circuit diagrams require no particular explanation since they are not unusual in any way. It is necessary, however, to mention that the photoelectric cell should be inclosed in a light-tight box, preferably fitted with an iris diaphragm to control the beam of light

The parts which are suggested for the construction of this power amplifier are the following.

- 1 Photoelectric cell, gas or vacuum type.
- 1 UX-210 Power Tube.
- 1 Type 365 General Radio transformer.
- 1 Raytheon BH tube.
- 1 Mershon 30 MF electrolytic condenser.
- 1250 ohm Ghegan relay.
- 2 Daven grid leaks, 7 meg and 0.1 meg.
- 1 Bradleystat.

which falls within. The source of light may be an ordinary incandescent filament lamp. The photoelectric cell used by the authors of the above-mentioned paper was a potassium hydride, gas-filled cell.

In operation, when light falls upon the sensitive cathode of the cell, the "light signal" charges the grid of the vacuum tube and actuates the relay in its plate circuit. The relay can be made to operate any apparatus that is designed.

A NEW TYPE OF SELENIUM CELL

AN extremely simple process of making selenium cells was recently described by R. E. Martin in the April, 1928 *Journal of the Optical Society of America*. This simplicity of construction should appeal to experimenters who are interested in making light-sensitive cells and especially those who must work with limited resources.

Powdered vitreous selenium is placed in a pyrex test tube and heated to slightly above its melting point (217 deg. C.) in an electric furnace or over a Bunsen flame. The selenium is then allowed to cool slowly and, as the temperature decreases, it becomes more plastic. By turning the tube nearly upside down, the viscous selenium can be poured from the edge of the tube in long cylindrical threads, the diameters of

which depend upon the temperature. The size of the threads which were found to be most suitable for making up into cell form were about 2 cm. long and 0.1 cm. (79 x .039 in.) in diameter.

The annealing or rendering the selenium light-sensitive is the next step to be undertaken. A thread of selenium is placed on a piece of glass or mica which rests on a copper plate. This is heated from below by an open flame or, preferably, by an electric heater, the latter permitting better temperature regulation. As the temperature is gradually raised to about 130 deg. C. (266 deg. F.), the selenium changes from a shiny black material to the familiar dull grey of the light-sensitive crystalline variety. After the thread is entirely crystallized, the temperature is slowly raised toward the melting point and the thread is observed through a small magnifying glass. When the first signs of melting are noticed (that is, as soon as the crystalline structure shows signs of disappearing), the temperature is immediately lowered 6 or 7 degrees and held constant for about 30 minutes. Again the temperature is gradually lowered to about 180 deg. C. (357 deg. F.), held there for several hours, and finally reduced slowly to room temperature.

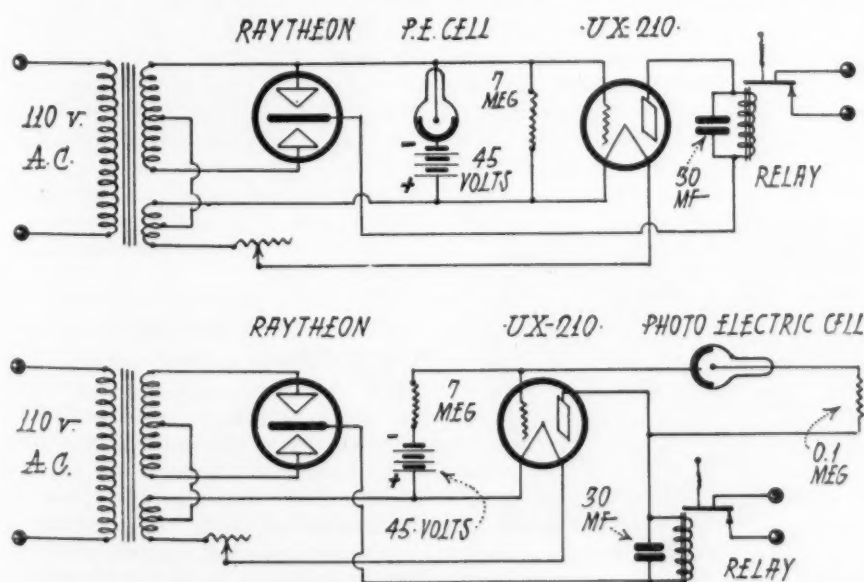


Fig. 1. Construction of Selenium Cell

The electrodes or terminals of the cell are now attached. These may be fine wires of platinum, nickel or copper which are passed through the holes previously drilled in the glass or mica insulating base and bind the selenium tightly to it. The advantage of this form of construction is that the electrodes may be attached after the cell has been annealed, since the metal of the electrodes combines with the selenium to produce metallic selenides, a combination which is thought to be detrimental to the action of the cell.

When this cell is connected in series with a battery and a current measuring instrument (0 to 15 scale milliammeter), a current flows through the cell even in the dark. Exposure to light lowers the electrical resistance of the selenium and the pointer of the milliammeter will indicate this by moving to a higher value according to the intensity of the light. These cells have a resistance of about 1/2 megohm.

Selenium fumes are poisonous, especially affecting the delicate membranes of the throat. Therefore, the experimenter should work either in the open air or carry out the heating under a hood as used in chemical laboratories.



Circuit Diagrams for a Photoelectric Power Amplifier

SYNCHRONOUS MOTORS FOR VISUAL COMMUNICATION

IN a recent paper T. Thorne Baker observes that the attainment of absolute synchronism between transmitting and receiving equipment is one of the chief reasons for the success of modern phototelegraphic systems, as the greatest failures in the early days of this means of communication were largely due to the lack of perfect timing between the apparatus of the two stations.

The earlier methods of obtaining synchronism included the use of electrically controlled clocks, pendulums, etc. The so-called "stop-start" system was also in vogue. By this method the receiving cylinder was turned over at a rate slightly in excess of that of the transmitting cylinder and was stopped at the completion of each revolution by some mechanical means until a signal from the sending station released it as the transmitting cylinder began the next revolution. This system, while simple and economical, is not very effective in the transmission of photographs in which a high grade of reproduction is demanded.

Synchronism for television is only another name for trouble raised to the nth power. When it is seen that the sending of a single picture in about four minutes involves difficulties, the synchronizing of apparatus which must deal with about sixteen pictures per second, might seem to come under the head of impossibilities, although someone has said that the word should be banished from the dictionary.

At any rate, modern television experimenters, with very few exceptions, employ synchronous motors. Motors of this type are controlled by the application of a pulsating current. They are used, of course, to rotate the conventional Nipkow disc or some similar device which scans the scene or object before the transmitter, and recomposes the image at the receiving station.

Alternating current motors for this work must be built in accordance with rigid specifications to obtain satisfactory results. The motor should be of the induction type, which does not rely upon a commutator either for starting or running. Since this motor must be placed rather close to the amplifying apparatus, a sparking commutator would create electrical disturbances which seriously distort the pictures. The ideal motor should be silent in operation and free from hum. Moreover, the motor at the receiving station must be so designed that, by inserting a suitable control mechanism in the form of a switch, and a variable resistance, reactance, or a combination of the two, its speed may be changed to and kept constant with the speed of the motor at the transmitting end of the system.

As some of the problems of photoelectricity and electrical image transmission are highly technical, and consequently not of general interest to the average reader, such problems are often not fully treated in these columns. But in order that we may be of service to the more advanced experimenter, we will gladly answer specific questions of this nature by mail. There is no other obligation than that the correspondent accompany such requests for information with a self-addressed, stamped envelope. Address the communication to John P. Arnold, 541 S. Yewdell Street, Philadelphia, Penn.

A recent engineering test of the requirements of motors employed for driving television scanning discs has revealed some interesting facts. The scanning disc as used for television reception is usually anywhere from 9 to 24 in. in diameter, 1/16 to 1/8 in. thick, and is often made of aluminum, although other metals and some materials like bakelite are used. Such discs can be driven by 1/15 h. p., 110-volt, 60-cycle, single-phase motors. With a perfectly true 15-in. disc, such a motor runs within 50 or 75 revolutions of the synchronous speed.

In order to reduce the speed to that required for the particular television system, it is only necessary to place a series resistance in the circuit with a means of short-circuiting about 15 per cent of the resistance. For example, a 15-in. disc, 1/8-in. thick, with a required speed of 1080 revolutions, needs a fixed resistance of 160 ohms, with a switch shunted across 25 or 30 ohms for the purpose of control.

Although this method has proved fairly successful, there is another way of obtaining more stable operation. As a flat disc is practically a frictionless load upon a motor, it is an advantage to load it in some way. For instance, if six small blades, 1 by 2 in. are placed around the circumference of the scanning disc, a slight load is placed on the motor, enabling the receiving operator to hold the speed of the disc more constant because the motor then responds to changes in speed much more readily. The motor will require only 30 ohms fixed

resistance, with approximately 5 ohms to be short-circuited for adjustment, assuming the use of a 15-in. disc turning at a speed of 1080 r.p.m.

With a load of this kind, it is possible to produce any speed from about 1700 r.p.m. down to 300 and maintain it very easily by the selection of the proper amount of resistance placed in the supply lead. A mechanical resistance, such as fins or blades attached to the scanning disc, helps to stabilize and enables the operation to more rapidly synchronize the receiving motor with the transmitter.

Although the 1/15 h. p. motor is quite

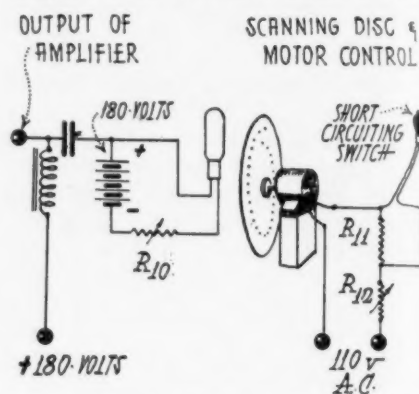


Fig. 1. Circuit Diagram of Television Receiving Equipment

satisfactory in the case of scanning discs of from 9 to 15 inches, when larger sizes are used or heavier loads are involved the 1/8 h. p. Baldor condenser type motor will be more suitable for the work. A motor of this type is shown in the accompanying illustration and is employed in both transmitting and receiving stations. Such motors can also be used for synchronizing in "still" picture systems.

The circuit diagram (Fig. 1) shows the use of such a motor with the usual television receiving equipment. The operator views the illuminated plate of the neon tube, the brightness of which varies in accordance with the television signals, through the scanning disc. When the motor gets slightly out of step with the transmitter, which will be noted when the image appears to be "out of frame," the short-circuiting switch may be closed, speeding up the disc slightly or, when open, the speed is somewhat decreased. In this way, synchronism is maintained between the transmitting and receiving discs.

The Unholy Writ

WE MAKE no bones about defying the lexicographer when it suits our fancy to torment the language of our fathers; yet the recent verbal atrocity, "to televise," causes a rill of shudders to course our spine. We look forward with horror to the possibility of the report that some operatic tenor was "highly enthused to have been televised and broadcasted to an admiring world."



1/8 H. P. Baldor Condenser Type Motor (Interstate Elec. Co.)

PICTURES TRANSMITTED IN ONE MINUTE AT RADIO SHOW

A **RADIO**PHOTO apparatus capable of picking electrical impulses out of the air and converting them in less than one minute into a complete 5x7 photograph was demonstrated at the New York Radio World's Fair. This apparatus, developed in the research laboratories of the Westinghouse Electric and Manufacturing Company, has been used in experimental transmissions over short waves from Station KDKA at East Pittsburgh, Pa.

Because of the difficulty in securing radio wave channel assignment, the demonstrations at Madison Square Garden used wires, rather than air channels, for the transmission of the pictures. Westinghouse engineers state, however, that the equipment functions equally as well by radio as by wire within the limits of fading and static.

The Westinghouse apparatus employs standard photographic processes for making pictures. Its pictures are made by the exposure of sensitized paper to light, in exactly the same way pictures are customarily made in photographic studios.



Dr. Vladimir K. Zworykin, Westinghouse Research Engineer, Inserting One of His Photoelectric Cells Into the Radiophoto Transmitter

In addition to ordinary short wave transmitting apparatus, the system uses three principal pieces of equipment: a sending set, a receiving set, and a "synchronizer."

In the sending set, an ordinary photograph or manuscript is placed on a cylinder which rotates slowly and at the same time moves forward longitudinally. In this way, every point on the picture comes within the range of a tiny beam of light. By a system of mirrors, the

beam of light is reflected at an angle from the photograph to a photoelectric cell, which gives out an electrical impulse corresponding in intensity to the degree of light or shadow of the particular pin-head of space on the photograph covered by the beam of light at



Westinghouse Radiophoto Receiving Set

that particular moment. This procedure, in other equipments, generally requires that a transparency be prepared.

For radio transmission, the feeble currents given out by the photoelectric cell pass through three stages of amplification and then go by wire to the radio broadcasting station, which may be located a short or long distance from the radiophoto sending set. There the light waves, already converted into electricity, go out into the ether in the form of radio waves. At KDKA, the short-wave 63-meter channel was used.

At the receiving end, which could be situated anywhere within the effective range of short waves, a standard short wave receiving set is used to pick the impulses out of the air. The impulses are carried to a special lamp, which flickers according to the fluctuations in intensity of the current. The light from this lamp is focussed into a tiny beam which plays on a cylinder moving in the same ways and at the same speed as the cylinder at the sending end. This cylinder is covered with sensitized paper, and as the light falls on it with varying brightness, a series of impressions of varying degree are made on the paper, which, when "developed," present a facsimile of the picture placed on the sending cylinder.

An essential feature of this system is that the cylinders at the sending set and at the receiving set rotate and move forward at exactly the same speed. To accomplish this very difficult feat is the duty of the "synchronizer." Synchronization is accomplished by the transmission, over the same wavelength used for the radiophoto transmission, of a con-

stant frequency note which regulates the speed of identical synchronous motors driving the two cylinders.

The finished photographs, after passing through the "dark-room" processes of developing and drying, correspond in practically every detail with the originals. If the pictures are held two feet away, it is impossible to tell the original from the copy which has been sent through the air.

SCANNING FOIBLES

Aristarchus, a Greek and astronomer of classical times, noted that the moon has always providentially avoided collisions with our earthly planet. Feeling called upon to exploit away this perverse circumstance, he did so by recourse to the principle which Huygens, later, denominated *vis centrifuga*, a phrase which seems to denote, being translated, the centrifugal force of the physics textbooks. To bring this paragraph up to the very minute, we may point out that the conventional scanning disc for television is an excellent example of the tendency of parts of rotating systems to move away from their center of circumvolution. We mention this because it has been brought to our attention by experimenters who have been treated to impromptu demonstrations of the phenomenon that a disc, insecurely attached to a motor shaft, may depart from thence on a tangential and destructive journey and end up abruptly and partially buried in a wall or ceiling or, mayhap, in some other semi-inert body which stands in its path. Thus, by the operation of the very principle which Aristarchus believed governed the movements of the heavenly orb, a scanning disc will perform certain parabolic peregrinations which may reduce a parlour laboratory to debris and an ardent experimenter to sampling the contents of the arnica bottle. Such happenings are to be deplored; yet to suggest the remedy partakes of the obvious.

Satisfactory radio reception for all tenants in an apartment house may be secured from an untuned antenna and a centrally located r.f. amplifier having a flat characteristic for all broadcast wavelengths. The amplified r.f. current corresponding to each channel may then be separated by a system of filters or fixed tuners. The amplified detector output from each channel can be conducted to a terminal board in each apartment. This board may be equipped with a number of jacks into any one of which the listeners can plug a loudspeaker cord. By providing each jack circuit with a resistance unit having the same impedance as the speaker, a listener may change from one channel to another without affecting the volume of reception in other apartments.

Radio Aids Air Races

By WALLACE S. WIGGINS

OF the 350,000 people who watched the 1928 National Air Races from the grandstands at Mines Field, Los Angeles, from September 8 to 16, not to mention other thousands who failed to get closer than the gates, it is probable that only a few hundred were aware of the important part played by amateur radio in contributing to the success of this great event. The contribution was not "spectacular" in the common meaning of the word in comparison to the hair-raising aerobatics of the contestants, but in the minds of the officials it exceeded all expectations for its utility. The Amateur Radio Research Club of Los Angeles, affiliated with the American Radio Relay League, saw their opportunity to render a service. With the assistance of radio friends, they rendered this service to their credit.

In addition to the transcontinental and international races which finished at the field, several races were scheduled daily over distances of 25 to 120 miles around courses of five and ten miles each. The courses were marked by "pylons"—steel towers flying the "wind sock" at the top and having black and red checkered sides for greater visibility. As the planes circled the pylons, observers checked them according to their lap numbers and closely watched for fouling or cutting pylons, forced landings, plane trouble of any kind, crashes, etc., which made it necessary to have speedy and reliable communication from pylon to pylon and with the judges' stand at the field. Many minor needs for fast communication developed as the races progressed.

Signals by flags or semaphore between pylons were obviously impractical because of distances. Telegraph and telephone were too expensive and the time was too short for such installations. As a last resort, radio seemed to be the only practical solution to the problem, but the expense likely to be incurred might amount to more than the cost of either telephone or telegraph. The air meet was not intended to be a financial profiteering stunt, but rather as a means of contributing to the "air-mindedness" of southern California, in which endeavor it certainly succeeded.

M. E. McCreery, 6LJ, was a member of the committee on communications as sponsored by the Los Angeles Junior Chamber of Commerce. He saw the need of the race officials and put up the proposition to Robert Parrish, 6QF, president of the A. R. R. C. Parrish took the proposition to the members of the club who gave their hearty approval of the stunt and conferred upon their



Bert Fox at 6EMI, Transmitter Constructed by Don Champion, 6FA

president full authority to supervise the job—and a generous share of the work.

Licenses were obtained from the Commission for five stations: one for each of three pylons, one for the judges' stand, and one for an aeronautical exhibit booth in the exposition. "Bob" Parrish, manager of the Pacific Engineering Laboratory Co., supplied the main transmitters and a few receivers. Other transmitters and receivers were supplied by members of the club.

The pylons were not supplied with power, so portable power was necessary. The final decision was for batteries, but how could they pay for them? The average radio club never gets endowments. At least 350 volts were necessary at each pylon to supply plate current to the $7\frac{1}{2}$ -watt transmitting tubes in tuned-plate tuned-grid circuits. Storage batteries were needed for all filament supply, but there was no means for recharging them. What to do? The answers to these questions came in the form of friendly cooperation of the French Battery Co., the Durkee Thomas Corp., and the Western Auto Supply who furnished all the batteries and tubes without charge.

From an inclosed box at the top of the crowded grandstand, a splendid view of the field was had by the operator at "6EMF." Directly in front of the stand was Pylon Number 1. Off to the right and to the west could be seen Pylon Number 2, at a distance of a mile. Here was located station 6EMH. On a line south of the grandstand and about two miles away was Pylon Number 3, with station 6EMI. Pylon Number 4, two and a half miles farther on and in line with Pylons 2 and 3, was designated as station 6EME. It was five miles around Pylons 1, 2 and 3, and ten miles around all four pylons.

Let's watch a race! Here are six planes at the starting line ready for the 720 cu. in. event. The planes are "at rest," waiting for the starter's flag, with motors turning over slowly. Dots and dashes from 6 EMF in the grandstand are flashed to all pylons and they form

the following words: "QST QST DE 6EMF RACE ABOUT TO START QRX (Stand by) FOR QST TON (Take-off numbers)."

The operators at the pylons inform the observers and everyone is in readiness. The starter walks out to the first plane and suddenly dips his flag. The motor roars, the plane moves, rapidly gains speed, and soars into the air toward Pylon Number 2. 6EMF flashes: "THEY'RE OFF!" The remaining planes are started at thirty second intervals and are flown against time. To start all the planes at once would invite needless dangers. Take-off numbers are broadcast to the pylons, and as the last plane leaves the field, the first one may be seen on the home stretch of the first lap. When the "QST TON" has been completed, all pylons answer: "QST OK 6EMH," etc.

Watch these three planes in a bunch as they go around Pylon Number 1! Look at that little monoplane. See how it flits past the others like a little sparrow! Zoom! Zoom! Zoom! The three planes dart off toward Pylon Number 2 again on their second lap as the observers call off the numbers and check. The operator at 6EMF is constantly moving the dial on his receiver between two points. Operating on the 80-meter band, he finds the pylon stations only a few kilocycles apart. 6EMH is at 54, 6EMI at 49.5, and 6EME at 45.5. Not so bad.

Several laps have been completed now. Here comes a plane that seems to be having trouble. The motor sputters, indicating a broken pipe or valve, perhaps. Awful strain, these races on planes and pilots. The plane makes a graceful landing and taxis out of the way. The number is immediately flashed to all pylons. Why? Inside of three minutes would come as many inquiries about the plane and its failure to appear.

Now let's go out to 6EMI, at Pylon Number 3. We are out of sight of the grandstand, but we could reach it by auto in ten minutes through traffic. By airplane, we could get there in one minute! The surrounding country is practically level, but between us and Pylon Number 2 is a small ravine and some trees. We can see the planes coming straight toward us, flying dangerously low, barely clearing the tree tops, and now skimming along the ground to the pylon. They bank sharply, usually gaining a little altitude, circle the marker, and fly off toward the field. This is a five mile race, so they are not using Pylon Number 4.

(Continued on Page 46)

Battery Charging with a Synchronous Rectifier

Complete Details Regarding the Construction and Operation of a Synchronous Rectifier

By G. F. LAMPKIN

A SYNCHRONOUS rectifier is an excellent source of high potential d.c. for transmitting, as testified by the many "syncs" owned by amateur operators. Such a rectifier, as may be known, utilizes a synchronous motor, a commutator disc, and a brush rigging. The commutator is rotated in step with the alternating current, and functions as a switch, reversing at the correct instant so as to bring the output voltage right side up. In its use for high-voltage, full-wave rectified supply it is eminently satisfactory. With a small amount of care it will function just as satisfactorily to deliver several amperes at comparatively low voltages.

The chief advantage of a sync lies in the range of currents and voltages over which it can be used. In the role of battery charging 20 amperes is by no means the limit of current obtainable; while for a transmitter the output voltage can be run upwards of 3000 volts. The metal to metal contact assures a high rectification efficiency. A disadvantage is that the rectifier works best into a resistance load. If an attempt is made to work into a condenser or inductance, as in a filter system, trouble immediately develops through sparking at the brushes. Only by special means can a filter be used on a sync.

A description of a synchronous rectifier will serve the dual purpose of illustrating the processes involved in its operation, and of affording a basis for constructional work. The heart of the rectifier is of course the synchronous motor. The usual nameplate data for a sync-rectifier motor are $\frac{1}{4}$ h.p., 1800 r.p.m., single-phase, 60-cycle, 110-volt. An 1800 r.p.m. motor allows the simplest sort of commutator construction with only two segments.

The brush rigging uses two brushes into which a.c. is fed, and two from which full-wave d.c. emerges—a total of four brushes equi-spaced around the commutator periphery. Fig. 1 shows the commutator position and current


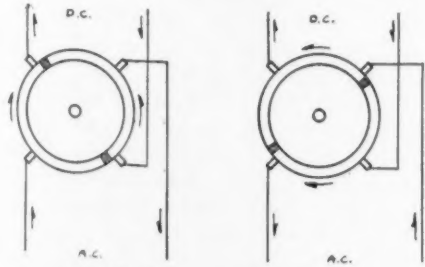


Fig. 1. Commutator Positions

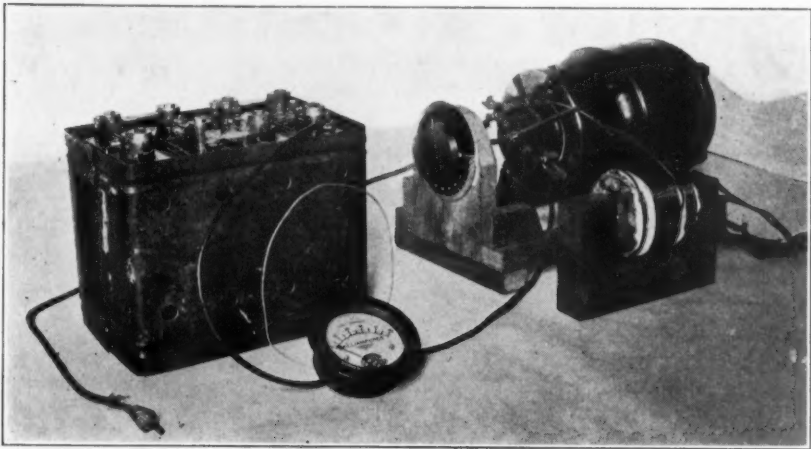

Complete Charging Outfit

flow at the beginning of a positive half cycle, and at the start of the succeeding negative half cycle. The disc, turning 1800 r.p.m., advances one-quarter of a revolution in a half cycle, 1-120 of a second. Thus the conditions of the sketches hold true—though the direction of current in the a.c. source reverses, the commutator maintaining unidirectional flow in the output.

A $\frac{1}{4}$ h.p., single-phase induction motor can be made into a synchronous motor of only slightly less capacity by facing off four flats on the rotor, approximately $\frac{1}{16}$ -in. deep, as indicated in Fig. 2. It is a simple machining operation, which, with the turning of the commutator disc, is the total of machine work necessary. The flats on the rotor of an induction motor form air gaps across which the flux is reluctant to slip, and the rotor holds in step with the impressed

frequency. The induction motor must of course have four poles, so that its name-plate speed would be around 1740 or 1760 r.p.m.

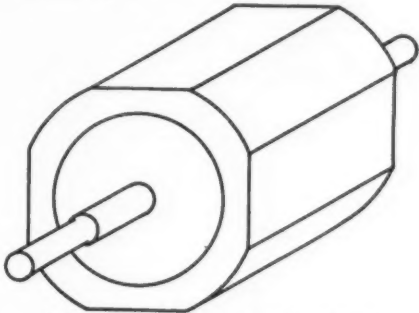


Fig. 2. Conversion of Induction to Synchronous Motor

The commutator disc in Fig. 3 was designed as small as was consistent for operation at 3000 volts. The larger the wheel, the greater is the space available

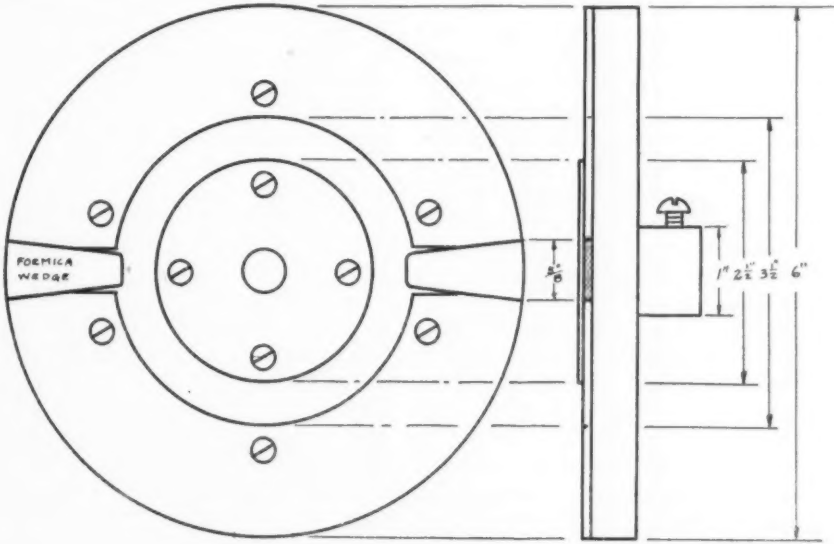


Fig. 3. Commutator Disc

for insulation. But also greater is the power necessary to turn the disc, for the friction and windage losses are increased. The disc proper, shown in the sketch, was cut from $\frac{1}{2}$ -in. micarta. The bushing for the shaft was turned from $2\frac{1}{2}$ -in. round brass bar; and the commutator was made from $\frac{3}{32}$ -in. brass. The latter was fastened to the disc by screws inside the brush path. Both this, and the filling of the slots between segments with drive-fit formica plugs, afforded a smooth brush path. Such a path not only reduces brush friction, but aids materially in keeping sparking at a minimum. In turning the disc a final smoothing cut should be taken over both segments and insulating sectors.

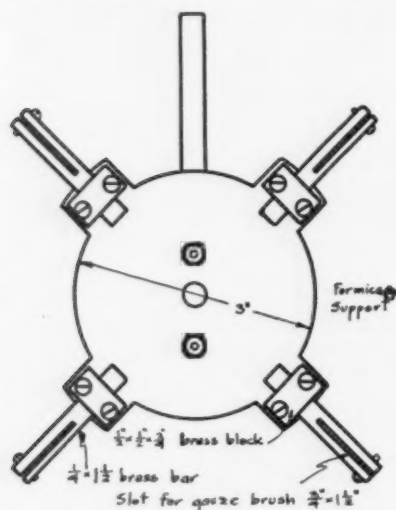


Fig. 4. Brush Details

Two bakelite dials were made to the foundation of the brush rigging. Copper gauze brushes and brass fittings completed the assembly, of which Fig. 4 gives details. The set-screw in one dial was removed and replaced by a threaded insert in an insulating rod. The latter was to afford a means of brush adjustment. Four thicknesses of medium copper gauze were used in each brush.

In the adjustment of the brushes lies the secret of sparkless commutation. When motor, commutator disc, and brush rigging have been assembled, the brushes should be carefully adjusted to bear equally on the commutator; the ends of the brushes should be parallel to a radius of the disc; the brushes should be exactly 90° apart; and two diametrically opposite brushes should make and break contact with the segments at the same instant. It is essential that severe sparking be eliminated, otherwise the brush and commutator life will be short. Elimination of sparking on a transmitter sync spells the difference between hash, and the distinctive, musical sync note.

Before using the sync under load the disc should be thoroughly cleaned, especially around the insulating sectors, of all metallic dust. Then place 110 a.c. on two brushes, 180° apart, and connect a

lamp to the other two. Determine and fix the position of the brushes for maximum brilliancy of the lamp. The rectifier is then ready to feed 20 amperes to a battery, or 3000 volts to a transmitter.

For ordinary battery-charging, a 50 or 75-watt toy transformer is ideal. It is cheap, convenient, and usually with adjustable secondary voltage so that the charging rate can be varied. For each charging rate it is necessary to adjust the position of the brushes slightly. Both angular position and pressure on the disc should be changed till sparking is at a minimum.

The design data for a transformer which has been in this use by the author for over a year are as follows:

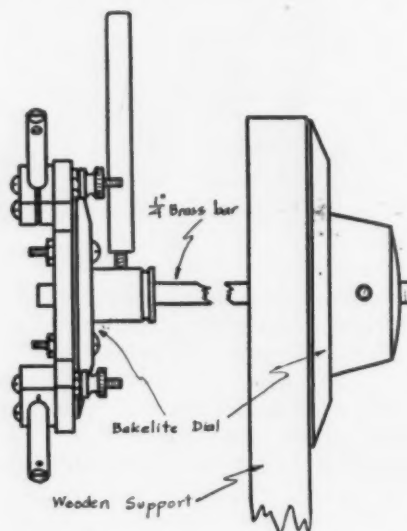


Fig. 5. Circuit Diagram with Reversing Switch

stance as drawn in Fig. 5. With a d.c. voltmeter the polarity of the rectifier can easily be determined, and correction made if necessary, before closing the charging switch. An a.c. voltmeter can be used by closing one side only of the charging switch. The voltage of both battery and rectifier in series is then read across the other open side of the switch, and that polarity of the rectifier which gives the smaller reading is correct for charging.

It is a simple matter to make a shunt for a milliammeter so that it will read the d.c. charging current, and by doing so it will aid materially in the operation of the sync. The meter in the picture was a Jewell, pattern 54, 0-100 d.c. milliammeter. A shunt of $17\frac{3}{8}$ " of No. 14 tinned bus wire converted it into a 20-ampere meter. If a standard ammeter is temporarily available it is only a matter of minutes to find the size and length of wire necessary to give any desired ammeter scale on a milliammeter.

The overall efficiency of any a.c. to d.c. unit is something that is seldom mentioned. Figures for such range from 50 to 5 per cent. With this outfit the input to the motor on the sync was 220 watts. If no resistances are used for charging-rate regulation, that figure may be taken as representative of practically the total power loss of the system. The more power put through the rectifier into the output circuit, the less is the cost per unit of output.

As stated before, the rectifier may be used for a 3000-volt transmitter supply. Actually it has been used to rectify 3300 r.m.s. or 4650 peak volts, when supplying 150 milliamperes to a c.w. transmitter.

Any a.c. hum from a filter circuit may best be reduced by increasing the capacities of the second and third condenser so as to by-pass the a.c. component of the rectified current. Humless operation requires that this component be less than 0.1 per cent. With a load of 75 milliamperes, 4 mfd. each in the second and third condensers give 0.07 per cent of hum, whereas 2 mfd. condensers give 0.3 per cent. When an eliminator is intended to supply more than 85 milliamperes a condenser block of 2-6-6 mfd. is desirable as such a great current drain increases the tendency to hum.

Core cross section..... $1\frac{1}{2}$ " x $1\frac{1}{2}$ "
Core window..... $1\frac{1}{4}$ " x 4"
Primary winding 330 turns No. 20 SCE on long leg.
Secondary winding 45 turns No. 12 PE over primary.
Voltage primary 110, secondary 16.3, 60 cycles.

The layout was used to charge an 8-cell, 20-ampere-hour Edison battery at around 20 amperes. Such a charge filled the battery up in short order. More conservative rates should be used, of course, when charging lead cells. The secondary voltage of the transformer may be cut as desired by reducing the secondary turns proportionally. That is, for a secondary voltage of E , the new number of secondary turns is $E \div 16.3 \times 45$. The charging rate may be varied by using variable resistors of appropriate rating in the transformer primary or secondary. The best method is to use a tapped transformer.

A battery may be charged at around 5 amperes by connecting it to the rectifier output, and placing an electric iron in series with the 110-volt lines on the input—though such is hardly economical, because the iron gets most of the watt hours. The service man, however, may have enough batteries to connect in series and charge directly from the 110 supply.

The polarity of the output must be checked each time the rectifier is started

A Complete Tube Testing Set

By CLINTON OSBORNE

WHILE a number of tube testers have been described in past issues of RADIO, there have been none so complete in the number of possible tests which can be made, as the one described herewith. This tester was made up from suggestions contained in a tube data book recently published by E. T. Cunningham, Inc., and with it, the service man, experimenter or tube salesman can tell practically everything necessary about the condition of any of the standard tubes.

The tester is shown in the picture, and the circuit is shown in Fig. 1. The set has been designed to test all types of tubes, both a.c. and d.c. with the exception of the 374 glow tube, the 376 resistance lamp and the 300-A detector. It will give an accurate indication of the condition of the elements and, if the tube is operative, will also indicate the efficiency of the filament. Above all, it is inexpensive to construct.


The necessary materials for construction are given in the list of parts. The work is simple inasmuch as there are no complicated circuit arrangements; the meters, sockets, rheostats, etc., may be conveniently mounted on a bakelite or wooden panel, with a cabinet to conceal the wiring, or can be laid out on a baseboard. The actual layout and constructional details are left to the judgment of the builder, as it is thought that

the circuit diagram and picture will furnish sufficient data for all practical purposes.

In building the test set, the variable rheostat should be of the 10-ohm size, capable of carrying $1\frac{1}{2}$ amperes under continuous load. The fixed resistance R should be exactly 6 ohms, and is placed in the negative A lead from the No. 2 and 3 sockets to the 4-volt line of the battery. The switchboard key must be connected so that in its normal position it will indicate short circuits. If this connection is reversed so that the emis-

sion reading is taken first, the meters or the tube may be damaged, if the tube elements are shorted together.

To place the set in operation, turn the rheostat on slightly and set the switch A to the point indicating the corresponding socket number or numbers, these figures indicating which tubes may be tested in the correspondingly numbered socket. For example if switch is on contact 2-3, type '99s, 220s, or 322s in socket No. 2 may be tested, and '99s in socket No. 3 may be tested. If switch is on contact 4, C-11s, 12s and 326s may be tested

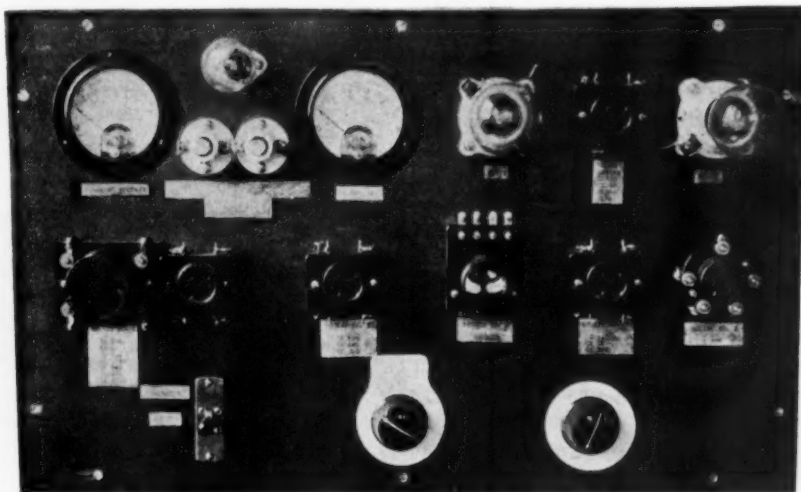

Panel View, showing Arrangement of Sockets and Meters

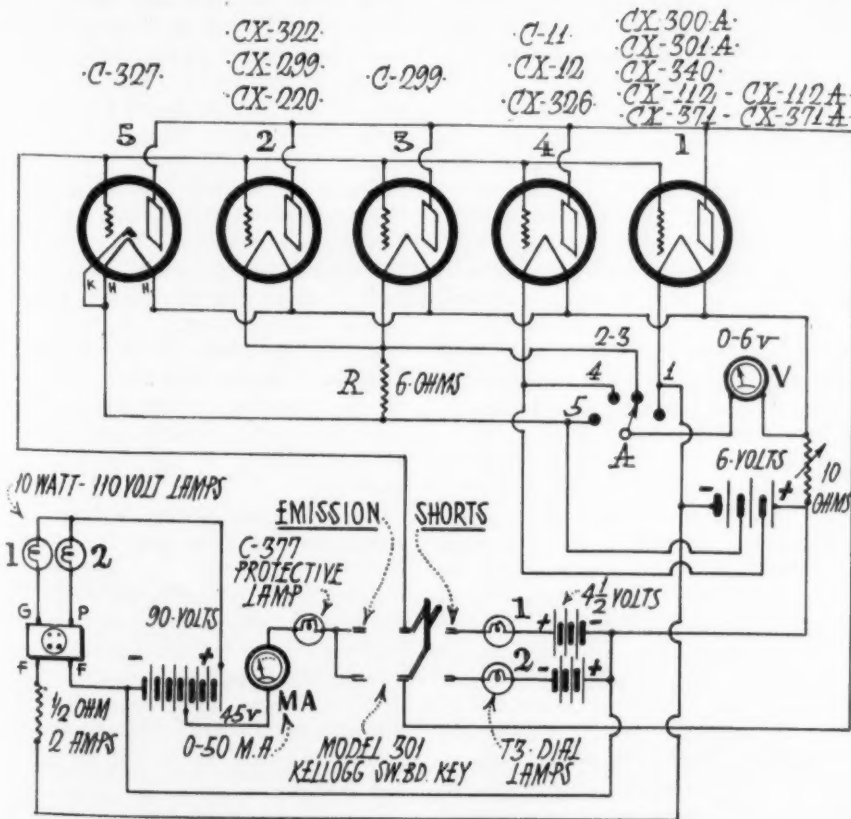


Fig. 1. Circuit Diagram of Complete Tube Tester

in socket No. 4 and so on: the tube to be tested is then inserted into its proper socket.

Note very carefully whether the dial lamps Nos. 1 and 2 are lighted, or even very faintly glowing. If they are, it is an indication that two or more elements within the tube are shorted, or that the filament is open and resting against the grid. To determine if the latter is the case, turn the rheostat up and if no regulation of voltage is possible, an open filament is indicated. If lamp No. 1 lights, a short between filament and grid is indicated; if No. 2 lights, it indicates a short between filament and plate; if Nos. 1 and 2 light, it indicates a short between grid and plate.

If neither lamp lights, then the elements are free from short circuits and the rheostat should be turned up until the voltmeter shows that exactly the proper voltage, as given in the accompanying chart on voltage and emission limits, is being applied to the filament. If the rheostat has no effect on the filament voltage it indicates an open filament, either broken or burned out. When the voltage is correct, momentarily press the switch indicating the emission current.

(Continued on Page 50)

The Marshall Short-Wave Receiver

A New Short-Wave Circuit Developed for the Navy and Using Screen-Grid Tubes

By S. R. WINTERS

A NEW high-frequency receiving set designed and built at the Bellevue Naval Research Laboratory incorporates the screened-grid or four-element electron tube. This receiver, intended for use on battleships and other floating units as well as at shore stations of the United States Navy, marks the introduction of a push-pull, screened-grid type of receiving set in the Government service—a type of amplifier already popularized by broadcast listeners and radio amateurs. However, this novel circuit is said to be the most sensitive yet developed by the Navy for high frequencies.

This high-frequency receiver is described as a single-stage tuned radio-frequency amplifier, preceding an autodyne detector and two stages of audio-frequency amplification. It is a six-tube unit, including two four-element tubes, connected for push-pull operation, as well as two detector tubes. A frequency range from 4,000 to 25,000 kilocycles is embraced—this extensive wavelength range requiring the use of five inductance coils of varying sizes. Thomas A. Marshall—then a student and research worker in electron tubes at the Bellevue Naval Research Laboratory—designed this receiver.

The so-called "Marshall Receiver" employs two tubes of the '22 type in the radio-frequency circuit—each of these tubes having two grid elements and being wired for push-pull operation. These two four-element tubes operate on 3.3 volts for the filaments, 120 volts for the plates, and 60 volts for the plate screens.


The two detector and two audio-frequency tubes are the '01A type and require 5 volts on the filaments. Forty-five volts are impressed on the plates of the detector tubes but this potential may be varied by use of a potentiometer. The two audio-frequency tubes use only 60 volts on their plates as the sole negative bias available for the grid elements is a one-volt drop in the filament rheostat. The batteries necessary for the entire power supply are a 6-volt, 100-ampere-hour storage battery for the *A* supply, and a 120-volt *B* battery with 45- and 60-volt taps.

The antenna circuit of this novel short-wave Naval receiver consists of a small antenna coupling condenser, connected through a series inductance to the ground. This series inductance coil is coupled to the tuned input-inductance of the amplifier. These two inductance units are wound on a plug-in coil system.

When the latter is plugged into the receiver, the tuned-input inductance is connected across the tuning condenser or series inductance. A compensating condenser is employed across the tuning condenser to compensate the extra residual capacity which is present in the tuned detector circuit. This effects a dial alignment of the two circuits, thus insuring a similarity of dial readings for both the radio-frequency and detector variable condensers. The tuned circuit of the radio-frequency amplifier tuning con-

that of the internal tube output impedance. This could, in a receiver of limited tuning range, be accomplished by adding a plate-circuit tuning control. But as simplicity of control, and a minimum of parts and space, is a general and important requirement in Naval service receivers, attempt has been made to employ fixed chokes for this purpose."

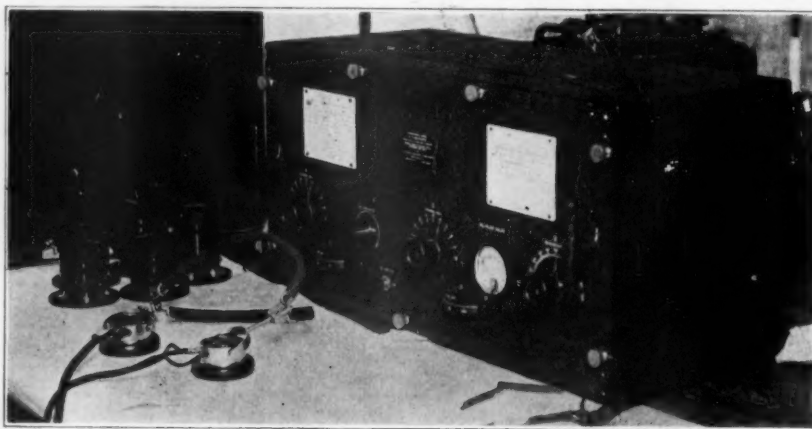Therefore, in the "Marshall Receiver," two high-inductance, low-capacity chokes are employed throughout the frequency range of 4,000 to 25,000



Marshall Short-Wave Receiver, as Used by Navy

denser and the radio-frequency amplifier grid-circuit inductance feeds to the grids of the two push-pull tubes through two grid-coupling condensers.

The tuning condenser comprises two series halves with a rotor member common to both. The rotor is connected to the filaments and virtually is at ground potential. This is intended to eliminate hand or body capacity effect. Likewise, this series connection affords a relatively low capacity value—a minimum of approximately 8 mmfd. and a maximum of 57 mmfd. This gives a ratio of about 7.1 to 1, and yet the maximum capacity is quite small—resulting in a relatively high ratio of inductance to capacity. This is essential to effective amplification. The radio-frequency amplifier grids obtain their direct-current bias through 1-megohm grid leaks, which are connected to the junction between two filament-control resistances, thus affording a negative bias of 1.7 volts. The plate screens are maintained at plus 60 volts with respect to the filaments.

"In all amplifier work," emphasizes the Bellevue Naval Research Laboratory, "it is essential for greatest amplification that the external plate circuit impedance be kept relatively higher than

kilocycles. A third and similar choke has been positioned at the junction of the two plate chokes and in series with the *B* battery lead-wire. The latter choke coil serves the function of barring radio-frequency currents from the *B*-battery circuit. This additional or third choke likewise serves the purpose of isolating the junction of the two plate chokes from the ground potential. This permits of the chokes finding their own electrical center, which may be different from that of the apparent center, due to electrical irregularities in the two tube and choke circuits. This arrangement is an aid in the preservation of symmetry, which is essential to efficient and stable operation of the receiver at the ultra-high frequencies.

The detector circuit and the radio-frequency amplifier are in individual shielded compartments. The two are coupled by two fixed condensers, small enough to prevent reaction of the amplifying circuit on the oscillating detector circuit. The capacity values of these two condensers, however, are not detrimentally low—that is, they do not cause a loss of signal in so far as ear tests can determine.


The tuned detector circuit employs a "plug-in" inductance system similar to

that used in the antenna circuit. This, labelled "Detector Coil," includes the grid inductance and the tickler feed-back inductance. The tuning condenser in the detector circuit is similar to that employed in the amplifier circuit. The push-pull performance of the two detector tubes again gives practical application to the sound engineering principle of a large inductance in relation to capacity. This insures a greater amount of inductance with which to couple the inductive tickler feed-back than any single-

tube circuit. Furthermore, we are assured by the Navy Department, this combination gives a circuit that oscillates with ease throughout the entire frequency range from 4,000 to 25,000 kilocycles.

The tickler feed-back inductance coil is tapped in the center—the two ends being associated with their respective plates and the center to the plus-B battery through a radio-frequency choke and the primary winding of the first audio-frequency transformer to the re-

generative-control potentiometer slider. This, in turn, is connected across 45 volts. Regeneration or oscillation control is effected by varying the direct-current voltage on the plate elements of the two detector tubes, using the potentiometer for varying the potential. The potentiometer slides, operated by manipulation of a knob on front of the radio-receiver panel labelled "Regeneration Control," is by-passed to shield or ground through a 2-microfarad condenser.

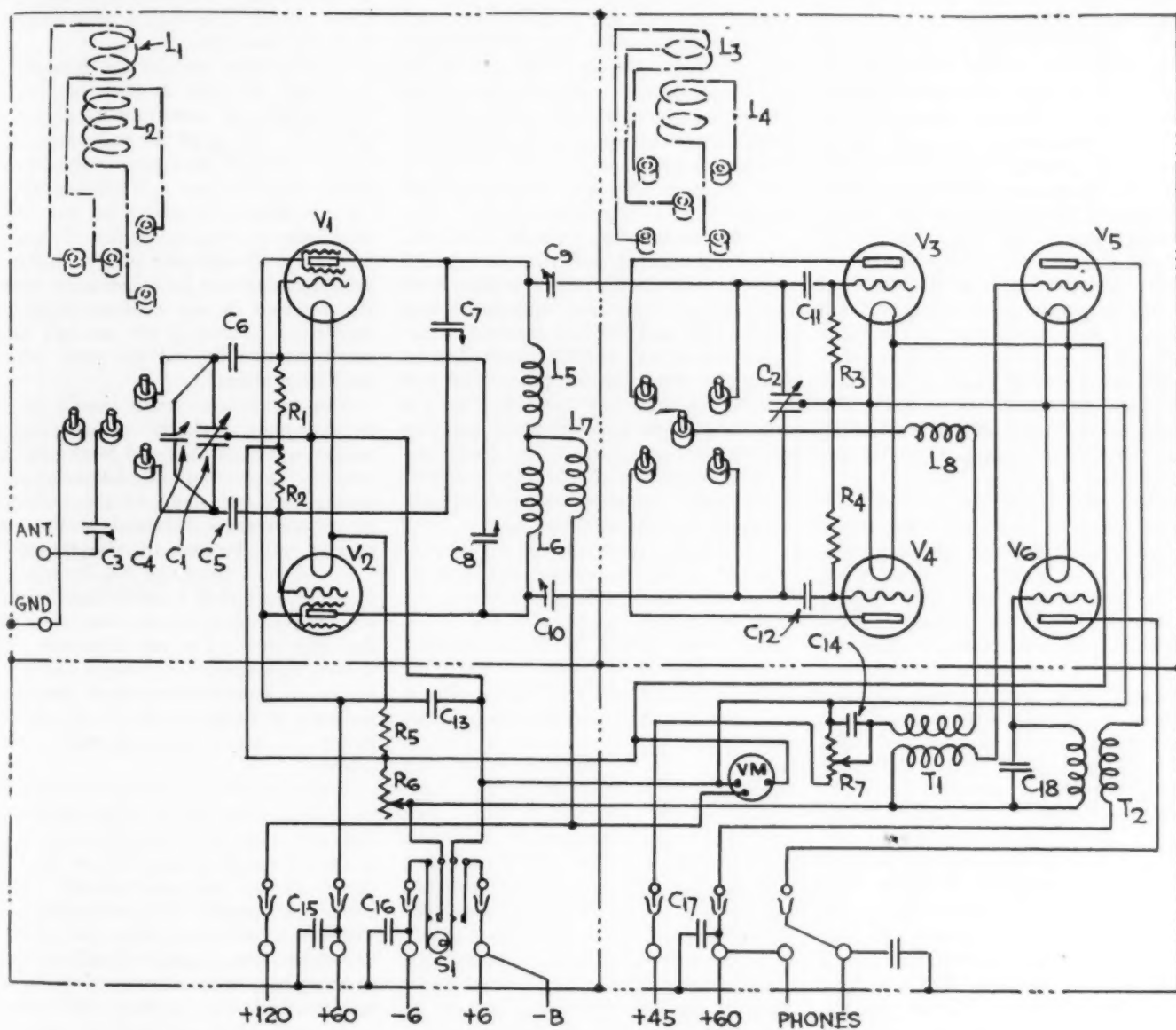

Circuit Diagram of Marshall Short-Wave Set

V₁ V₂—Radio-frequency amplifier tubes, type UX-222.

V₃ V₄—Detector tubes, type UX-201-A.

V₅ V₆—Audio Amplifier tubes, type UX-201-A.

L₁—Antenna Coupling Inductance.

L₂—Radio-frequency amplifier grid circuit inductance (Both L₁ and L₂ wound on r.f. amplifier coil form).

L₃—Tickler feed-back inductance. (Wound on "DET" coil form).

L₄—Detector grid circuit inductance. (Wound on "DET" coil form).

L₅ L₆—Low distributed capacity 250 m.h. plate chokes in r.f. plate circuits.

L₇ L₈—Low distributed capacity 250 m.h. plate chokes in battery leads.

C₁—R.F. amplifier tuning condenser.

C₂—Detector circuit tuning condenser.

C₃—Antenna coupling condenser.

C₄—Compensating condenser to assist in dial alignment of r.f. and "DET" tuning condenser.

C₅ C₆—Grid coupling condensers from tuned r.f. circuit.

C₇—Balancing condensers to balance out reaction of amplifier on autodyne circuit.

C₈ C₉—Coupling condenser from r.f. stage to autodyne circuit.

C₁₀ C₁₁—Detector grid condensers.

C₁₂—Bypass condenser on plate screen voltage lead.

C₁₃—Bypass condenser on oscillation control resistance.

C₁₄ C₁₅ C₁₆—Bypass condenser on battery leads.

C₁₇—Tuning condensers on second audio transformer to cut out audio oscillation.

R₁ R₂—Grid closure resistances to establish proper bias on amplifier tubes.

R₃ R₄—Grid leak resistances for detector tubes.

R₅—Fixed resistance in series with R₆ giving 3.3 volts on amplifier tube filaments.

R₇—Variable filament control resistance.

R₈—Potentiometer 100,000 ohms on 45-volt detector plate battery for oscillation control.

S₁—Filament switch that also disconnects R₇ from circuit.

T₁ T₂—Audio-frequency transformer type CAY 4342.

The first audio-frequency tube is fed from the secondary winding of a transformer—type CAY4342—while this tube's plate circuit feeds into the primary winding of another transformer, of the same type as the first. The primary winding of the second transformer is slightly tuned with a .0001-microfarad by-pass condenser on the oscillation-control resistance. This, in effect, cuts down the amplification of the higher audio-frequencies, above 1,500 cycles, and correspondingly reinforces the lower frequencies. The secondary winding of this transformer feeds the second audio-frequency tube, while the plate circuit of the latter extends to the telephone connection and through the head telephones to the 60-volt *B*-battery terminal.

The controls on the front of the receiver panel, reading from left to right, are the radio-frequency tuning condenser for bringing into resonance the radio-frequency amplifying stage, the autodyne-detector-circuit tuning condenser, and the regeneration control. An "on" and "off" filament switch is located centrally and near the bottom of the front panel. This switch opens both sides of the filament battery and at the same time opens the potentiometer across the 45-volt supply, thus preventing the *B*-battery from discharging when the receiving set is not in operation.

A voltmeter gives indication of the filament voltage on the '01A type tubes. When the voltmeter-push-button switch is pressed the maximum *B* voltage as applied to the two screened-grid tubes is indicated. These four-element tubes require a filament voltage of 3.3 volts and this current is supplied when the voltmeter reads 5 for the 'A tubes. A single filament rheostat is supplied for the *A* battery control. The screened-grid tubes are fed with energy through the latter resistance unit and through an additional series resistance. The latter should afford a drop of 1.7 volts as required for the efficient operation of the receiver.

The receiver is 22¼ in. long, 10¾ in. high, and 9¼ in. deep. The parts, including diaphragm shielding and wiring, are made secure to the front panel. Withdrawal of the latter displaces completely the receiving set from the box and at the same time automatically disconnects battery, telephone, antenna, and ground leads. These leads, entering the box or receiver container, are permanently fixed to the box fittings. The external connections are made to the receiver circuits through sliding contacts, which close when the panel is secured in place.

The outstanding feature of this new short-wave circuit—its extreme sensitivity—is also its serious limitation. "This receiver has much greater sensitivity at the higher frequencies than any previously supplied to the service," is the unqualified statement of the Navy Department. For this same reason, the

set must be mounted on a shock-absorbing pad and the detector tubes inserted in jackets of sponge rubber; otherwise, microphonic noises are so disturbing as to practically defeat the otherwise superior merit of this receiver, namely, ultra-sensitivity.

"The high-frequency receivers as developed in the past," points out the Bellevue Naval Research Laboratory in discussing the theory and operation of this new circuit, "using the customary three-element tubes, have been incapable of giving much amplification over the higher-frequency end of their range and in some cases give a loss above 8,000 kilocycles. With the development of the new four-element tube, which may be called the shielded-plate tube, together with a new circuit arrangement, it is possible to get an appreciable amount of amplification over the entire high-frequency band as now employed.

"The two factors which have previously prevented radio-frequency amplification at the higher frequencies have been the relatively low input impedance of the tube and the low ratio of inductance to capacity, which has existed when using the three-element tube. The low input impedance has resulted from the relatively high grid filament capacity which has under operating conditions been in effect several times the geometrical capacity—being controlled principally by the grid-plate capacity.

"The new circuit employs a push-pull type of radio-frequency amplification, where each of the tube-grid-filament circuits are across but half of the tuned circuit input voltage. This decreases the grid-filament conductance to half for each tube and as the two reactances are in series the total conductance across the tuned circuit is one quarter what it would be for a single-tube-amplifier stage. When the effect of the grid-plate capacity of the three-element tube is considered it is apparent that the push-pull combination with four-element tubes will increase the tube input impedance many times. This improved condition makes it possible to maintain a much higher potential across the tuning-condenser terminals, or the two input grids, than by previous methods. The use of the symmetrical push-pull circuit, which permits a larger ratio of inductance to capacity to prevail, together with the adoption of the four-element tube, has been highly responsible for the improved results at the higher frequencies."

The two screen-grid tubes are equipped with balancing condensers to avoid interplay or disturbing reaction between the stages of radio-frequency amplification and detector. These condensers are located beneath the two holes in the cover which have been blanketed with a butterfly-spring arrangement. Reaction between the different stages in the circuit may be overcome by shifting the vacuum tubes in different sockets.

If, however, the trouble persists, the Navy Department indicates that the balancing condensers will accomplish the desired result if this procedure is followed:

The receiver—which may be operated on an antenna only a few feet in length or one several wave-lengths long—is connected to the pickup system and No. 1 inductance coil brought into use. The cover over the adjusting holes in the main cover is removed or loosened and turned 90 degrees, in order to render accessible the condensers with the main cover closed. The lock-screws on these units are loosened.

The receiver circuits are brought in resonance with the detector oscillating. An unbalanced condition is evidenced when the tuning of the radio-frequency circuit through resonance with the detector circuit, when it is barely oscillating, produces a squeal in the head telephones or stops oscillation. This condition is well-nigh ever present, but it is possible to obtain an adjustment where the reaction is not evident when the oscillation control is set one-half of a small division beyond the point where oscillation starts.

The oscillating circuit should be set to this point and the radio-frequency control operated back and forth past the resonance point until the balancing condensers are adjusted. If the receiving set is apparently balanced at the top, middle and bottom of the frequency range of inductance coil No. 1 then it is to be assumed that a satisfactory balance has been assured for the four other inductance coils. For the balancing condenser adjustments a bakelite, fiber or hardwood screwdriver is used, since the presence of metal would defeat any attempts to adjust these balancing condensers.

While the Radio Division of the Bureau of Engineering is prone to classify this new short-wave receiver as still in an experimental stage—due to its tendency to set up microphonic noises when not situated in a shock-absorbing, steadfast position—twelve or fifteen units have been manufactured. Several of these have been introduced to Naval service—both on surface and subsea craft—and when subjected to comparative tests with a standard short-wave set of Navy design the results have been gratifying, in some particulars at least.

For example, while in service on the *Eagle*, a patrol boat for conducting sound and radio experiments, the strength of the signals received by the "Marshall receiver" were stronger than those tuned by the standard Navy short-wave set—though the signals of the latter were more readily tuned and the distant stations more easily located. The selectivity of the "Marshall receiver" was marked and once the stations were logged the dial could be consulted time

(Continued on Page 49)

TECHNICAL BRIEFS



TRANSATLANTIC radiotelephone service between the United States and Great Britain as well as various cities of Continental Europe, Canada, and Cuba is normally available from 5:30 a. m. to 8:00 p. m., eastern standard time. The British receiving station is at Cupar, Scotland, as far north as conveniently possible so as to reduce interference caused by atmospheric disturbances.

THE R. C. A. projector system used in long distance radio communication includes both directive transmission and directive reception on short waves. Several receiving antennas, directive in themselves, are spaced so as to eliminate the momentary fading which originally limited the use of short waves.

RAILWAY radiotelephone equipment has been developed for front-to-rear communication on long freight trains. A four-months test of the equipment by the Chesapeake & Ohio Railroad showed that telephonic communication could be maintained between the locomotive and caboose whether the train was standing or in motion and even when the train was broken if the separation did not exceed five miles. A signal system of lower power has been developed for service between the front and rear of long freight trains. One-way telephonic communication with low power equipment may also be maintained between the yardmaster's office and any locomotive in the yards.

THE demand for quartz crystals for controlling the frequency of radio transmitters is supplied mostly from Brazil. The present price is about \$3.00 per lb. To be acceptable to the Naval Research Laboratory at Anacostia, D. C. they must be single crystals weighing at least two pounds and must show growth lines on at least two faces. They must be free from imperfections such as internal fractures and inclusions of foreign matter. They must be absolutely clear when viewed by transmitted light.

THE radio experimenter may find much interest in utilizing the radiated output of a short-wave oscillator to produce luminous discharges through rarefied gases in tubes such as the neon tubes which are now used in electric signs. Whereas a high voltage is necessary to produce a glow when low frequency alternating current is used, relatively low voltages are needed at high frequency.

Thus James and Wilfred Taylor, in a recent issue of *The Wireless Engineer*, London, describe some experiments with a 35,000 k.c. (8.57 meters) oscillator whereby beautiful discharges were produced at 15 volts. In the circuit diagram of Fig. 1 the plate *B* and the grid *D* are connected to two parallel copper wires about 50 in. long and 3 in. apart. A

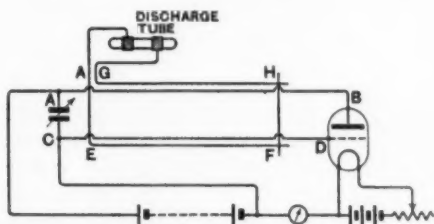


Fig. 1. Circuit Diagram for High Frequency Generator and Discharge Tube

.001 mfd. variable condenser is shunted across the ends of these wires at *A C*, *A* being connected to the positive terminal of a 220-volt d.c. source and *C* to the negative terminal. *E, F, G, H* is a tuned system coupled to *A B D C* by the Lecher wire method. Two annular rings of copper foil are wrapped around the outside of the glass tube to serve as electrodes.

Different colors and forms of discharge occur as the gas pressure or gas composition is varied. The experiments were made with air, neon, helium and mercury vapor. The discharges are caused by the motion of the electrons between the electrodes; light is emitted as an electron jumps from an outer to an inner orbit as it collides with a gas molecule.

THE economically-minded person sometimes objects to the thought of using an apparently wasteful voltage divider to supply 45 and 90 volts to

a radio set from a rectifier-filter system which also supplies 180 volts or more for a power tube. But when it is realized that the waste current through the divider not only may improve the voltage regulation or stability of voltage output, but also reduce the strain on the filter condensers, its use is well justified.

A rectifier-filter system is a constant wattage device. The voltage drops as the load or current drain increases, increasing the load resistance decreases the load current. When the current drain is increased from any tap, the voltage output and current supplied from the other taps is correspondingly decreased. Part of the increased load current comes from the rectifier-filter system and part from the voltage divider system, both at the expense of decreased voltages.

These facts are used by the Aerovox Wireless Corporation to explain the advantage of a low resistance voltage divider over a high resistance device, i. e. the advantage of a voltage divider having a relatively high waste current. Tests were made with eliminators having a wide range of regulation curves and with voltage dividers having waste currents of 5, 10, 20 and 30 milliamperes. In all cases the calculated load was assumed to be 20 m.a. at 180 volts, 12 m.a. at 90 volts, and 2 m.a. at 45 volts. The results are tabulated herewith to show the voltage change produced at any tap by increasing or decreasing the load by 1 m.a.

I. 5 MIL VOLTAGE DIVIDER

Tap	45V.	90V.	180V.
45V.	4.25	1.85	negligible
90V.	2.20	3.98	1.88
180V.	0.53	1.40	1.25

II. 10 MIL VOLTAGE DIVIDER

Tap	45V.	90V.	180V.
45V.	3.02	1.37	negligible
90V.	1.53	2.95	1.30
180V.	.38	1.05	.87

III. 20 MIL VOLTAGE DIVIDER

Tap	45V.	90V.	180V.
45V.	2.05	.96	negligible
90V.	1.12	2.03	.93
180V.	.25	.73	.63

IV. 30 MIL VOLTAGE DIVIDER

Tap	45V.	90V.	180V.
45V.	1.75	0.56	negligible
90V.	.92	1.17	0.77
180V.	.21	.50	.50

Thus it is shown that an increase in the load resistance at the 45-volt tap of a 5 m.a. divider so as to produce a decrease of 1 m.a. at that tap, will cause

increases of 4.25 volts at the 45-volt tap, 2.2 volts at the 90-volt tap, and 0.53 volts at the 180-volt tap, as compared to 1.75, .92 and .21 volts respectively when using a 30 m.a. divider. A decrease in the load resistance to produce a 1 m.a. increase in current causes voltage drops of corresponding values. The 90-volt tap is evidently the most easily and greatly disturbed, and the 180-volt tap, which feeds without passing through the divider, the least disturbed by any change in the load. As the 45-volt tap is very sensitive to changes of load at 45 volts, many eliminators do not work satisfactorily when feeding a set which has a large 45-volt load, like a super-heterodyne.

It is evident that voltage variations due to variable loads may be minimized by using as heavy a waste current as possible. Furthermore the rise in voltage due to removing the load is thus minimized.

THE general theory of sound picture reproduction which was recently explained in these columns, was based upon the Vitaphone and Movietone systems, which record the sound waves on phonograph records, or film respectively, in the form of parallel lines. A third system was inadvertently omitted, this being known to the trade as the Photophone system. The latter is similar to the Movietone in that the sound waves are recorded photographically on the same film with the picture, but these waves are in the form of a single, jagged heavy line that looks like a cross-section of a mountain range. Its width varies in accordance with the frequencies recorded. A photoelectric cell and aperture somewhat like the Movietone system converts this solid black strip into sound, to be amplified and projected into the theatre by means of loud speakers.

Many of the latest types of motion picture projectors are equipped with special fittings so that any of the three systems of sound reproduction can be used by changing the aperture plates, projection lenses, and making minor adjustments requiring only a few minutes. The size of the picture on the Photophone film is somewhat smaller than for ordinary silent pictures, so as to allow a greater width for sound recording, but the picture is rectangular in shape instead of square as for the Movietone system shown in the September issue. This requires a different set of lenses, and a smaller aperture for the picture, but the change is quickly made, and hence no inconvenience is caused by the different systems. Probably the first radio movies which will eventually be made available to the general public will use this system.

AN exhaustive series of measurements of the amplification and selectivity of sixteen different types of r.f. coils, by Alfred J. Daniels of Aero Products,

Inc., shows that in the conventional r.f. circuit the most efficient practical type of those coils tested has its primary wound to occupy $\frac{1}{2}$ in. inside and opposite the low potential end of the secondary. But by means of a special circuit, herein described as the "Chronophase," still better results with screen-grid tubes were secured from an autotransformer whose primary is a portion of the secondary, the low potential ends being common.

All of the coils were of the type shown in Fig. 1, being air-spaced wound to approximately the ideal shape-factor

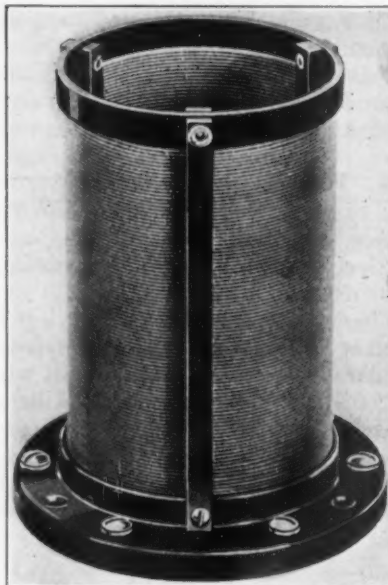


Fig. 1. Type of Coils Tested

and supported by a skeleton bakelite frame to minimize insulation losses. Each type had various numbers of primary turns and, where possible, was tested with variable coupling. The secondaries, measured independent of the primaries,

had an inductance of 167.4 microhenries and an r.f. resistance of from 3.85 ohms at 550 meters to 9.6 ohms at 200 meters. These figures are changed by the presence of a primary.

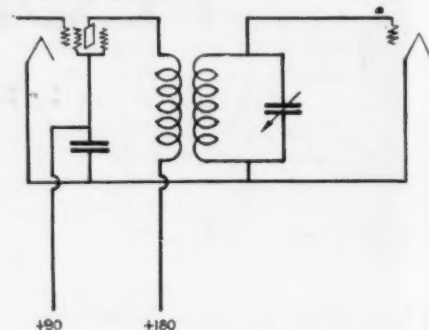


Fig. 3. a. R. F. Circuit Connections for Screen-Grid Tube with Conventional Transformers

The coils under test were supplied with a constant input signal at various frequencies in the broadcast spectrum, and the output was measured with a

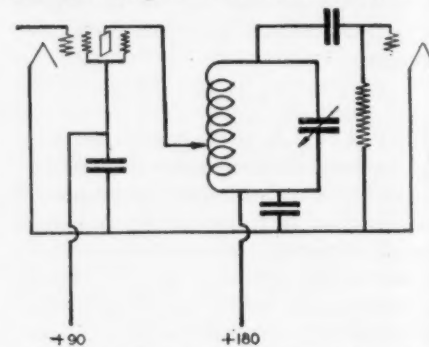


Fig. 3. b. R. F. Circuit Connections for Screen-Grid Tube with Autotransformer

vacuum tube voltmeter. The test conditions were nearly identical with those surrounding a coil in an actual receiver.

Fig. 2 shows the amplification curves obtained with the autotransformer and (Continued on Page 56)

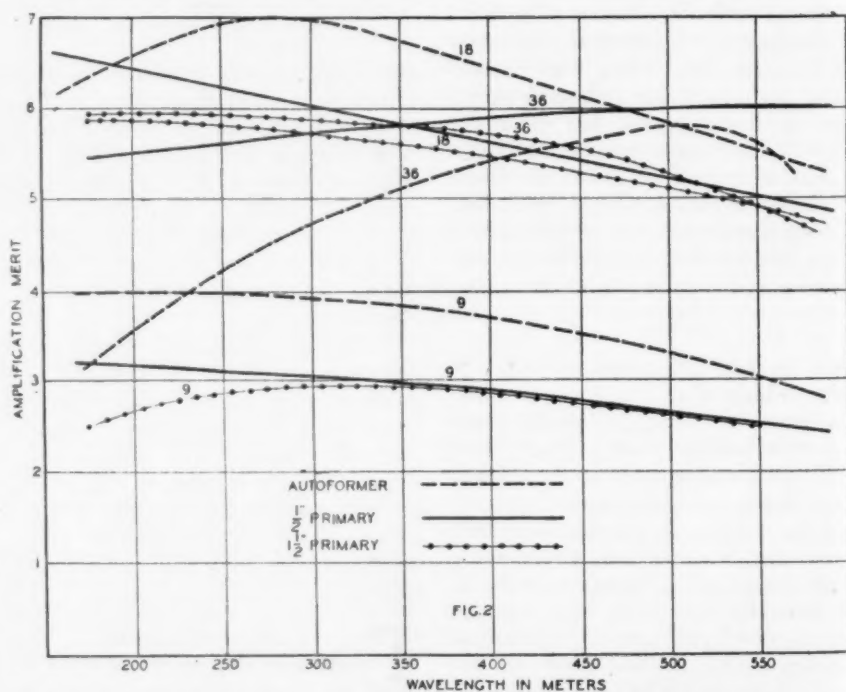


Fig. 2. Amplification Curves for Three Types of Coils with Varied Number of Turns



The COMMERCIAL BRASSPOUNDER

A Department
for the Operator
at Sea and Ashore



Edited by P. S. LUCAS
R. O. COOK, Assistant



A LETTER from Fred M. Winckel comments upon L. W. Gillis' article in June RADIO. Mr. Gillis, you remember, pointed out several reasons why radio operating conditions seem to be going from bad to worse, and made a few suggestions which might help remedy the situation.

Mr. Winckel believes that the only way to improve matters is to go right down to the bottom of things and attack the existing radio laws. No doubt he is right; but, as he goes on to say, the radio operator alone is not in a position to approach the radio commission or the senate committee on such a subject. He feels that the idea of an association of sea-going operators is still good, even if it has failed on several attempts. That is a subject that is always open for debate.

Even if we had an association of radio operators; even if we were solidly organized; where would it get us? Our strength would serve as a threat, but would the threat scare anyone into improving conditions for us? It would certainly antagonize the steamship companies, the radio companies and even the ill-informed public. "Radio operators imperil many lives." We can see the newspaper headlines—and the general public thinks we are having a lovely time of it.

No, radio operating is a profession, and strikes always belittle a profession. The world as a whole is drifting away from such methods of improving conditions; conditions are improving themselves. Employers are acquiring educations; they are learning, through the advancement of psychology, that it is to their advantage to show a little consideration to their employees.

We'll agree with you that our theorizing sounds very nice, but that it does *not* apply to our situation. Why? Are we so different from all other professions?

Well, here's our theory; and this is open to argument. We may be on the wrong track entirely. Anyway, it is our humble opinion that the great majority of operators take life too easily. It is difficult for a man to go onto a job, boss of his own time and unwatched by any authority, without falling into easy going habits. It is extremely difficult when the operator knows full well that he can do all that is required of him in three or four hours a day. If he can handle his job in four hours of concentrated effort, why shouldn't he do so? That's reasonable logic. But here's the reason why he shouldn't; the reason why he should find enough work to keep him busy for at least eight hours a day as regularly as any man on the crew.

The general impression is abroad that the wireless operator has an easy time of it. This starts with the other officers immediately associated with the op. It spreads to the crew, to the marine offices, to the higher officials. Not one man in a thousand gives the radio operator credit for doing a good day's work in all his existence. And here we have it. The officials require very little from an

operator; and pay him what the fulfillment of those requirements are worth to them. The operator works about as hard as he is paid for; the report gets out that the operator has an easy life; the officials—etc., etc. It goes around in circles.


Now what can we suggest as a remedy for this peculiar condition? In the first place the operator, every operator, must make up his mind to putting in a good, full eight-hour day. He should make out a schedule for himself and, figuratively speaking, "punch the clock." He should win the captain and the mates to his side by voluntarily giving them every available aid to navigation. He should insist that that is a part of his work and he is paid for doing it. (Fingers crossed). If the engineers ask for any aid on their generators he should jump at this opportunity of winning their friendship. While listening in for "roll-calls" and other signals he should not only keep his log up to date,

And one parting shot to the man who intends to take one trip or spend one year, then quit. You will get a whole lot more out of your trip or your year, you will have more to look back upon, and you will equip yourself for a more successful future if you will play the game as if it were to be your life's work. While you are in it feel yourself a part of our development program. Men, it's up to you.

A PRACTICAL "B" ELIMINATOR FOR SHIP USE

By R. M. HUGHES

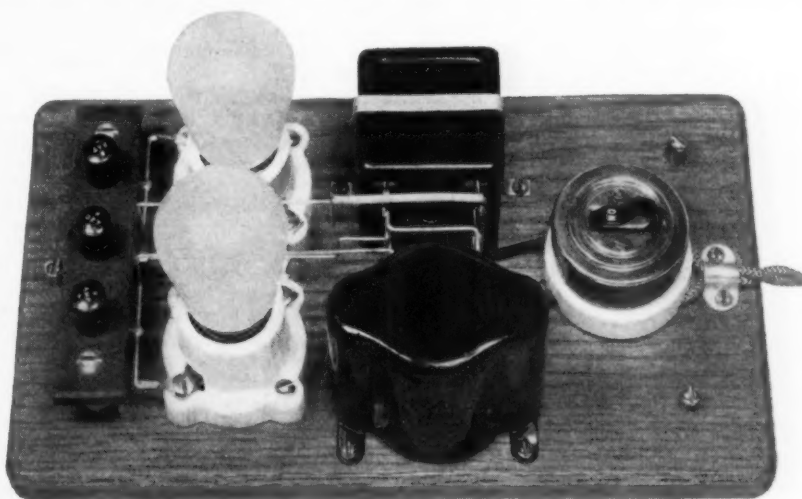Many sea captains, as well as mates, engineers and radio operators, have their own broadcast receivers aboard ship. Yet few of them use a B eliminator, although there is no place where local conditions are better suited for its use. The ship dynamo supplies



"B" Eliminator for D.C. Supply

but file away in his head, every bit of information possible so that if anyone asks him any questions he might be able to give the impression that he is well informed. In brief, he must consider his job more important than his officials consider it, and organize it accordingly. How long, under such conditions, would it take for a vastly different sort of "underground telegraph" message to be buzzing in the ears of the officials?

This should be the one great object of an organization: to so enthruse the mass of operators with the possibilities of improving conditions ashore and afloat that they will carry out the suggestions just made. Let the organization be formed to promote the member's interest in his work. Every operator must feel his responsibility in this matter or the situation will be worse twenty years from now than it is today.


direct current at about 110 volts. This contains a commutator ripple which must be filtered out before it is suitable for use as the plate supply for a radio set.

All that is needed to make the satisfactory battery eliminator shown in the picture and circuit diagram herewith, can be bought at a chain store for less than four dollars, or for slightly more if purchased from a regular dealer in radio parts. This equipment can be quickly and easily assembled on a baseboard and will furnish hum-free current at 45 and 90 volts.

An ordinary snap-switch is used to turn the current on and off. The choke coil has an inductance of about 20 henries. Each of the three condensers has a capacity of 1 mfd. and should withstand 200 volts. The voltage dividing circuit consists of two 2 c.p. lamps connected in series, one being connected di-

rectly to the negative side of the ship's generator and other through the choke coil to the positive side of the line. The center tap gives 45 volts.

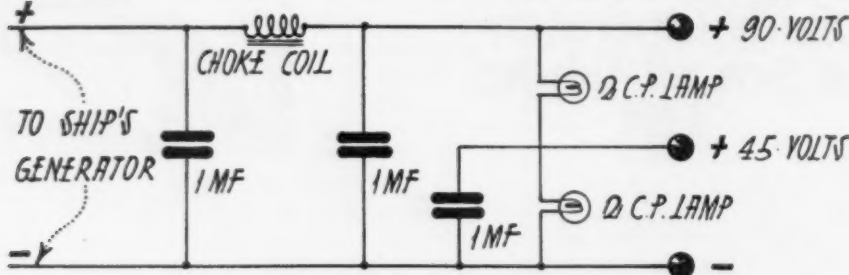As a ship's power system is not grounded, a necessary precaution requires a 2 mfd. condenser in the ground-lead of the receiver. This does not interfere with the receiver's r.f. ground, but does prevent shorting the ship generator.



Circuit Diagram for Eliminator

All of the parts can be assembled on a baseboard 6 by 10 by $\frac{5}{8}$ in. The condensers can be stacked on top of one another and held in place by a small strip of brass. This device has proven to be satisfactory with many different receivers in many locations.

TRANSLATION OF ESSENTIAL WORDS USED IN XDA WEATHER

By PAUL OTTO

Several operators have asked me where I got the impression that XDA weather is easy to translate! Here is a list of twenty words that chiefly constitute the construction of these weather reports. Of the twenty, there are only eight whose meaning in English is not self-evident. Judge them for yourself.

From experience I have found that the weather contained in the number groups, from coast towns, is the most desired.

In the first group the first three figures are the barometer in centimeters. The fourth is the wind direction, and the fifth the wind force. In the second group the first figure is the state of the weather, and the third is the sky report. These figures can be very easily decoded by referring to a copy of "Radio Aids to Navigation," which can be purchased for seventy-five cents at any store that carries hydrographic publications.

Here are the words:

ENGLISH	SPANISH
Somewhat	Algo
Lower	Baja
Cape	Cabo
Coast	Costa
Of	De
Light	Debil
Of the	Del
The	El, or La
East	Este
Strong	Fuerte
Gulf	Golfo
As far as, or to	Hasta
Moderate	Moderado
Very	Muy
North	Norte
West	Occidental, or Occ.
East	Oeste
Shifting, or changing	Rolando
South	Sur
Winds	Vientos
Northeast	Noreste
Northwest	Noroeste
Southeast	Sureste
Southwest	Suroeste

CCA, ANTOFAGASTA, CHILI

By CHARLES F. STEWART

Having read pleas for South American material in the Commercial Brasspounder, I decided to take advantage of a stop-over in Antofagasta last May to check up on Station CCA.

CCA is a naval station and handles Gov-

ernment business only, on 1800 and 2800 meters. It is intended, however, to install a 600-meter spark, with which to handle commercial ship to shore traffic. Perhaps this service has already been inaugurated.

I was cordially met by the chief operator of CCA, Mr. Stienbacher, who kindly showed me the installation and later introduced me about the town, even throwing a party for me. He told me that I was the first American operator he had met and asked that I extend the invitation to any other operators who might come to Antofagasta, which I hereby do. Take him up if you ever drop your hook in Antofagasta; you will not be sorry.

Now for the station: CCA is housed in a three-story building. Mr. Stienbacher and family live on the first floor where the power supply is also located. On the second floor are the living quarters of the three assistant operators, while on the third floor are the receiving apparatus, control room and land line.

There are two receivers, one Marconi, the other made by Telefunken. The transmitter is on the ground floor near the generators, and is a 10 kw Marconi outfit, with 10 1 kw tubes. The transmitter occupies a room to itself and is surrounded by a brass rail, only the tubes and rheostats being mounted on a panel.

Although the soil is extremely dry a ground is used for transmission and reception. I asked Mr. Stienbacher about the possibilities of a counterpoise, but he had never heard of one and was quite interested when I explained it to him. A Marconi engineer made the installation and I cannot understand why he didn't install a counterpoise.

The Chilean Navy was experimenting with short waves at that time, and was sending its operators small booklets on that subject. It might be well to mention that all stations in Chili are under the control of either the Chilean Army or Navy. The Navy maintains a school in Valparaiso, where its operators are trained. English equipment predominates, although a few Telefunken tubes and receivers are used.

To listen to a Chilean coast station handling commercial traffic you would think the operators and equipment very poor, but the stations handling government traffic have first-class equipment and operators. Only men with a high rating are used for this type of service. It is easier to understand this when it is known that the Chileans believe the Army and Navy to be the most important elements of their country's organization.

Mr. Stienbacher speaks excellent English and is very anxious to get acquainted with American operators. As we said before, if you want to be well received, drop in on CCA.


AN EASILY CONSTRUCTED BREAK-IN

By J. A. BENDER, S. S. West Cactus

A LOT of fine machine work can be put in on a break-in, but when the all-important consideration is cash there is just one item, outside of efficiency, to be discussed, and that is simplicity. Therefore, if you are interested, read about the one you can make out of parts retrieved from your junk-box.

Delve into the aforementioned curio shop and bring out the following trinkets:

- 1 piece of bakelite panel 5"x3".
- 1 piece of bakelite strip 3"x $\frac{1}{2}$ ".
- 1 piece of heavy brass strip 3"x $\frac{1}{2}$ ".
- 1 piece of heavy brass strip 1 $\frac{1}{2}$ "x $\frac{1}{2}$ ".
- 1 piece of spring brass strip 2"x $\frac{1}{2}$ ".
- 2 binding posts.
- 1 8/32 screw about 2" long with nut.
- 1 brass bushing about $\frac{1}{2}$ " long, tapped on one end to an 8/32 thread and on the other end to same thread as on the key contacts named below.
- 1 piece of brass bushing about $\frac{1}{4}$ " long tapped 8/32 thread for key stop.
- 2 key contacts.

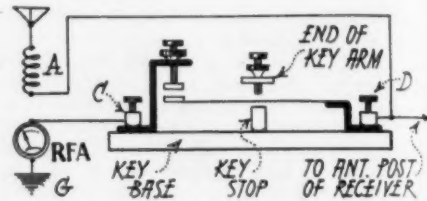

View of the After End of the Key Base

First, mount the key on the piece of panel so that about 3 in. of the base extends out in back of the key proper.

Second, drill three holes in the panel about $\frac{1}{4}$ in. from the end; the two outer holes being about $\frac{1}{8}$ in. from the edges of the panel and the center hole in line with the adjusting screw of the key proper. All the holes must be in line.

Third, take the brass $\frac{1}{4}$ in. bushing and screw it into the center hole.

Fourth, take the piece of strip bakelite and drill a hole in each end, tapping one hole with the same thread as the adjusting screw on the key. Remove the back adjusting screw from the key arm and bolt the bakelite strip to the arm, using the hole from which the screw was taken. Now screw the adjustment screw into the tapped hole of the bakelite strip.

Fifth, drill and tap one hole on the long strip of brass and bend the strip to right-angles about $\frac{3}{4}$ in. from the end, using an 8/32 tap to tap the hole.

Sixth, drill a hole in the other end and bend in the opposite way about $\frac{1}{4}$ in. from the end. Screw the long 8/32 in. screw into the tapped hole, leaving the nut on the screw, and screw the key contact to it, using the $\frac{1}{2}$ in. bushing. Now take the finished piece and bolt to one side of the panel, using a binding post.

Seventh, take the brass spring, drill a hole in each end and screw the other key contact to it. Take the short brass strip and drill a hole in each end, then bend it at right-angles about $\frac{1}{2}$ in. back from each end, reversing directions. Bolt the spring to the strip and bolt the whole thing to the panel.

Eighth, replace the arm of the key and you have the break-in completed. Not much to look at, but it surely does the work.

In hooking up the break-in, disconnect the transmitter from the r.f. ammeter, at A. Run a lead from the ammeter to the binding post C on the break-in. Run a lead from the binding post D to the antenna binding post on the receiver, also to the transmitter at A.

(Continued on Page 48)

With the Amateur Operators

AN ALL-SHORT-WAVE RECEIVER

By A. BINNEWEG, JR.

UNLESS particular attention is given to station design for 1929 conditions, amateurs may have difficulty in working at the higher frequencies. The experimenter will use the 10-meter and 5-meter bands with reflectors. Those who will use the 20 and 40-meter bands must use special care and apparatus.

The usual 40 and 20-meter receiver will not also operate at 5 and 10 meters, as the parts are too large. To satisfy 1929 requirements, the set must tune sharply over a narrow band, which means that midget condensers will be used. Many amateurs will leave the narrow bands and experiment with the much wider 10-meter one which has exceptional possibilities. The writer has developed a receiver which covers efficiently the 5 and 10-meter bands and meets the 1929 requirements for the 20 and 40-meter ones.

The receiver is constructed in two sections: a two-stage screen grid amplifier in one and a regenerative detector and two-stage audio amplifier in the other. The r.f. amplifier section is especially useful for the higher frequencies as the amplification falls off. It may be added to any short-wave receiver. By proper circuit design and parts placement, it is possible to operate the amplifier without any great amount of skidding, a grounded copper sheet between the two tubes usually being sufficient to prevent oscillation at 5 and 10 meters. Fig. 1 shows the complete circuit diagram.

The r.f. amplifier coils must be of small diameter to limit the field and minimize inductive feed-back. For 40 meters, 2-in. coils with 12 turns are about right, and at 20 meters 4 turns will do, the exact size depending upon the range of the tuning condensers. The antenna coil and its associated secondary are mounted on a 3 by 4-in. piece of bakelite placed directly below the condenser so that the wiring is short and direct. The plate coil of the first stage is mounted in a similar manner. A 10 by 11-in. baseboard provides ample space between the parts.

Separate batteries can be used for each stage. Separate binding posts are provided for each A and B battery supply and two posts are left free for the leads of the output coupling coil.

Filament current for each r.f. amplifier stage is supplied through two rheostats connected in series. One is variable for filament regulation. The other is fixed as regards

filament voltage, but is adjustable so as to give the best grid-bias. This bias adjustment is secured through a lead from the movable arm to a separate post. The four rheostats and binding posts are mounted on a 4 by 11-in. piece of bakelite, which is separated above the baseboard by two wooden uprights.

The second r.f. stage requires a .0002 mfd. grid condenser and 1 or 2 meg. leak. This amplifier will operate well at 40 meters without by-pass condensers. For shorter wave work .002 or .003 mfd. will serve.

The clips for the control grids consist of trimmed fahnestock clips to which the leads are soldered.


The main panel measures 7 by 12 in. and shows two 100-degree dials and a filament switch between. The ground post is mounted on the small panel, with the antenna coil, which is fitted with a strip of bakelite and

a G. R. plug; this rotates in a jack which can change the coupling. A flexible lead to the antenna coil connects to the antenna post at the rear of the set. The small panels supporting the plug-in coils are fastened to wooden supports and clear the baseboard about 1/2 in.

The tuning of the amplifier is not sharp at any frequency so that one can tune somewhere near the band, and the receiver is then the usual two-control affair. The input tuned-circuit to the amplifier has the most effect on the overall amplification.

The construction of the regenerative detector and audio section is almost self-evident from the circuit diagram and picture.

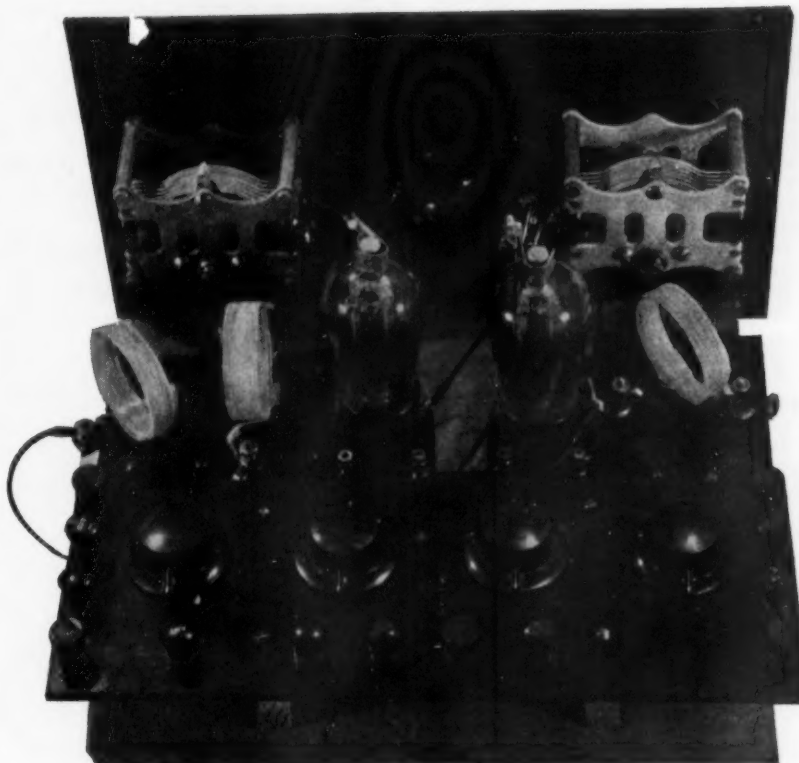For reception at 5 meters, both 100 pfd. midget shunt condensers are set at minimum, the 2-turn secondary is used, and tuning is as easy as usual. The shunt condensers are adjusted for a certain minimum capacity which is desirable in the secondary circuit,



Short-Wave R.F. Amplifier with Screen-Grid Tubes

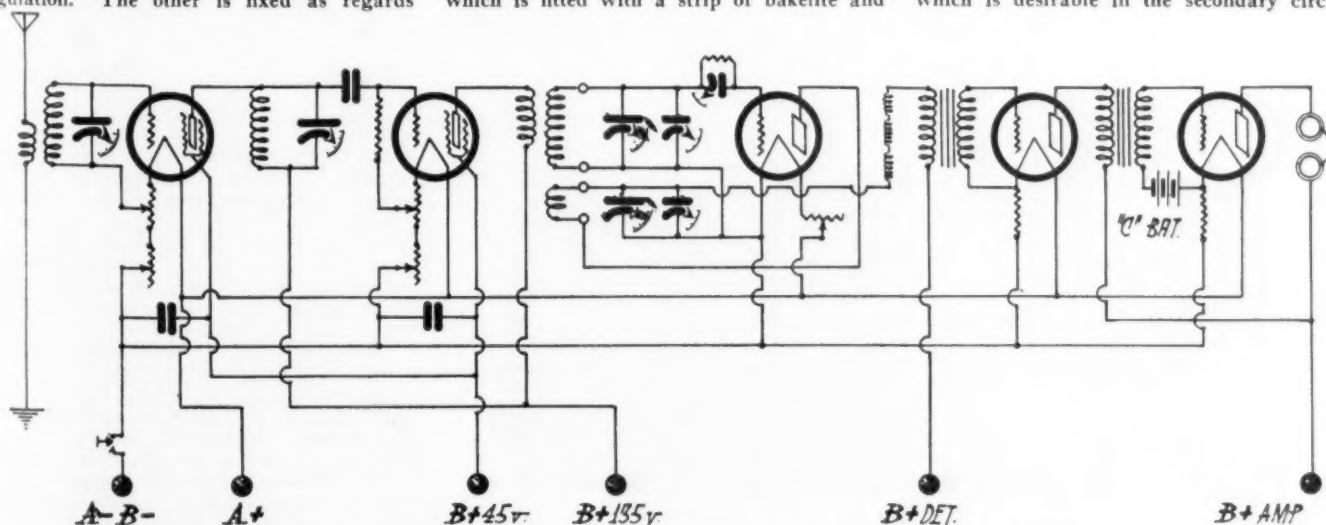


Fig. 1. Circuit Diagram for All-Short-Wave Receiver with Screen-Grid R.F. Amplifier

for the throttle-control has a large detuning effect when the total secondary capacity is near that of the tube capacities.

To operate at 10 meters, simply plug in the next coil and listen anywhere between 5 and 10 meters. The secondary shunt condenser is used to shift to a new band.

To operate at 20 or 40 meters, a large inductance can be used, or else the shunt condenser can be set somewhere near maximum and a smaller coil employed.

It is interesting to compare receiving conditions with the different LC ratios possible. Any size of inductance, within reason, is all right, as adjustment is made with the shunt condenser. When the proper position is once located, the knob-setting is noted, and rapid wave-changing is then possible. It certainly is a relief to have a receiver which will operate efficiently at the lower wavelengths also.

For 5 and 10 meters, the plug-in coils are self-supporting and are mounted in '99 bases; for 20 and 40 meters, the larger bases may be used with the coils wound directly on them.

If desired, celluloid-supported coils may be mounted horizontally on these bases. A good tube socket should be used for the plug-in coils; by a simple test, at even 10 meters, the capacity between the socket terminals (and what little wiring there is) alone, is sufficient so that the operation of one condenser has some effect on the other. The socket is mounted on a block between the condensers and the leads are thus short.

The throttle-control is a 100 pfd. midget which is sufficient for the shorter wave-bands. For the higher wave-bands, the other 100 pfd. midget, shunt condenser, is utilized and the receiver can thus cover a very large range without changing coils. It is important to adjust the tickler so that good regeneration-control is secured with the condenser near a maximum setting, so that detuning of the secondary circuit will be negligible.

The midgets are mounted on small brass angles; some midgets already have these. Extension handles are used, which allows efficient reception at the highest frequencies without any body effects. A half-inch wooden panel, screwed to two uprights, to which the sub-panel is screwed, makes a sturdy set. To properly center the extension handles, the condensers are first mounted in place and the handles extended to the panel, which is then marked and drilled. Large holes are drilled half way through the panel for the vernier-dial screws, and smaller ones the rest of the way. Often the advantage of a good vernier dial is lost by motion at the bottom; if two brass wood screws fitted with washers are used to hold it here, no trouble will be had. A small dial or knob is used on the regeneration control.


A good choke, which will cover the 5 and 10-meter bands also, consists of several small windings in series on a 1/4-in. dowel; these windings consist of 20, 40, 60, 80 and 100 turns, bunch-wound, and are spaced about 1/4-in. apart. Basket-weave coils may be used if desired.

LIST OF PARTS FOR ALL SHORT-WAVE RECEIVER


- 4 100-mmfd. Midget variable condensers
- 1 15-mmfd. Midget variable condenser
- Tube bases for coils
- 2 sockets for amplifier tubes.
- 5-meg. grid leak
- 1 filament switch
- 1 detector rheostat
- 112 detector tube
- 2 amplifying tubes
- 2 peaked audio amplifying transformers
- 2 fixed filament resistors
- 2 extension handles
- Wire for coils (No. 12 and No. 20); wire for chokes (No. 36), bakelite (7 by 12 and 7 by 7 suggested); baseboard and uprights, screws for same, etc.

The capacity of the grid condenser has considerable effect on the operation of a receiver of this type. If too large, considerable effect of one control on the other occurs through the tube capacities. For "all-wave" use, it is preferable to use a variable condenser so that best values may be selected in different bands. A midget having a maximum of 100 pfd. gives good results. At 5 and 10 meters, this condenser is turned down

(Continued on Page 52)

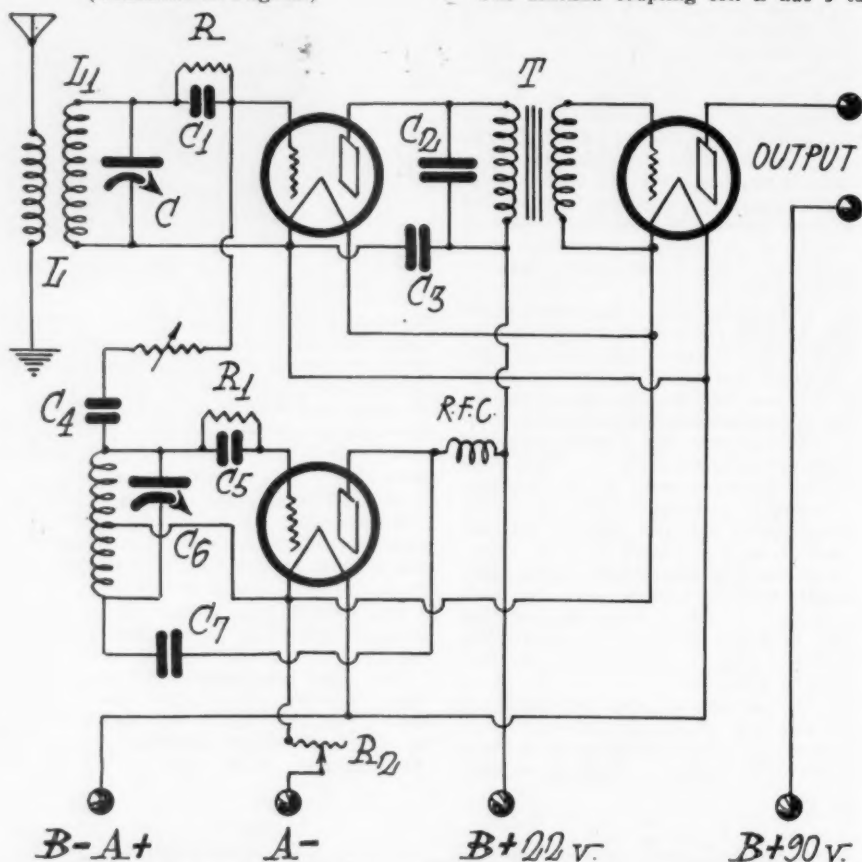

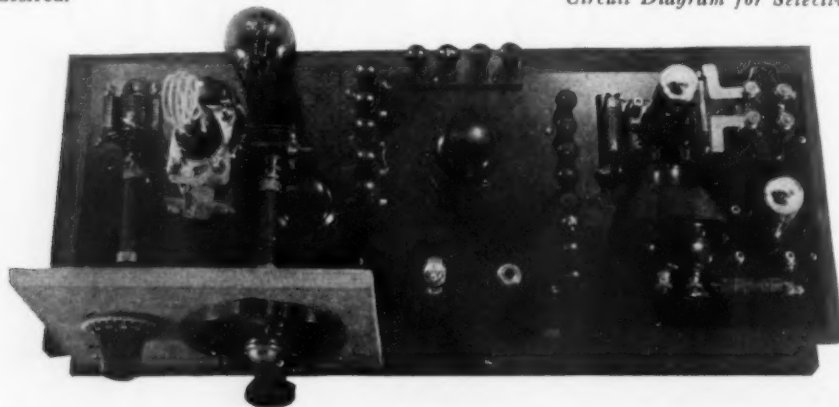Circuit Diagram for Selective Short-Wave Receiver with Oscillator



All-Short-Wave Receiver

A SELECTIVE SHORT-WAVE RECEIVER

By R. WM. TANNER

The selectivity of the usual regenerative short-wave receiver can be greatly improved by adding a Hartley oscillator and removing the tickler coil as shown in the accompanying circuit diagram. The oscillator control has no tuning effect on the detector. The pitch of the signal is not changed when the secondary condenser is varied after a signal is tuned in. This is in marked contrast to the detuning of the grid or secondary circuit which occurs when the tickler is varied in the usual form of regenerative receiver. If the tickler coil is retained when the oscillator is added, greater sensitivity is possible, but another control is added thereby.

While complete shielding is desirable, it is not necessary if the oscillator harmonics are used to produce beats. A slight rushing noise is heard when one of the harmonics crosses the wave of the detector. Although this set is a little harder to tune than a straight regenerative receiver, the results are more than worth it. R1 is a 1 megohm clarostat used in place of a pick-up coil.

The antenna coupling coil L has 5 turns

of No. 18 enamel wire and may well be variable so that close coupling can be used on weak signals and loose coupling on strong signals. The secondary plug-in coils L2 are space-wound with No. 18 enamel wire on a 3-in. form. They have 19, 8 and 3 turns respectively for the 80, 40 and 20-meter bands, being tuned by a .00014 mfd. condenser C. The detector grid condenser C1 is .00015 mfd. and the grid leak R 6 megohms.

The oscillator coil L2 has a wavelength range of about 180 to 400 meters when tuned with a .00025 mfd. condenser C2. A high ratio vernier dial must be used on this condenser. The coil consists of 50 turns of No. 26 d.c.c. wire on a 3 1/2-in. bakelite form, with a filament connection tap at the 25th turn.

(Continued on Page 54)

Inside Stories of Factory Built Receivers

III. Freshman Model Q-15

THIS is the first factory-built a.c. receiver to use a screen-grid tube as an r.f. amplifier. The other tubes in this four-tube set are a '27 tube as a detector, a '26 tube as a first audio amplifier, and a '71 tube in the second audio stage. Filament current at 3.1, 2.25, 1.4, and 4.8 volts, respectively, is supplied through a stepdown multiple-tapped transformer from a 110-volt a.c. source. Plate voltages are supplied through a full-wave

and sensitivity, a volume control, wherein a rheostat varies the antenna current, and an "on-and-off" switch. It uses an outside antenna and ground.

The tuning condenser and power plant are in separately shielded compartments. The screen-grid tube is also shielded.

The r.f. amplification from the screen-grid tube and its associated transformer is claimed to be from 25 to 40, despite the limitations

to more than compensate for the slight reduction in shield-grid tube gain. This is automatically maintained well below the oscillating point so as to avoid distortion.

Most of the circuit constants for the receiver and power plant are shown in the accompanying circuit diagram. The general construction and arrangement of the chassis may be seen in the picture thereof.


NEW RADIO CATALOGS

Radio Insulators of all types are illustrated and described in a pamphlet from Knox Porcelain Corp., Knoxville, Tenn., which also shows such antenna accessories as wire, lead-ins, and lightning arresters.

A new bulletin on socket power condensers from the Dubilier Condenser Corporation of New York City shows a complete line of paper dielectric condenser blocks as designed for use with various standard transformers. Dry "A" 2000 mfd. condensers are also listed and described.

Publication No. 84 from the U. S. Bureau of Standards is a Standard Time Conversion Chart which gives a direct reading for the standard time at any desired longitude corresponding to the time at a given place. The chart is printed on heavy Bristol board and consists of two concentric circles, one of which can be revolved. This can be secured from the U. S. Government Printing Office for ten cents.

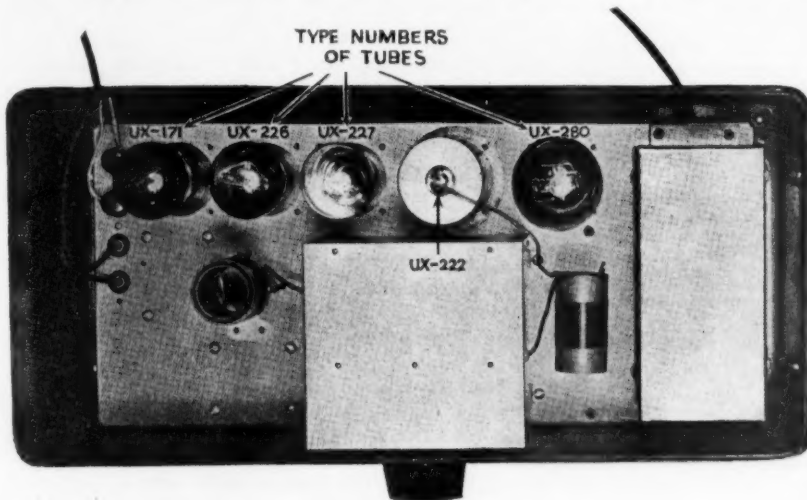Scientific Paper No. 568 from the U. S. Bureau of Standards contains "Methods, Formulas and Tables for the Calculation of Antenna Capacity," by Frederick W. Grover. This information is of value to an amateur transmitter who is designing an antenna system whose fundamental wavelength he desires to know.




Freshman Model Q-15 Chassis

rectifier-filter system using an '80 tube. The entire receiver, including the power supply equipment, is compactly assembled on a steel chassis.

The set has four controls: a 190 to 570 meter tuning dial which operates a two-gang .00036 mfd. condenser, a vernier .00004 mfd. condenser which adjusts for fine selectivity

imposed by operating the filament on raw a.c. Such amplification is as good or better than is secured with the usual two stages of r.f. amplification. One of the secrets of its performance is the use of a high grid bias to prevent a.c. modulation.

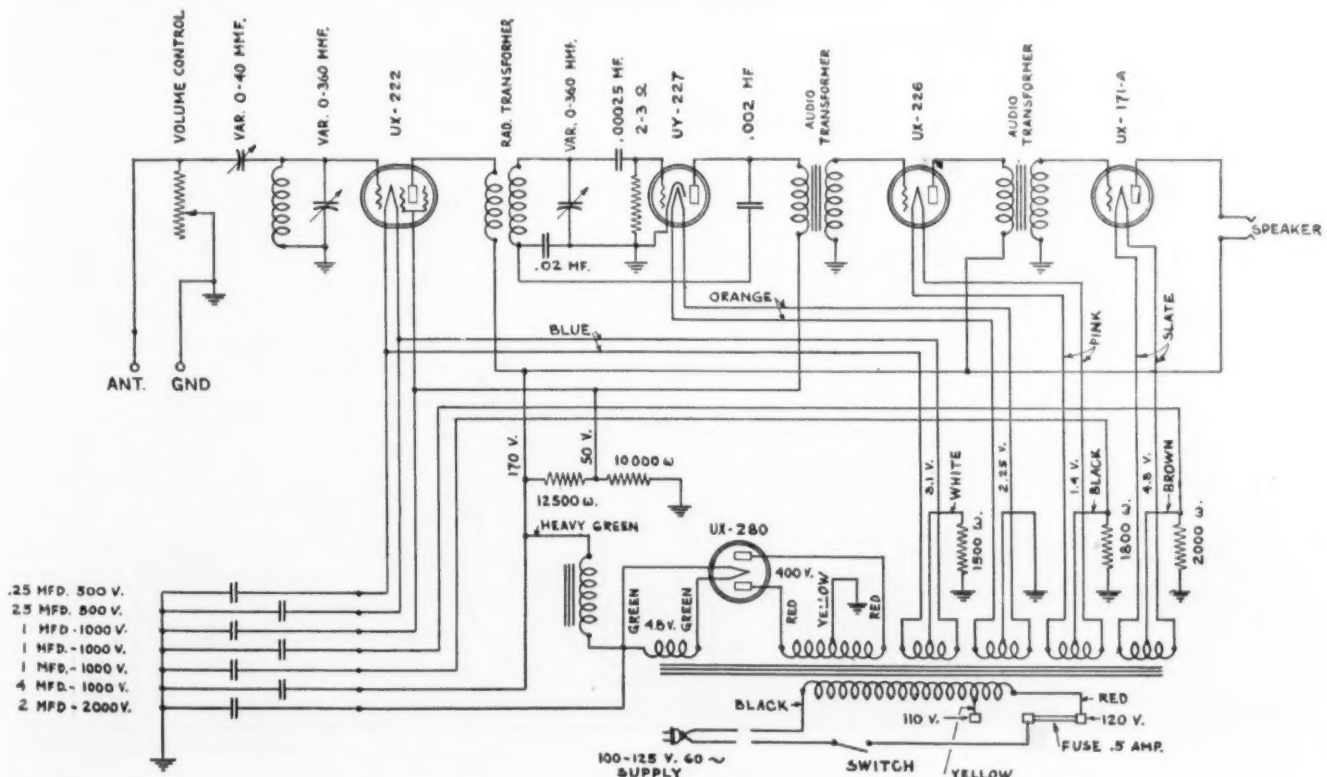A small amount of regeneration is ingeniously introduced into the detector circuit



Circuit Diagram of Freshman Model Q-15 Receiver

Radio Kit Reviews

HFL MODEL 10 ISOTONE

THE HFL Model 10 Isotone is a standard screen-grid superheterodyne, utilizing nine d.c. tubes as a radio receiver, with a tenth tube available as an extra stage of audio amplification for phonograph reproduction. It incorporates several new features, including a radiophone control switch on the panel. When this switch is turned to the phonograph side the oscillator, detectors and i.f. amplifiers are completely disconnected from the circuit, leaving three stages of a.f. amplification with '12A tubes for the first two stages and two '71As in push-pull for the third. This a.f. amplifier may be used in connection with any external detector, short wave or broadcast, by plugging the latter into the tip jacks designed for the phono-

is shunted across each of the larger .0001 secondary condensers, allowing each i.f. circuit to be separately tuned. This compensates for variations in the internal capacities of the tubes, making it possible to maintain the utmost selectivity of the amplifier at all times. The sensitivity of the i.f. amplifier is controlled by variation of the voltage applied to the screen grid. Each stage is said to have a radio-frequency gain of 65.

In the tuning unit a small trimmer condenser, shunted across the oscillator coils, makes it possible to adjust the oscillator and antenna tuning dials so that they read alike. In balancing the instrument for best results it is necessary to leave all the shield cans covered with the exception of the one to be balanced. Once the intermediate amplifier is balanced it should be left that way until such

to a metal sub-base drilled for speedy mounting. Six bakelite strips protrude through the bottom of the base pan and the terminals thereon are easily hooked up with nickel-plated connecting strips. The whole job of assembly can be done in less than an hour; each unit fitted into place and made fast, bottom connecting strips screwed on, panel and knobs mounted on front, tubes put into their sockets and covered with the individual shield cans. The panel is 7 x 26 in. in size, of walnut grained Micarta.


The manufacturers of the HFL Isotone have also designed a power pack which furnishes all of the required voltages to the receiver. This is sold completely assembled and wired and provides the following currents and voltages: *A* current, 2½ amperes at 6 volts; *C* voltages variable 0-15 and fixed 45 volts; *B* voltages 45 (variable 0-90), 135 and 180 volts. There is a variable resistor in the *A* supply circuit which allows the filament voltage to be increased or decreased. Oversize condenser sections and heavy chokes eliminate all tendency toward motor boating and voltage fluctuation. The instrument uses dry rectifiers and condensers throughout and the plate current is furnished by means of a 280 rectifier tube.

When using the power pack on the a.f. amplifier alone, i.e., on phonograph reproduction, with the filaments of the six unused tubes turned off, it was found necessary to use a compensating resistance. This is incorporated in the set.

The parts in the kit are:

1 HFL Isotone assembled and wired tuning unit, 1 HFL Isotone assembled and wired screen grid amplifier, 1 HFL Isotone assembled and wired audio amplifier, 8 HFL Isotone shield cans with tops, 1 base assembly plate, 1 drilled and engraved front panel, 1 seven-wire cable and plug, 2 gold escutcheons with knobs (attached), 2 dial lights (inside of drums), 2 large walnut control knobs, 1 small walnut switch knob, 2 steel panel supporting brackets, 12 plate connecting strips, 55 6/32 hexagon brass nuts, 14 ¾ in. hexagon spacer studs, 14 ¾ in. by 6/32 R.H. machine screws, 6 ¼ in. by 6/32 F.H. black machine screws, 4 ¾ in. by 6/32 R.H. machine screws, 11 tinned copper lugs, 6 ft. push-back wire.

(Continued on Page 58)

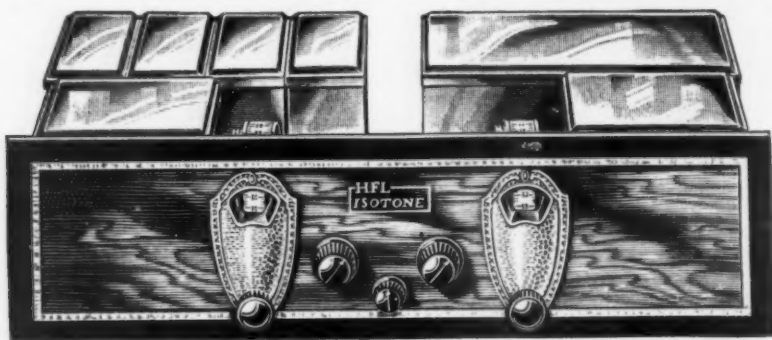

HFL Model 10 Isotone


graph pickup. When the switch is turned to "radio" one stage of audio is disconnected, and the other tubes thrown back into the circuit.

Either a loop or an outside antenna may be used. In the case of the latter, the phone tips hanging from the antenna coupler are plugged into the tip jacks marked for the loop. The oscillator and first detector use '01A tubes, the three i.f. stages use '22 type, the second detector and first two stages of a.f. use '12A type, and the last stage of push-pull audio '71A tubes.


The i.f. transformers are peaked at 450 k.c. so as to give one-spot tuning. It will be noticed that a 25 mmf variable condenser

time as any of the screen grid tubes have to be replaced. The only remaining variable control is the small trimmer condenser in the antenna tuning stage. This is non-critical in adjustment and does not usually have to be touched. It is possible, however, to make the receiver oscillate by tightening this condenser. All units are thoroughly shielded.

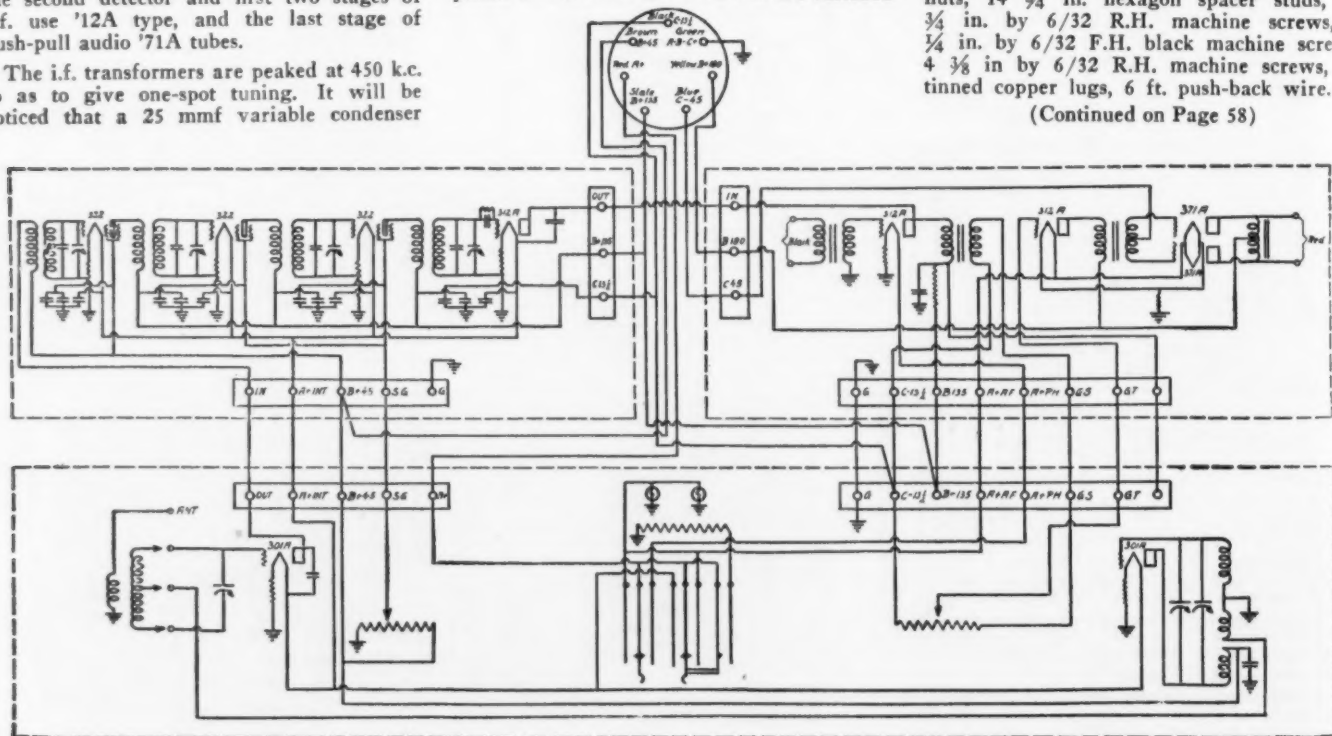The kit comes in four parts; namely the base pan, the front control unit, the i.f. amplifier unit and the a.f. unit. All are fastened



Circuit Diagram of HFL Model 10 Isotone

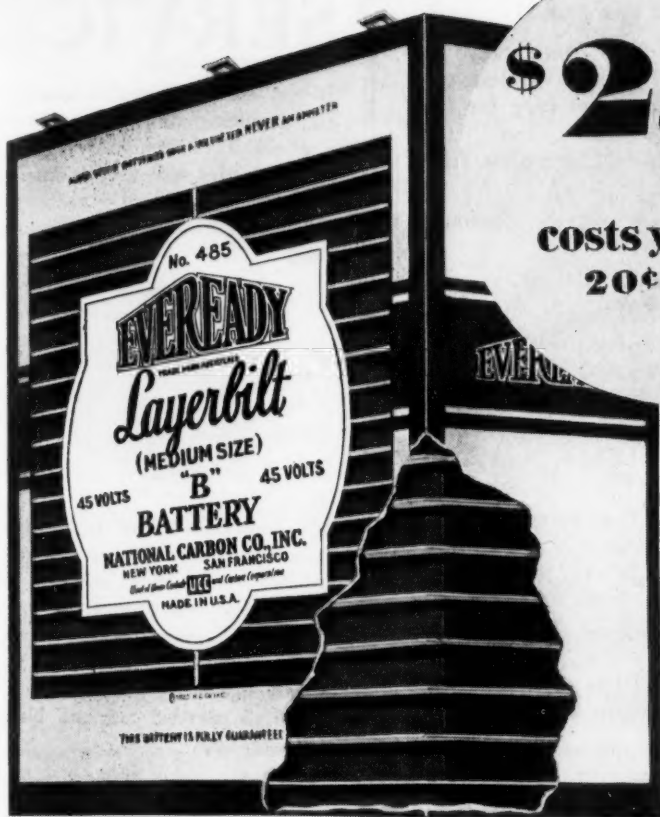


\$2.95
costs you only
20¢ more

This is the Medium Size Eveready Layerbilt "B" Battery No. 485. 3 1/4 inches thick. 45 volts, \$2.95.

If you use the medium size, you can buy the Eveready Medium Size "B" Battery No. 772, for \$2.75. It's a fine battery of its type—cylindrical cell. BUT, just add 20 cents to your price, and get the Eveready Layerbilt Medium Size "B" Battery No. 485. Same outside size as the older battery, but more active materials inside, and so you buy 25% longer life with your 20 extra cents. Another great battery bargain!

Both these Eveready Layerbilts are made of flat cells that fill all available space inside the battery case. This construction avoids the useless waste spaces between the cells of the older, cylindrical cell type of battery, and eliminates soldered connections between cells. The truly modern "B" battery is the Eveready Layerbilt. These two batteries, exclusive with Eveready, are longer lasting and more economical. Look for the name Layerbilt on the label.

NATIONAL CARBON COMPANY, INC.
New York  San Francisco

Unit of Union Carbide and Carbon Corporation

**Never was so much
extra service
bought for so
few extra cents**

**EVEREADY
Radio Batteries**

Layerbilt construction is a patented Eveready feature. Only Eveready makes Layerbilt Batteries.

**TUESDAY NIGHT
IS EVEREADY HOUR NIGHT**
East of the Rockies, 9 P. M. Eastern Standard Time, through WEAF and associated N. B. C. stations. On the Pacific Coast, 8 P. M. Pacific Standard Time, through N. B. C. Pacific Coast network.

YOU are a "B" battery user. You are most probably interested in one of two popular sizes. You use, in the majority of cases, either the heavy duty size, or the medium size. If you use the heavy duty "B" batteries, which is the most economical thing to do, you can get the Heavy Duty Eveready No. 770, which contains cylindrical cells, for \$4.00. BUT for only 25 cents more you can have the famous Eveready Layerbilt No. 486, which is the same size, outside, but which contains more active materials, and lasts 30% longer. For your extra quarter you get from a quarter to nearly a third more service. Never before did 25 cents buy so much battery service!

This is the famous original Eveready Layerbilt "B" Battery No. 486. The longest lasting of all Evereadys. 4 7/16 inches thick. 45 volts, \$4.25.

\$4.25
costs you only
25¢ more



SEE AND HEAR THE NEW EVEREADY RADIO SETS

Tell them you saw it in RADIO



Look for the



on top of all

Cunningham
RADIO TUBES

WHEN you look inside of your radio, be sure you see the monogram "C" smiling up at you on the top of each radio tube.

Thirteen years of experience and tireless research combined with a guarantee against mechanical and electrical defect stand behind this simple monogram.

Cunningham Tube quality has resulted in national leadership and public approval, two assets we zealously guard, and is your assurance of faultless modern reception.

Never use old tubes
with new ones—use
new tubes throughout

E. T. CUNNINGHAM, INC.
New York Chicago
San Francisco

Manufactured and sold under rights, patents
and inventions owned and/or controlled by
Radio Corporation of America.

Cunningham
RADIO TUBES

RADIO AIDS AIR RACES

(Continued from Page 30)

Here they come! There they go! Zoom! Zoom! That was a close one. He didn't miss the pylon very far that time! And we're inside, too. Here comes one that whines like a siren. After it passes, an observer calls:

"Operator! Plane number 159 fouled pylon! Sixth lap."

The operator grabs the key.

"6EMF 6EMF 6—"

He doesn't complete the third set of call letters before headquarters station, 6EMF, answers, using the "break-in" system.

"6EMI DE 6EMF GA (Go ahead)," says 6EMF.

6EMI: "QFP (Foul pylon) NR 159 SIXTH LAP K."

6EMF answers: "OK QRX." (O. K., stand by.)

In a few seconds come the signals from 6EMF again: "6EMI DE 6EMF NR 159 DISQUALIFIED AND SIGNALLED QSU (Will call you later.)"

The whole operation hardly took over thirty seconds! Before the plane could reach the field, flying well over 100 miles an hour, the judges knew what had happened at Pylon Number 3. Plane Number 159 is flagged out and is saved from going around several useless laps.

Even more important than "QFP" was QRR. This signal in amateur radio corresponds to the "SOS" of commercial radio. At the air races it was used as the signal for a crash, and we are glad to say that its use was seldom required.

One day, a plane failed to appear at Pylon Number 3 after three laps. 6EMI advised 6EMF, and the latter made an immediate investigation. It was found that the plane had completed three laps at Pylons 1 and 3, and had passed Pylon Number 2 on its fourth lap. The plane was therefore between 2 and 3. A search was made by a scout plane and it was found only a few minutes after it had made a forced landing because of minor trouble.

On another occasion one of the pylons reported a grass fire in the vicinity. A scouting plane was dispatched to the scene and an accurate report of the blaze was made to firemen within a very short time, thus aiding them materially in handling the situation.

It was one thing to tap out a few orders and acknowledgements at the key from time to time, but it was another thing to continue this work from hour to hour and from day to day. It was also quite a job to make five complete installations and then remove them after the races. Sometimes during the day there was considerable time between races. The most you had and the least you wanted was dust and heat! Ice cream sodas at a dollar each would be

Tell them you saw it in RADIO

SERVICE

If you are interested in commercial servicing of radio receivers, you should investigate the unusual merits of the following Weston instruments—each one a testing authority in its specific field.



This compact little instrument shown above has three ranges—150/8/4 volts. It is designed for line supply and filament voltage tests of A.C. Receivers. A handy kit instrument, exceptionally accurate, light and durable. Contained in mottled red and black Bakelite case.

MODEL 537 A.C. - D.C. SET TESTER

A complete servicing outfit that will quickly diagnose the trouble in any type of radio receiver set made—without need for any additional equipment. The meters provided are equivalent to ten instruments: A 3-range A.C. Voltmeter—150/8/4 volts; a D.C. Volt Milliammeter with five voltage ranges—600/300/120/60/9 volts, (all 1,000 ohms per volt); and two current ranges—150/30 milliamperes.

With this Weston Set Tester filament, grid, plate and cathode voltages are determined under actual operating conditions. It determines filament current requirements and plate current drain. It locates "shorts" between grid and plate as well as distortion in the audio system due to tube overloading. It provides for filament circuit and general continuity tests, and also serves as a rapid tube tester.

Write for descriptive circulars
just off the press



**WESTON ELECTRICAL
INSTRUMENT CORPORATION**
600 Frelinghuysen Ave.
NEWARK, N. J.

Pacific Coast Representatives
Graybar Electric Company, Inc. A. A. Barbera
84 Marion St. Los Angeles, Calif.
Seattle, Wash. Repair Service
J. H. Southard Laboratory
San Francisco, Calif. 682 Mission St.
San Francisco, Calif.

WESTON
RADIO
INSTRUMENTS

As a reward for their services they received the sincere thanks and appreciation of the race officials and the satisfaction that they had contributed, in no small way, to a good cause. They had saved the management some thousands of dollars. They had eliminated a large amount of worry for the officials. They received not a cent of money, as this is against the amateur's code of ethics and the rules of his license.

The boys operating the stations during the races were: Bert Fox (6DY), Charles A. Hill (6BRO-6DRO), Charles Lundblad (6CYX), William Breuer (6BZR), Charles A. Nichols (6ASM), Donald Champion (6FA), and Bob Parrish (6QF-6PS-6XC).

(Continued from Page 24)

rise on the low frequencies to compensate for the drop in the phonograph records. This may be accomplished by using an audio transformer in the first stage which has the primary circuit resonated at a low frequency, somewhere between 40 and 80 cycles per second. There are available on the market at least three varieties of transformers which have a resonant primary, generally with the condenser and *B* battery feed resistance, mounted inside of the transformer case. Such a transformer will give a decided peak on the very low notes when the unit is connected across it and the volume control is simply a variable resistance in shunt. With this arrangement much better music is available from phonographs than is available from most broadcast stations.

"Practical Radio," by James A. Moyer and John F. Wostrel, third edition, 378 pages, 5 by 7½ in. Published by McGraw-Hill Book Co., New York City. Price, \$2.50.

This text provides a simple answer to the question of what is radio and how is it transmitted and received. In an elementary manner it describes the circuits and parts ordinarily used in radio telephony and telegraphy. Its discussion of vacuum tubes is especially helpful to the novice. As part of a section devoted to the testing of sets is printed a trouble chart which shows at a glance the probable cause and remedy for the common troubles to which a set is liable. It also includes a somewhat sketchy treatment of a.c. filament tubes, rectifiers and loudspeakers. As a whole, it provides a good introduction to the serious study of the subject of radio stripped from its mathematical technicalities.

A low voltage filament is used in the '26 type of a.c. tube because thereby the a.c. hum is reduced. The lower voltage allows the use of a heavier filament and greater current with consequent smaller change in filament temperature and emission. The lower voltage also causes a smaller electro-static field and consequent tendency to hum.



Editor

M. L. MUHLEMAN

Managing Editor

G. C. B. ROWE

Associate Editors

JOHN F. RIDER

AUSTIN C. LESCARBOURA

Radio Engineering has been published for eight years for the engineers, technicians, manufacturers and dealers of the radio field.

It covers, in some forty text pages each month, the latest developments in manufacturing and engineering, design, production, etc. It includes valuable material on construction, testing and servicing.

In the "Commercial Developments" section, **Radio Engineering** deals with television, moving picture transmission, aeroplane and train communication, speech amplifying systems, etc.

Contributors and authors include the leading engineers in the electrical and radio field.

The Table of Contents of the Latest Issue includes:

By KENDALL CLOUGH

Engineering History

Past President A. I. E. E.

News of the Industry
(and other material)

"RADIO ENGINEERING" IS NOT SOLD ON NEWSSTANDS

If you are not already a subscriber, use the coupon below

BRYAN DAVIS PUBLISHING CO., INC.
52 Vanderbilt Avenue, New York, N. Y.

Enclosed find { \$2.00 for 1 year } Subscription to RADIO ENGINEERING.
 { \$3.00 for 2 years }

Enclosed find 20c for a sample copy of RADIO ENGINEERING.
(Please Print Name and Address)

Name


Address

City and State.....

Please check classification

☐ Manufacturer ☐ Dealer ☐ Professional Set Builder
☐ Engineer ☐ Service Man Anything Else.....

Tell them you saw it in **RADIO**

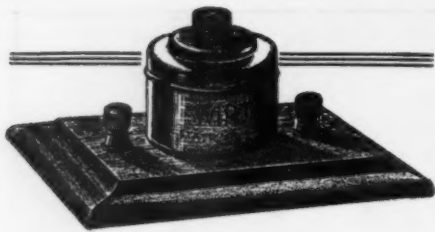


Cut out squeaks and squawks with Wirt Static Filter

Only \$2.25. Guaranteed to filter out practically all usual static noises—or get your money back. Sharpens selectivity. Sweetens tones, including high soprano. No distortion; volume stays the same. Fits any A-C or battery set, anywhere. Easy to install and adjust. Get one!


Save Your Tubes

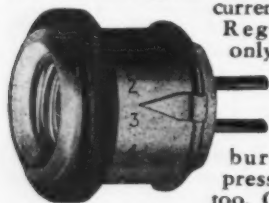with Wirt Voltage Regulator. A-C tubes and sets do best on 110 volts. Normal voltages are higher and there are frequent current "surges". Wirt Regulator admits only an even, constant flow into the set. Saves tubes and set from being burned out. Suppresses line noises, too. Only \$2.25.



Lightning Protection

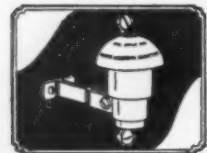Wirt Lightning Arrester safeguards not only the radio set, but all its parts, too—and, in any weather. Gives peace of mind during electrical storms. Easy to put in place. Stays rigid. Good looking. Only \$1.00.



Any radio dealer can get you Static Filter, Regulator, and Lightning Arrester. Or send check—we'll ship postpaid by return mail.

WIRT COMPANY

5221 Greene Street Philadelphia, Pa.
Makers of "Dim-a-lite" and "Dim-a-Lamp"

\$75 to \$125 Weekly

Charging Batteries Starts You

Let me show you how to make big money right from the start. I've prepared a FREE book explaining all details. First week's profit pays for all equipment. You can get all the battery charging business in your community with my Service Station Charger—it's years ahead of ordinary chargers—handles 50% to 70% more batteries. I explain everything—start you in a business of your own and put you on the way to big money. Write for FREE BOOK.

C. F. HOLMES, Chief Engineer, Dept. RM
Independent Electric Works
5118 Ravenswood Ave. Chicago, Ill.

FREE BOOK—Just Out



CONSTRUCTED BREAK-IN

(Continued from Page 40)

When the key is up you are receiving through the secondary of the transmitter's oscillation transformer. When the key is pressed the receiver is grounded out and the ground circuit of the transmitter is closed.

Be sure to adjust the contacts of the break-in so that they close just a fraction of a second before the main power contacts of the key close. In other words, the receiver must be grounded *before* the power goes into the transmitter for full protection. It is advisable to put a safety gap across the antenna and ground posts of the receiver as an added precaution; that is, if the receiver is not already so equipped.

AMATEUR RADIO RESEARCH CLUB BANQUET

By WALLACE S. WIGGINS

The largest amateur radio banquet in two years for Southern California took place in the Chamber of Commerce Building, September 12, 1928, sponsored by the Amateur Radio Research Club of Los Angeles. Over 115 enthusiasts of "brass pounding" were present in the banquet hall, which echoed and re-echoed with shrill whistles in true "ham" style.

A. H. Babcock, A. R. R. L. director, described the situation at Washington with regard to the status of the amateur, and stressed the importance of keeping up with the times in the design of transmitters and receivers for efficient operation in the new kilocycle bands. He also spoke of operation in channels other than the amateur bands, explaining the "American Eagle Channel," for the Army and Naval Reserve Units.

"Bob" Parrish, 6QF, president of the A. R. R. C., and chairman of the banquet committee, introduced the speakers. "Jimmie" Warner of KHAB, the "Southern Cross," first plane to fly from Oakland to Australia, modestly described part of the flight in a short speech, saying that the trip was "un-eventful," but that he appreciated the co-operation of the amateur operators. Bob Hutchings, 6AKF, related a most interesting story of a trip to Siberia and China on which they took portable receiving and transmitting equipment. The big "kick" of the evening came when Hutchings said that although reception was none too good, the strongest signals from the United States came from 6CUT. As the owner and operator of that station was present, he was called upon to describe his supposedly super-high powered transmitter for the benefit of those unfortunates who lacked the cash to purchase high-powered stuff. He was introduced as Homer F. Beal, Jr., of Riverside, Calif. The surprise and wonder of the assembly can well be imagined when Beal said he was using a 7½-watt tube with 1000 volts on the plate through a 30-henry choke. He explained further, however, that a zeppelin antenna, constructed with the greatest care, was being used. This probably accounted for a large share of the success of his strong signals in Siberia.

"Wally" Wiggins, 6CHZ, explained the operations at the National Air Races in connection with the club's activities in providing communication. Bert Fox, 6DY, supplemented this with an explanation of the details of installation and operation. It was announced that over 2400 messages had been handled, free of charge, for patrons of the recent radio show in Los Angeles.

Tell them you saw it in RADIO



Wire Your Home for Radio



Build Up Your Radio Sales



Radio Convenience Outlets

THE newest and fastest selling thing in radio—a convenience outlet for every radio need. No unsightly wires inside or outside of the building; no marring of the woodwork. Your customers can enjoy their radio programs in any room in the house. Every radio user is a prospect for radio outlets and radio wiring. Easily installed. Fit any standard switch box. Full instructions and wiring information.

No. 135—For Loud Speaker	\$1.00
No. 136—For Aerial and Ground	1.00
No. 137—For Battery Connections	2.50
No. 138—For A. C. Connections	1.00
No. 134—For Several Loud Speakers	2.50
No. 132—For Power Pack Connections	3.00

At Your Dealers

YAXLEY MFG. CO.

Dept. A, 9 So. Clinton Street
CHICAGO, ILLINOIS

MARSHALL SHORT-WAVE RECEIVER

(Continued from Page 36)

after time without any variation in the dial readings or numbers. Reception on 8000, 12,000 and 16,000 kilocycles was effected without interference. A temporary removal of one of the shielded-grid tubes, however, cut down the signal strength appreciably.

Using this receiver, the *Eagle* picked up signals in the daytime with regularity from Washington, D. C.; Key West, Fla.; New Orleans, La.; and Guantánamo, Cuba, while cruising in the Panama Canal Zone. However, the signals from stations northward from Louisiana to the Great Lakes were intercepted with the greatest clarity while the *Eagle* was located in the Panama Canal waters. Amateur stations on the Atlantic seaboard were also heard satisfactorily. The comparative tests between this receiver and a standard navy outfit were conducted with both receivers connected to the same antenna—using the so-called "coupled tube" arrangement of the Bellevue Naval Research Laboratory.

Tests on a submarine were restricted by the usual limiting factor of submerging radio in salt water, namely, at a depth of 20 feet there is a sudden and complete extinction of the received radio signal. However, this receiving set oscillated and was as easily controlled while submerged as when on the surface of the water. Furthermore, when using a loop or coil of wire as pick-up system on this submarine the distant signals—from Rocky Point and other transmitting stations—were nearly as loud as when employing the conventional high-frequency antenna on the *Eagle*. The use of one-half of the loop antenna on the submarine caused a material sacrifice in signal strength. When the submarine was resting on the surface of the water, this new receiver appeared to function most advantageously when receiving signals from distant stations on a frequency of 18,000 kilocycles.

IMPROVEMENTS IN CRYSTAL CONTROL

AMATEURS should take particular note of the improvements which are being incorporated into many of the broadcasting stations, in the form of crystal control. Several of the stations have two crystals, either of which may be used as the main control, and these crystals are cut so accurately as to be within 100 cycles of each other. To maintain accurateness of frequency, each crystal is heated electrically to a certain fixed temperature, at which it is calibrated.

With the coming limitations of the amateur bands, there will undoubtedly be an increased use of crystal control on the short waves. By the installation of a simple heating system and ther-

(Continued on Page 51)

ENJOY ANY MIRACO

30 DAYS=

Compare it with Costliest Radios

RETURN EVERYTHING, OUR EXPENSE, UNLESS DELIGHTED



Latest - Powerful - New

MIRACO

TRADE MARK REGISTERED

Cathedral Toned, Super Selective, Long Distance Getters

Battery or Electric AC Sets

ENJOY any Miraco 30 days in your home. Return everything, our expense, unless delighted **YOUR VERDICT FINAL.** Send for latest catalog and Amazing Special Wholesale Price Offer.

America's big, old, reliable Radio Corporation springs its 9th annual sensation! Latest shielded 1-dial, Super-powered, hum-free Electric AC and newest battery sets of finest construction and costliest features at astounding low factory prices.

Compare with radios at 2 to 4 times the price—unless your Miraco proves itself the **MOST SELECTIVE, RICHEST, CLEAREST TONED, and MOST POWERFUL DISTANCE GETTER**, don't buy! Miracos have phonograph pick-up connection.

Delighted thousands report programs from Coast to Coast, Canada, Cuba, Mexico, with magnificent clear, cathedral tone. 3 year guarantee on each set. Choice of beautiful consoles, metal or wood table cabinets, latest dynamic power speakers, radio-phonograph combinations.

Insure complete satisfaction, save or make much money—deal direct with a big old maker of fine radios—9th successful year. Get amazing offer!

MIDWEST RADIO CORP'N, 414-CN Miraco Bldg., Cincinnati, O.

BEAUTIFULLY ILLUSTRATED CATALOG, AMAZING SPECIAL FACTORY OFFER, TESTIMONY OF NEARBY USERS—All the proof you want—of our honesty, fairness, size, financial integrity, radio experience and the performance of our sets—including Amazing Factory Offer—sent with catalog.

Free MIDWEST RADIO CORP'N 9th Successful Year

414-CN Miraco Bldg., Cincinnati, O.

WITHOUT OBLIGATION, send free catalog, Amazing Special Factory Offer, testimony of nearby users, etc. ☐ User ☐ Agent ☐ Dealer

NAME ADDRESS

Ultra8
\$49.88

Electric
AC-8
\$71.50

Electric
AC-9
\$83.75

Big
Discounts
and
Exclusive Ter-
ritory to User-
Agents on Bat-
tery or AC Elec-
tric Outfits

THIS COUPON
IS NOT
AN ORDER

NEW LOW FACTORY PRICES SAVE 50%

Choice of Cabinets AC or Battery Sets

30 Days' Trial

Richly designed genuine walnut console of finest type. Electro-dynamic magnetic power speaker.

Graceful Spinnet console, genuine walnut. Choice of speakers. Also comes in Radio-Phonograph Comb'n.

A Le-Boy Console that costs little. Dynamic Power Speaker.

Popular inexpensive combination. Set on table speaker.

New-type arm-chair console of genuine walnut-latest speakers.

A REAL SPECIAL OFFER!!

UNI-RECTRON POWER AMPLIFIER

(Ideal for use with Dynamic Speakers)

Model AP-935



As the Uni-Rectron stands it is a super power amplifier, which can be used in connection with any radio set and loud speaker. Binding posts are provided for input to the Uni-Rectron and output to the speaker. Requires no batteries for its operation. It obtains its power from the 110 volt, 60 cycle alternating current lighting circuit of your house.



List Price \$88.50
(without tubes)

SPECIAL \$19.75 Ea.

Every one now and packed in original factory carton

The UX-210 super power amplifying tube and the UX-216B or 281 rectifying tube are used with this amplifier, which cannot overload. From the faintest whisper to the loudest crash of sound—R. C. A. Uni-Rectron amplifies each note at its true value. High and low notes are all treated alike. The volume and quality delivered will be a revelation.

AMERICAN SALES COMPANY, 19-21 WARREN STREET, NEW YORK CITY

Tell them you saw it in RADIO

LONGER LIFE



WHEN you install a set of CeCo Tubes in your radio, you immediately notice the greater clarity of reproduction—the increased sensitivity and the better volume.

But your greatest satisfaction will come with their longer operating life, making CeCo the most economical tubes to buy, and worthy of their slogan “they cost no more, but last longer.” This is made possible partly by the exclusive method of evacuation.

To avoid disappointing results, make sure each socket is equipped with CeCo tubes. Whether for battery or A. C. operation—there’s a CeCo for every radio need—including “special purpose” tubes that are not obtainable elsewhere. They are sold by leading dealers everywhere.

Write for copy of our booklet entitled “Getting the most out of your radio.”

CeCo MANUFACTURING Co. Inc.
PROVIDENCE, R. I.

TUBE TESTING SET

(Continued from Page 33)

The reading should then be compared with the nominal limits as indicated on the accompanying table. If the emission

POWER AND RECTIFIER TUBE TESTS

Indication for Good Tube

CX 310	No. 1	Dull red
	No. 2	Dull orange
CX 313	No. 1	Dull orange
	No. 2	
CX 316B	No. 1	Dark
	No. 2	Dull orange
CX 350	No. 1	Dull red
	No. 2	Dull orange
CX 380	No. 1	Dull orange
	No. 2	
CX 381	No. 1	Dark
	No. 2	Dull orange

reading is below these figures it indicates, as a rule, that the tube has been overloaded due to excessive filament or plate voltage, or both, or that there has not been sufficient C battery voltage provided.

To take an emission reading on a 322, the screened grid amplifier, it is necessary to connect the two grids together; this may be easily done by arranging an X base socket on an X tube base, connecting a flexible wire with a clip on it to the grid terminal of the socket, inserting the 322 into this adapter, placing the whole assembly into the proper socket in the test set. If no short circuits are shown on the lamps, connect the clip to the top contact on the 322 and then press the emission key momentarily. To test the C-11 it will be necessary to use an adapter to accommodate the special arrangement of contact pins to the C-12 socket.

Type 300-A gas filled detector tubes require a special test for sensitivity, and can only be tested for short circuits and filament emission in this test set.

The testing of 310, 313, 316-B, 350 and 381 tubes is extremely simple, it being only necessary to place the tube in the socket with the switch in position No. 1, the condition of the tube being indicated by the glowing of the lamps. Make certain before placing the tube in the socket that there is no short circuit between the elements. A low emission tube usually indicates abuse resulting from too high filament voltage, too high plate voltage, or insufficient grid voltage. A gassy tube may cause the lamps to glow as if O. K., but of course, is de-

World's lowest priced power speaker radio operating



6 tube
GEMBOX \$65
AC ELECTRIC

You will not be satisfied with your old set after you hear one of the new Crosleys. The new full toned power speaker Crosley sets are 1928's greatest radio achievement. Compare a Crosley set with any other and you will find it to be up-to-date—genuine neutrodyne, selective, sensitive, illuminated dial, completely shielded, volume without distortion and adaptability for installation in any type console cabinet.



Showbox \$80



Bandbox \$55



Musicone \$15



Bandbox Jr. \$35

FIVE DAYS FREE TRIAL IN YOUR OWN HOME

Crosley Dealers are authorized to home demonstrate any Crosley Receiver. This is the only way to buy radio. Visit your nearest dealer or write Dept. 19 for his name and address.

CROSLEY

The Crosley Radio Corporation
Powell Crosley, Jr., Pres. CINCINNATI, O.
Montana, Wyoming, Colorado, New Mexico
and West prices slightly higher
Prices of Crosley Radio Receivers do not include tubes

Newest Information TO SET BUILDERS

LATEST RADIO GUIDE

Elections, football games, big National events will boost radio business this year. Set builders will reap a rich harvest. Barawik service will make you money. Everything in A-C sets, parts, supplies. World's largest radio stocks on hand. Orders shipped same day. Lowest rock-bottom wholesale prices.

Mail coupon for free Radio Catalog now

BARAWIK CO. 1811 Canal St., CHICAGO, U. S. A.

Mail this coupon for Free Radio Guide

Name _____
Address _____

	C 11	C-CX'	CX	CX	CX	CX	CX	CX	CX	CX	CX	C
	CX12'	299	220	301A	300A	340	112	112A	371	371A	326	327'
Filament												
Voltage (Min. MA)	1.1	3.3	3.3	5.0	5.0	5.0	5.0	5.0	5.0	5.0	1.5	2.5
Emission	6.0	5.5	13.0'	20.0'	14.0'	14.0'	45.0'	45.0'	40.0'	40.0'	35.0'	35.0

Tell them you saw it in RADIO

fective. Make certain that there is no decided blue glow surrounding the filament. A faint glow on the 380s, 381s and 350s is the normal condition and does not indicate a defect.

LIST OF PARTS FOR TEST SET

- 1 Panel 12 x 20 in.
- 4 X base sockets
- 1 Navy type socket
- 2 Dial lamp sockets (Edison Min. base)
- 2 110-volt lamp sockets, Standard type
- 1 Socket for 327 a.c. tubes
- 1 Socket for old style 99 tubes
- 1 Socket for 377 protective lamp, Bayonet type
- 2 10-watt, 110-volt Mazda lamps
- 1 6-ohm, $\frac{1}{4}$ -amp. fixed resistor
- 1 7-wire cable, 5 ft. long
- 1 Kellogg Model 301 Key
- 1 10-ohm rheostat, $1\frac{1}{2}$ amps. load
- 1 0-6 V. voltmeter
- 1 0-50 M. A. milliammeter
- 1 4-contact switch
- 1 $\frac{1}{2}$ -ohm 2-amp. resistor (6 in. No. 22 Nichrome wire)
- 2 Dial lamps, 6 volts

The thoriated tungsten filament tubes may be reactivated if the overload has not been too severe. The coated type of filament cannot be reactivated due to its design, and any attempt will result in its immediate burnout. The tubes which may be reactivated are as follows: 99, 220, 322, 300-A, 301-A, 340, 371, 310, 313 and 316-B.

In reading the tables accompanying this description, it is well to keep in mind the following notes:

If the dial lamps light, it indicates a short circuit; do not then attempt to take an emission reading or you will damage the meters.

Lighting of lamp No. 1 indicates a grid to filament short; lamp No. 2 indicates a plate to filament short; both lamps indicate grid to plate short.

An open or burned out filament may fall against the grid or plate, causing the lamps to light. This may be determined by turning the rheostat up and if voltage regulation is impossible, the filament is open; such tubes are called open filaments, either broken or burned out, according to the results of the inspection at the service station.

IMPROVEMENTS IN CRYSTAL CONTROL

(Continued from Page 49)

mometer as an indicator, the amateur can maintain an absolutely dependable constant frequency of transmission. By placing the crystal with its associated tube, inductance and condenser in a closed box or compartment, together with a 25 or 40-watt mazda lamp controlled by a rheostat, a control of the temperature can easily be had, at little or no additional expense.

The broadcast stations are commencing to use an enclosed automatic heating unit and crystal which is supplied by the Western Electric Co. But an amateur does not need the automatic feature if he watches the thermometer.

The New Knapp "A" Power Kit



*Magically
Silent*

Absolutely Dry

This is the "A" power after you have assembled it. A professional job! Operates on 105 to 120 volts, 50 to 60 cycles AC. Supplies rippleless DC current for operating any set using Standard 5 or 6 volt tubes and power tubes.

Greatly Improved—and at a Lower Price New Money-Making Plan for Set-Builders

The new Knapp "A" Power has all of the features of the old model—magic silence—absolutely dry—"B" Eliminator receptacle—voltage regulator—complete, tooled part kit, etc., etc., and also eight new improvements which make it the finest "A" Power ever put out.

Compare the appearance, read the improvements—and remember that the price has been reduced!

The Only "A" Power Adaptable to Short Wave, Super-Heterodyne and Television Reception

The Knapp "A" because of its superior filter system and the special Elkon rectifier is so silent and so steady that it functions perfectly.

The 8 Improvements

1. Larger Filter System—3 Elkon Condensers instead of 2. Ideal for Super-Hets, Short Wave sets and Television.
2. Improved Choke Coils
3. Pendant Switch Controlling "A", "B" Eliminator and Set
4. Dial for regulating voltage
5. Celeron Front Panel
6. Baked finish
7. Heavier gauge metal cover
8. Die Cast Base Plate instead of wood

COMPLETE KIT—EASILY ASSEMBLED

The New Knapp Kit is a tooled job—the parts seem to fall into place.

Every hole is drilled—all you do is put the screws and nuts in place and connect a few wires. Just follow instruction sheet. No extras to buy.

THE SET-BUILDER TAKEN CARE OF

Regardless of what the established trade may think about it—I am going to continue to give you the maximum discounts. The coupon will bring you the full details of both the new "A" Power and the special discounts to set-builders.

David W. Knapp, Pres.

KNAPP ELECTRIC, Inc., Port Chester, N.Y.
—Div. P. R. Mallory & Co., Inc.—



Mr. David W. Knapp, President,
KNAPP ELECTRIC, Inc.,
Dept. K-10, 350 Madison Ave., New York City
Kindly send me complete information on the
Knapp "A" Power and your special discounts for
Set-Builders.

Name _____
Address _____

LONGER LIFE



CeCo
RADIO TUBES
PRONOUNCED
SEE - CO
Radio Tubes

WHEN you install a set of CeCo Tubes in your radio, you immediately notice the greater clarity of reproduction—the increased sensitivity and the better volume.

But your greatest satisfaction will come with their longer operating life, making CeCo the most economical tubes to buy, and worthy of their slogan “they cost no more, but last longer.” This is made possible partly by the exclusive method of evacuation.

To avoid disappointing results, make sure each socket is equipped with CeCo tubes. Whether for battery or A. C. operation—there’s a CeCo for every radio need—including “special purpose” tubes that are not obtainable elsewhere. They are sold by leading dealers everywhere.

Write for copy of our booklet entitled “Getting the most out of your radio.”

CeCo MANUFACTURING Co. Inc.
PROVIDENCE, R. I.

TUBE TESTING SET

(Continued from Page 33)

The reading should then be compared with the nominal limits as indicated on the accompanying table. If the emission

POWER AND RECTIFIER TUBE TESTS

Indication for Good Tube

CX 310	No. 1	Dull red
	No. 2	Dull orange
CX 313	No. 1	Dull orange
	No. 2	
CX 316B	No. 1	Dark
	No. 2	Dull orange
CX 350	No. 1	Dull red
	No. 2	Dull orange
CX 380	No. 1	Dull orange
	No. 2	
CX 381	No. 1	Dark
	No. 2	Dull orange

reading is below these figures it indicates, as a rule, that the tube has been overloaded due to excessive filament or plate voltage, or both, or that there has not been sufficient C battery voltage provided.

To take an emission reading on a 322, the screened grid amplifier, it is necessary to connect the two grids together; this may be easily done by arranging an X base socket on an X tube base, connecting a flexible wire with a clip on it to the grid terminal of the socket, inserting the 322 into this adapter, placing the whole assembly into the proper socket in the test set. If no short circuits are shown on the lamps, connect the clip to the top contact on the 322 and then press the emission key momentarily. To test the C-11 it will be necessary to use an adapter to accommodate the special arrangement of contact pins to the C-12 socket.

Type 300-A gas filled detector tubes require a special test for sensitivity, and can only be tested for short circuits and filament emission in this test set.

The testing of 310, 313, 316-B, 350 and 381 tubes is extremely simple, it being only necessary to place the tube in the socket with the switch in position No. 1, the condition of the tube being indicated by the glowing of the lamps. Make certain before placing the tube in the socket that there is no short circuit between the elements. A low emission tube usually indicates abuse resulting from too high filament voltage, too high plate voltage, or insufficient grid voltage. A gassy tube may cause the lamps to glow as if O. K., but of course, is de-

World's lowest priced power speaker radio operating



New Dynamic
DYNACONE
‘25

6 tube
GEMBOX \$65
AC ELECTRIC

You will not be satisfied with your old set after you hear one of the new Crosleys. The new full toned power speaker Crosley sets are 1928's greatest radio achievement. Compare a Crosley set with any other and you will find it to be up-to-date—genuine neutrodyne, selective, sensitive, illuminated dial, completely shielded, volume without distortion and adaptability for installation in any type console cabinet.



Showbox \$80



Bandbox \$55



Musicone \$15



Bandbox Jr. \$35

**FIVE DAYS
FREE TRIAL
IN YOUR
OWN HOME**

Crosley Dealers are authorized to home demonstrate any Crosley Receiver. This is the only way to buy radio. Visit your nearest dealer or write Dept. 19 for his name and address.

CROSLEY

The Crosley Radio Corporation
Powel Crosley, Jr., Pres. CINCINNATI, O.
Montana, Wyoming, Colorado, New Mexico
and West prices slightly higher
Prices of Crosley Radio Receivers do not include tubes

Newest Information TO SET BUILDERS

Elections, football games, big National events will boost radio business this year. Set builders will reap a rich harvest. Barawik service will make you money. Everything in A-C sets, parts, supplies. World's largest radio stocks on hand. Orders shipped same day. Lowest rock-bottom wholesale prices.

Mail coupon for free Radio Catalog now
BARAWIK CO. 1811 Canal Sta., CHICAGO, U. S. A.
Mail this coupon for Free Radio Guide

Name _____
Address _____

	C 11	C-CX'	CX	CX	CX	CX	CX	CX	CX	CX	CX	C
	CX12'	299	220	301A	300A	340	112	112A	371	371A	326	327'
Filament Voltage	1.1	3.3	3.3	5.0	5.0	5.0	5.0	5.0	5.0	5.0	5.0	2.5
(Min. MA)												
Emission	6.0	5.5	13.0'	20.0'	14.0'	14.0'	45.0'	45.0'	40.0'	40.0'	35.0'	35.0

Tell them you saw it in RADIO

fective. Make certain that there is no decided blue glow surrounding the filament. A faint glow on the 380s, 381s and 350s is the normal condition and does not indicate a defect.

LIST OF PARTS FOR TEST SET

- 1 Panel 12 x 20 in.
- 4 X base sockets
- 1 Navy type socket
- 2 Dial lamp sockets (Edison Min. base)
- 2 110-volt lamp sockets, Standard type
- 1 Socket for 327 a.c. tubes
- 1 Socket for old style 99 tubes
- 1 Socket for 377 protective lamp, Bayonet type
- 2 10-watt, 110-volt Mazda lamps
- 1 6-ohm, 1/4-amp. fixed resistor
- 1 7-wire cable, 5 ft. long
- 1 Kellogg Model 301 Key
- 1 10-ohm rheostat, 1 1/2 amps. load
- 1 0-6 V. voltmeter
- 1 0-50 M. A. milliammeter
- 1 4-contact switch
- 1 1/2-ohm 2-amp. resistor (6 in. No. 22 Nichrome wire)
- 2 Dial lamps, 6 volts

The thoriated tungsten filament tubes may be reactivated if the overload has not been too severe. The coated type of filament cannot be reactivated due to its design, and any attempt will result in its immediate burnout. The tubes which may be reactivated are as follows: 99, 220, 322, 300-A, 301-A, 340, 371, 310, 313 and 316-B.

In reading the tables accompanying this description, it is well to keep in mind the following notes:

If the dial lamps light, it indicates a short circuit; do not then attempt to take an emission reading or you will damage the meters.

Lighting of lamp No. 1 indicates a grid to filament short; lamp No. 2 indicates a plate to filament short; both lamps indicate grid to plate short.

An open or burned out filament may fall against the grid or plate, causing the lamps to light. This may be determined by turning the rheostat up and if voltage regulation is impossible, the filament is open; such tubes are called open filaments, either broken or burned out, according to the results of the inspection at the service station.

IMPROVEMENTS IN CRYSTAL CONTROL

(Continued from Page 49)

nometer as an indicator, the amateur can maintain an absolutely dependable constant frequency of transmission. By placing the crystal with its associated tube, inductance and condenser in a closed box or compartment, together with a 25 or 40-watt mazda lamp controlled by a rheostat, a control of the temperature can easily be had, at little or no additional expense.

The broadcast stations are commencing to use an enclosed automatic heating unit and crystal which is supplied by the Western Electric Co. But an amateur does not need the automatic feature if he watches the thermometer.

The New Knapp "A" Power Kit



This is the "A" power after you have assembled it. A professional job! Operates on 105 to 120 volts, 50 to 60 cycles AC. Supplies rippleless DC current for operating any set using Standard 5 or 6 volt tubes and power tubes.

Greatly Improved—and at a Lower Price New Money-Making Plan for Set-Builders

The new Knapp "A" Power has all of the features of the old model—magic silence—absolutely dry—"B" Eliminator receptacle—voltage regulator—complete, tooled part kit, etc., etc., and also eight new improvements which make it the finest "A" Power ever put out.

Compare the appearance, read the improvements—and remember that the price has been reduced!

The Only "A" Power Adaptable to Short Wave, Super-Heterodyne and Television Reception

The Knapp "A" because of its superior filter system and the special Elkon rectifier is so silent and so steady that it functions perfectly.

The 8 Improvements

1. Larger Filter System—3 Elkon Condensers instead of 2. Ideal for Super-Hets, Short Wave sets and Television.
2. Improved Choke Coils
3. Pendant Switch Controlling "A", "B" Eliminator and Set
4. Dial for regulating voltage
5. Celeron Front Panel
6. Baked finish
7. Heavier gauge metal cover
8. Die Cast Base Plate instead of wood

COMPLETE KIT—EASILY ASSEMBLED

The New Knapp Kit is a tooled job—the parts seem to fall into place.

Every hole is drilled—all you do is put the screws and nuts in place and connect a few wires. Just follow instruction sheet. No extras to buy.

THE SET-BUILDER TAKEN CARE OF

Regardless of what the established trade may think about it—I am going to continue to give you the maximum discounts. The coupon will bring you the full details of both the new "A" Power and the special discounts to set-builders.

David W. Knapp, Pres.

KNAPP ELECTRIC, Inc., Port Chester, N. Y.


—Div. P. R. Mallory & Co., Inc.—



Mr. David W. Knapp, President,
KNAPP ELECTRIC, Inc.,
Dept. K-10, 350 Madison Ave., New York City
Kindly send me complete information on the
Knapp "A" Power and your special discounts for
Set-Builders.

Name _____
Address _____

(Continued from Page 42)

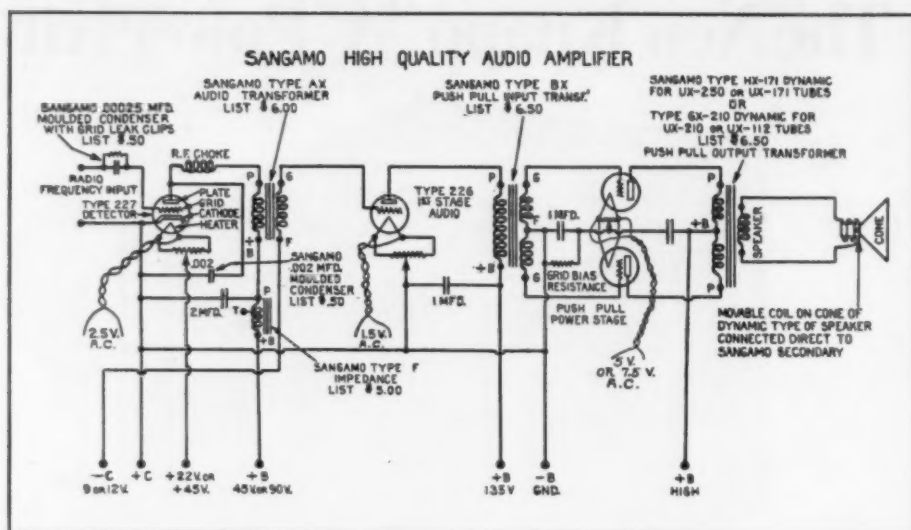

Now! Sangamo Transformers at a new low price. And push-pull transformers to match new power tubes and dynamic loud speakers.

A small expenditure and you can have one of these modern amplifiers with plenty of capacity to handle the low notes. Nothing equals the full toned beauty of an amplifier built according to the diagram shown above. Write for descriptive circulars.



**SPRINGFIELD,
ILLINOIS**

SANGAMO ELECTRIC COMPANY

Pacific Coast Offices:
1061 Howard St.
SAN FRANCISCO
730 Subway
Terminal Bldg.
LOS ANGELES

TYPE 254
TRANSFORMER
CENTRAL RADIO CO.
LAUREL, MICHIGAN

V	A	W
115	0.1	12.5
250	0.05	6.25
500	0.025	3.125
1000	0.0125	1.5625

TYPE 565-A TRANSFORMER
(200 watts)

PRICE - - - \$13.50

The General Radio Type 565 Power Transformers consist of two models for both half and full-wave rectification utilizing the 281 type of rectifier tube. The Type 565-A Half-Wave Transformer illustrated consists of one 600-volt secondary, two secondaries of 7.5 volts and one of 2.5 volts. It is designed for 105 to 125-volt, 50 to 60-cycle lines.

Bulletin No. 931 will be sent on request.

General Radio Co.

30 State Street, Cambridge, Mass.

• 274 Brannan Street San Francisco, Calif.

PROFESSOR HERMANN SCHNITZEL

Of the Ooniversity of Cincinnati, O-ho-ho

has written a booklet containing 21 short radio lectures which have been broadcast from many stations. 50 cents per copy, postpaid. You will enjoy this book.

For sale by "RADIO," Pacific Building, San Francisco

to a low value and the setting noted. A pair of grid-leak clips are mounted on it and a variable grid leak is best, although 5 megohms is the usual value.

A 112 used as detector oscillates easily at the highest frequencies. No tube-socket is used, since different tubes change things so much. The set ought to be built around the particular type of tube employed. Holes are drilled through the bakelite and the leads are soldered in place. Should another tube be necessary, the 112 is easily removed as it is at the rear of the set.

No short-wave receiver should be without a filament switch, as best oscillation is always secured at some particular filament-setting. These tubes usually work best with very low filament and about $67\frac{1}{2}$ volts on the plate; other tubes will sometimes require comparatively large values of tickler turns and often higher plate voltages. The correct adjustment of the set, for the higher frequencies, is important and will require some experimentation for values giving best results.

The arrangement of apparatus is convenient for the experimenter as the filament rheostat and switch, phone jack and audio amplifier are mounted on a separate panel. All parts are arranged so that they can be used separately.

The whole set is mounted on a heavy base-board and is supported above it. The 4½-volt *C* battery is mounted underneath. Dry cell tubes can be used and the set made semi-portable; it is a simple matter to mount the layout on the seat of the car and study the 5 or 10-meter signals at a distance from the station.

The audio transformers peak at 1000 cycles and the set therefore gives best response at this audio frequency. There are still AC signals on the air so that a very selective audio amplifier would hardly be desirable yet, especially for all-wave use. In this amplifier, the better signals are received with excellent results and extraneous noises are greatly reduced. Often one can "tune" an audio transformer to about the correct value by using condensers across the windings; some transformers are designed for peaks in the audio range.

The selection of proper midget condensers is important, as many types are not so good. If these are of the one-bearing type, this bearing should be well-constructed and about this the amateur knows. These condensers will eventually replace the larger sizes for most short-wave uses. Almost a whole set of these may be obtained for the price of the usual large instrument. They are as good electrically, if not better, than the larger sizes, especially at the higher frequencies as shown by repeated tests at 5 and 10 meters.


The coils can be celluloid-supported and No. 20 wire is about right for the well-spaced turns. The 5-meter coil consists of about 2 heavy turns on a 1-in. diameter, and the 10-meter one is about double that; at 40 meters, 18 or 20 spaced turns is about right, but the values are not critical because the shunt condenser will compensate. Large coil diameters for 5 and 10 meters should be avoided as movement of the body then has considerable effect on regeneration.

Fixed filament resistors are used in the audio amplifier. To use the set without r.f. amplifier, the antenna is connected directly to a lug on the secondary condenser through a small midget. The output of the r.f. amplifier may be similarly connected; it is perhaps better to use separate batteries for the r.f. amplifier but one will work all right with the same batteries for the whole layout. Often the tube will oscillate much better if the filament leads to the detector are reversed.

The actual wave-change caused by supposedly small effects is too large. In the usual

amateur wavemeter employing a flashlamp indicator, the wave may be changed as much as 1/2 meter at 40 meters by simply changing lamps or shorting a given lamp in or out. Such changes are too large for 1929 conditions. There are perhaps only two arrangements which are practical for average amateur use.

One of these consists of the tuned circuit described above to which is coupled a 2-turn loop (at 40 meters) including a flashlamp in series. Some flashlamps give very broad tuning, but tests show that the 1.25-volt type ("S" filament) is about the best to use, as the filament cools rapidly and gives a sensitive indication. If the main inductance consists of about 18 turns on a 2-in. tube, this 2-turn loop should be set at about 3/4 in. from it. Indications will be quite sharp, and with loose coupling, the effect of the lamp circuit causes very little tuning effect. The lamp when turned into, or out of, the socket will have a small effect on the wave, but if left in place, will give good results and tuning will be sharp.

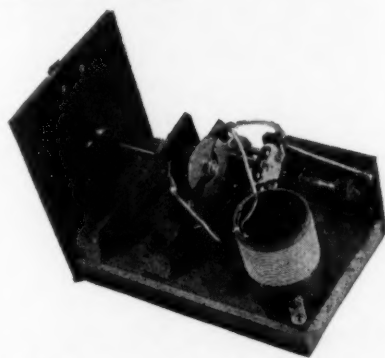

Wavemeter with Neon Tube Indicator

An accurate wavemeter is necessary for calibrating the set. The picture and circuit diagram in Fig. 2 show one using a neon lamp as a resonance indicator. It uses a 15 mmfd. midget tuning condenser cut down to three plates and a 20-turn coil, which is wound on a threaded length of 2 in. bakelite tubing. A 50 mmfd. midget condenser is shunted across the tuned circuit.

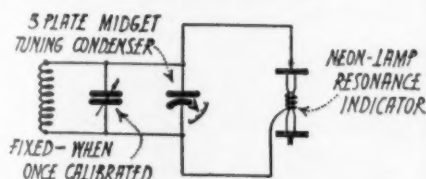


Fig. 2. Wavemeter Circuit Diagram

The condensers are mounted on a hard rubber strip which, together with the panel supporting the vernier dial, is securely fastened to heavy baseboard blocks. A small extension handle eliminates the necessity of shielding. The threaded tubing is secured to the baseboard by small metal angles at the base. Heavy copper wire is used for connections.

The neon lamp should be of 5-watt size or larger. It is somewhat more sensitive if one terminal is left open and a length of copper wire, wound around the middle, is used as the other. The lamp is securely fastened to a bakelite piece and is held by a piece of wire passed around the lamp and through holes.

For accuracy, it is best to have a separate instrument for the 40-meter band. The small condensers are economical and at small expense accurate instruments can be constructed for 20 and 40 meters. The 10-meter band is wide and accuracy is not as important.

To calibrate the wavemeter accurately, the transmitter can be operated without an

Positive Line Voltage Control Safe

PROTECT your A.C. tubes from excessive filament voltage and insure maximum efficiency from your new A.C. receiver, which is designed to operate at a certain specified line voltage. To be safe, you must have some means of controlling the voltage from the light socket, which varies in different localities and during certain times of the day.

The Centralab Radio Control Box is the most advanced form of voltage regulator. It is so designed that it will provide absolute positive and safe control of line voltage. A simple manual control is the only adjustment. No meters or technical knowledge required to operate, although meter can be attached at little extra cost if desired.



PRICE \$3.00

26 Keefe Avenue

Centralab
CENTRAL RADIO LABORATORIES

Milwaukee, Wisconsin

TELEVISION

although still in an experimental stage, has now advanced sufficiently to enable amateurs to build outfits that will give edifying results.

Write today for our price list of television apparatus.

Photo Electric Devices, Inc.
594 Fifth Ave. Brooklyn, N. Y.

Gerald Best's SUPER BLUE PRINTS

The complete working plans in full size for building the new incomparable Gerald Best 115 Kilocycle superheterodyne with full instructions for building.

25c Per set. Postpaid anywhere in the U. S. Send remittance by cash, check or money order. Stamps also accepted. "RADIO," Pacific Bldg., San Francisco, California.


Free

A Continental Control Switch will be given free with a one year subscription to RADIO (\$2.50) if you act immediately. Only a few on hand.

"RADIO"
Pacific Building San Francisco

Marvelous Reception

Full tone over the entire receiving range by equipping your Power Amplifier with a Potter Condenser Block.

No. T2900 where one 250 Type Power Tube is used		No. T2950 where two 250 Type Power Tubes are used
\$20.00		\$22.50

Highly Efficient—Long Life

The Choice of Leading Radio Engineers

Ask your dealer for full information


POTTER MFG. CO.
North Chicago, Illinois

LAST MINUTE SPECIALS!

E210 BRADLEYSTATS, list \$4.00	Our Price \$1.60 ea.
MESCO Wireless Keys, list \$2.00	" 95c ea.
U. S. ARMY Aeroplane Spark Transmitters, Gov. cost \$47 each	" 4.75 ea.
G. E. Kenotron Rectifying Tubes (type T.B.1)	" 1.25 ea.
Eby A.C. Adapter Harness with Volume Control. For 6 tube Sets, list \$10.00	" 5.00 ea.
Gould Kathanode Unipower, Automatic Radio "A" Power (6 volt), list \$39.50	" 13.75 ea.

AMERICAN SALES CO., 19-21 WARREN ST., NEW YORK CITY

Tell them you saw it in RADIO

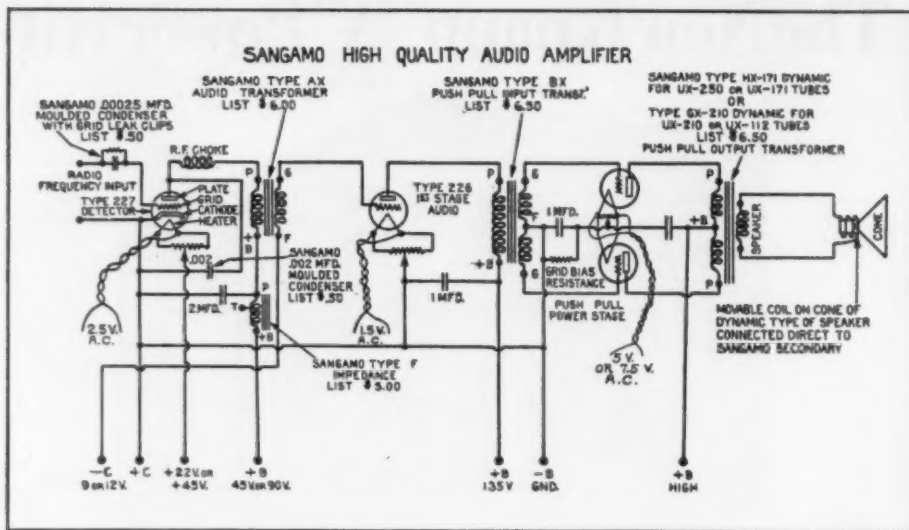

Build this modern amplifier at Low Cost!

Now! Sangamo Transformers at a new low price. And push-pull transformers to match new power tubes and dynamic loud speakers.

A small expenditure and you can have one of these modern amplifiers with plenty of capacity to handle the low notes. Nothing equals the full toned beauty of an amplifier built according to the diagram shown above. Write for descriptive circulars.



SPRINGFIELD,
ILLINOIS

**SANGAMO
ELECTRIC COMPANY**

Pacific Coast Offices
1061 Howard St.
SAN FRANCISCO
750 Subway
Terminal Bldg.
LOS ANGELES

POWER TRANSFORMERS for the UX 250 Power Tube



TYPE 565-A TRANSFORMER
(200 watts)

The General Radio Type 565 Power Transformers consist of two models for both half and full-wave rectification utilizing the 281 type of rectifier tube. The Type 565-A Half-Wave Transformer illustrated consists of one 600-volt secondary, two secondaries of 7.5 volts and one of 2.5 volts. It is designed for 105 to 125-volt, 50 to 60-cycle lines.

Bulletin No. 931 will be sent on request.

General Radio Co.

PRICE - - - \$13.50

30 State Street, Cambridge, Mass.

274 Brannan Street

San Francisco, Calif.

PROFESSOR HERMANN SCHNITZEL

Of the University of Cincinnati, O-ho-ho

has written a booklet containing 21 short radio lectures which have been broadcast from many stations. 50 cents per copy, postpaid. You will enjoy this book.

For sale by "RADIO," Pacific Building, San Francisco

ALL-SHORT-WAVE RECEIVER

(Continued from Page 42)

to a low value and the setting noted. A pair of grid-leak clips are mounted on it and a variable grid leak is best, although 5 megohms is the usual value.

A 112 used as detector oscillates easily at the highest frequencies. No tube-socket is used, since different tubes change things so much. The set ought to be built around the particular type of tube employed. Holes are drilled through the bakelite and the leads are soldered in place. Should another tube be necessary, the 112 is easily removed as it is at the rear of the set.

No short-wave receiver should be without a filament switch, as best oscillation is always secured at some particular filament-setting. These tubes usually work best with very low filament and about 67½ volts on the plate; other tubes will sometimes require comparatively large values of tickler turns and often higher plate voltages. The correct adjustment of the set, for the higher frequencies, is important and will require some experimentation for values giving best results.

The arrangement of apparatus is convenient for the experimenter as the filament rheostat and switch, phone jack and audio amplifier are mounted on a separate panel. All parts are arranged so that they can be used separately.

The whole set is mounted on a heavy base-board and is supported above it. The 4½-volt C battery is mounted underneath. Dry cell tubes can be used and the set made semi-portable; it is a simple matter to mount the layout on the seat of the car and study the 5 or 10-meter signals at a distance from the station.

The audio transformers peak at 1000 cycles and the set therefore gives best response at this audio frequency. There are still AC signals on the air so that a very selective audio amplifier would hardly be desirable yet, especially for all-wave use. In this amplifier, the better signals are received with excellent results and extraneous noises are greatly reduced. Often one can "tune" an audio transformer to about the correct value by using condensers across the windings; some transformers are designed for peaks in the audio range.

The selection of proper midget condensers is important, as many types are not so good. If these are of the one-bearing type, this bearing should be well-constructed and about this the amateur knows. These condensers will eventually replace the larger sizes for most short-wave uses. Almost a whole set of these may be obtained for the price of the usual large instrument. They are as good electrically, if not better, than the larger sizes, especially at the higher frequencies as shown by repeated tests at 5 and 10 meters.


The coils can be celluloid-supported and No. 20 wire is about right for the well-spaced turns. The 5-meter coil consists of about 2 heavy turns on a 1-in. diameter, and the 10-meter one is about double that; at 40 meters, 18 or 20 spaced turns is about right, but the values are not critical because the shunt condenser will compensate. Large coil diameters for 5 and 10 meters should be avoided as movement of the body then has considerable effect on regeneration.

Fixed filament resistors are used in the audio amplifier. To use the set without r.f. amplifier, the antenna is connected directly to a lug on the secondary condenser through a small midget. The output of the r.f. amplifier may be similarly connected; it is perhaps better to use separate batteries for the r.f. amplifier but one will work all right with the same batteries for the whole layout. Often the tube will oscillate much better if the filament leads to the detector are reversed.

The actual wave-change caused by supposedly small effects is too large. In the usual

amateur wavemeter employing a flashlamp indicator, the wave may be changed as much as $\frac{1}{2}$ meter at 40 meters by simply changing lamps or shorting a given lamp in or out. Such changes are too large for 1929 conditions. There are perhaps only two arrangements which are practical for average amateur use.

One of these consists of the tuned circuit described above to which is coupled a 2-turn loop (at 40 meters) including a flashlamp in series. Some flashlamps give very broad tuning, but tests show that the 1.25-volt type ("S" filament) is about the best to use, as the filament cools rapidly and gives a sensitive indication. If the main inductance consists of about 18 turns on a 2-in. tube, this 2-turn loop should be set at about $\frac{3}{4}$ in. from it. Indications will be quite sharp, and with loose coupling, the effect of the lamp circuit causes very little tuning effect. The lamp when turned into, or out of, the socket will have a small effect on the wave, but if left in place, will give good results and tuning will be sharp.

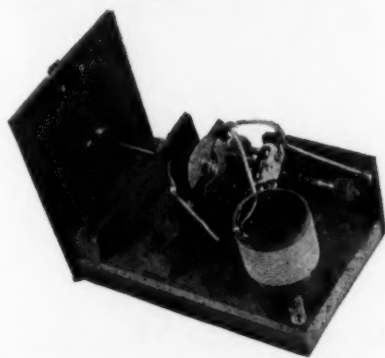

Wavemeter with Neon Tube Indicator

An accurate wavemeter is necessary for calibrating the set. The picture and circuit diagram in Fig. 2 show one using a neon lamp as a resonance indicator. It uses a 15 mmfd. midget tuning condenser cut down to three plates and a 20-turn coil, which is wound on a threaded length of 2 in. bakelite tubing. A 50 mmfd. midget condenser is shunted across the tuned circuit.

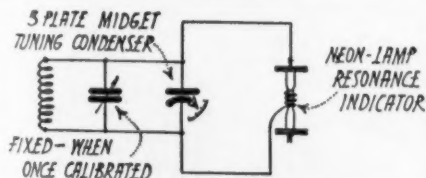


Fig. 2. Wavemeter Circuit Diagram

The condensers are mounted on a hard rubber strip which, together with the panel supporting the vernier dial, is securely fastened to heavy baseboard blocks. A small extension handle eliminates the necessity of shielding. The threaded tubing is secured to the baseboard by small metal angles at the base. Heavy copper wire is used for connections.

The neon lamp should be of 5-watt size or larger. It is somewhat more sensitive if one terminal is left open and a length of copper wire, wound around the middle, is used as the other. The lamp is securely fastened to a bakelite piece and is held by a piece of wire passed around the lamp and through holes.

For accuracy, it is best to have a separate instrument for the 40-meter band. The small condensers are economical and at small expense accurate instruments can be constructed for 20 and 40 meters. The 10-meter band is wide and accuracy is not as important.

To calibrate the wavemeter accurately, the transmitter can be operated without an

Positive Line Voltage Control Safe

PROTECT your A.C. tubes from excessive filament voltage and insure maximum efficiency from your new A.C. receiver, which is designed to operate at a certain specified line voltage. To be safe, you must have some means of controlling the voltage from the light socket,



PRICE \$3.00

which varies in different localities and during certain times of the day.

The Centralab Radio Control Box is the most advanced form of voltage regulator. It is so designed that it will provide absolute positive and safe control of line voltage. A simple manual control is the only adjustment. No meters or technical knowledge required to operate, although meter can be attached at little extra cost if desired.

26 Keefe Avenue

Centralab
CENTRAL RADIO LABORATORIES

Milwaukee, Wisconsin

TELEVISION

although still in an experimental stage, has now advanced sufficiently to enable amateurs to build outfits that will give edifying results.

Write today for our price list of television apparatus.

Photo Electric Devices, Inc.
594 Fifth Ave. Brooklyn, N. Y.

Gerald Best's SUPER BLUE PRINTS

The complete working plans in full size for building the new incomparable Gerald Best 115 Kilocycle superheterodyne with full instructions for building.

Per set. Postpaid anywhere in the U. S. Send remittance by cash, check or money order. Stamps also accepted. "RADIO," Pacific Bldg., San Francisco, California.

25c


Free

A Continental Control Switch will be given free with a one year subscription to RADIO (\$2.50) if you act immediately. Only a few on hand.

"RADIO"
Pacific Building San Francisco

Marvelous Reception

Full tone over the entire receiving range by equipping your Power Amplifier with a Potter Condenser Block.

No. T2900 where one 250 Type Power Tube is used		No. T2950 where two 250 Type Power Tubes are used
\$20.00		\$22.50

Highly Efficient—Long Life

The Choice of Leading Radio Engineers

Ask your dealer for full information

POTTER MFG. CO.
North Chicago, Illinois

LAST MINUTE SPECIALS!

E210 BRADLEYSTATS, list \$4.00	Our Price \$1.60 ea.
MESCO Wireless Keys, list \$2.00	" 95c ea.
U. S. ARMY Aeroplane Spark Transmitters, Gov. cost \$47 each	" 4.75 ea.
G. E. Kenotron Rectifying Tubes (type T.B.1)	" 1.25 ea.
Eby A.C. Adapter Harness with Volume Control. For 6 tube Sets, list \$10.00	" 5.00 ea.
Gould Kathanode Unipower, Automatic Radio "A" Power (6 volt), list \$39.50	" 13.75 ea.

AMERICAN SALES CO., 19-21 WARREN ST., NEW YORK CITY

Tell them you saw it in RADIO

AMERTRAN PF-250 Power Transformer for


UX 250 Power Tubes

A husky transformer built for doing the job, not for looks. The PF-250 is rated at 1200-600 volts plate, 7½ volts power tube, 7½ volts rectifier tube filament. Center taps are provided on each of the filament windings. Continuous rated capacity of plate windings, 160 MA., continuous rated capacity of each 7½ volt winding, 3 Amperes. DC plate output with two UX 281's full wave, up to 450 volts with sufficient excess for "C" Bias.

Ask for Bulletin No. 1033 describing fully the PF-250.

Price, each—\$30.00
Slightly higher West of Rocky Mountains

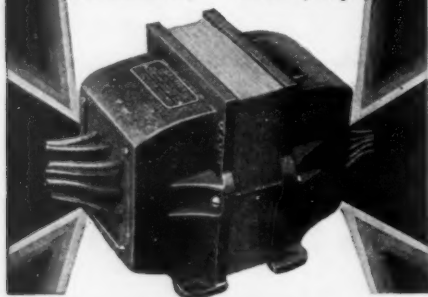American Transformer Co.
Transformer Builders for more than 25 Years
274 Emmet St., Newark, N. J.



CUSTOM SET BUILDERS


Browning-Drake has an interesting and unusual proposition. Take advantage of the fact that more Browning-Drakes are built than any other. Write today.

BROWNING-DRAKE CORP.
CAMBRIDGE, MASS.

CARDWELL CONDENSERS

The Taper Type
Type "E"
Cardwell

Unexcelled
for Short Wave
Receivers

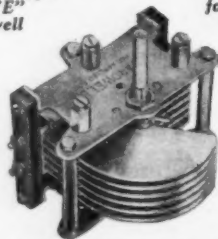

STABILITY Is Vital

In the short wave receiving circuit. The effect of a rising and falling note so often troublesome in CW code reception, due to instability in the circuit, will obviously play havoc with Broadcast Reception on the short waves, if at all pronounced.

CARDWELL TAPER PLATE CONDENSERS are rigid and vibrationless and will absolutely hold their calibration, thus eliminating one of the important causes of circuit instability in short wave receivers.

The tuning curve is ideal, midway between SLW and SPL, attained without eccentrically shaped plates, thus concentrating the weight of the rotor close to the shaft. It will pay you to investigate.

Transmitting Condensers for powers up to 50KW and more. Receiving Condensers in all standard capacities. Send for literature.

The Allen D. Cardwell Mfg. Corp.
81 Prospect Street
BROOKLYN, N. Y.

"The Standard of Comparison"

antenna with a very small input, and so a harmonic falls exactly on the wave of a broadcast station which has been carefully tuned in with any ordinary nearby regenerative, broadcast receiver. By using different stations, various points on the wavemeter calibration-curve are easily obtained. The wavemeter in each case is checked with the wave of the transmitter, the wavelength of which is calculated from the broadcast frequency by dividing by the proper whole number.

Operation is simplified by using a sensitive grid d.c. milliammeter in the transmitter in series with the grid leak. For a 210 tube, this meter ought to be about a 0/25 size. Resonance is denoted by the dip of the grid meter. Several check points should be used and the average curve taken.

The transmitter must also receive special attention for 1929 conditions. It should be sharply tuned and not "modulated" by a poor plate supply, giving the usual broad wave. Good d.c. plate supply will help considerably. Many amateurs may desire to operate with small "99" transmitters. These are quite cheaply constructed and give exceptional results in these days of sensitive, screen-grid r.f. receiving systems, like the one described.

The average amateur transmitter is too closely coupled to the antenna. A broad interfering wave is caused and operation in two frequencies, close together. With loose coupling, the wave is sharpened, transmission is on only one frequency, the note is improved, and the antenna system has less effect on the oscillating circuit, reducing considerably, any "wobbling" effects. One should use a large capacity in the oscillating circuit, which usually eliminates "creeping." If the tubes are run cool, this effect is greatly reduced. Any circuit, when properly adjusted, gives a good constant oscillating frequency.

Since bringing up a tuned antenna circuit to the primary changes the plate current and therefore the tube temperature, the value of coupling will have some effect on the frequency of the transmitter. The coupling depends on so many factors that a general rule cannot be given; if one adjusts the coupling so that 85 or 90 per cent of the antenna current is obtained with close coupling, good results will be secured. The note should be studied near the set and is affected to some extent by antenna tuning. In general, any change in the transmitter which changes the plate current value will have an effect on the frequency and any such will have less chance, if a low LC ratio is used.

If all amateurs in the 40-meter band would use direct current plate supply, operation would be improved because of the sharp waves. The high-pitched notes would encourage the use of peaked audio amplifier systems, thus reducing other interference and amplifying, to a maximum degree, the proper signal. A surprising number of such stations could operate without interference if both the transmitting and receiving systems were sharply tuned. The all-short-wave receiver here described is a step in that direction.

SELECTIVE SHORT-WAVE RECEIVER

(Continued from Page 42)

The r.f. choke consists of 300 turns of No. 36 wire, scramble-wound on a 1-in. core. A .00025 mfd. oscillator grid condenser C_5 and 1 megohm grid leak R_1 lowers the plate current somewhat. The condenser C_7 is of .002 mfd. capacity, C_2 .0005 mfd., C_3 1 mfd. and C_4 .0005 mfd.

The filaments are all controlled by one 6 ohm rheostat R_2 . Sockets are mounted on sponge rubber cushions to prevent microphonic noises. All parts are mounted on a 7 by 18-in. panel.

Tell them you saw it in RADIO

"DRESNER" SHORT WAVE CONVERTER



Complete
\$22.50
Special

Wave
Length
Range
15 to 550
Meters

SIMPLE TO ATTACH— EASY TO OPERATE

Some of the best entertainment of the air is broadcast on the short waves by many powerful stations. There is no longer any reason why all should not receive these excellent programs from all over the world. The Dresner Short Wave Converter Unit is completely assembled. It efficiently covers a wave band of 15 to 550 meters, and makes reception easily obtainable for all. Offered at the special price of \$22.50—complete ready to plug into your receiver in a few seconds.

If your dealer cannot supply you, send money order direct and we will ship P. P. Prepaid. Guaranteed.

(When ordering unit, be sure to specify whether it is to be used on AC or DC set.)


Dresner Radio Mfg. Corp.
642 Southern Blvd. New York City
Dept. F

ENJOY THE THRILL OF ELECTRIFIED RADIO at SMALL COST

only
\$6.85
complete
FREE TRIAL

Banish forever all the annoyance and expense of buying new "B" Batteries with a TOWNSEND "B" POWER UNIT. Hooked up in a few moments—and you have permanent power from your light socket from that time on. Use same tubes now in your set. No changes.

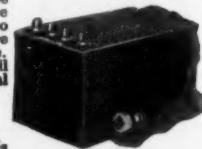You'll be amazed at the way Townsends improve your reception and add to distance getting. More than 50,000 now in use. Send Coupon today for full information and free trial offer.



TOWNSEND
LABORATORIES
Chicago Illinois

COUPON
TOWNSEND LABORATORIES 11/28
Dept. 18, 713 Townsend St., Chicago, Ill.
Please send me full information on the Townsend "B" Power and Free Trial Offer.

Name.....
Address.....

Send for New Radio Book—It's Free!

New hook-ups. This book shows how to make short-wave receivers and short-wave adapters. How to use the new screen grid tube in D. C. and A. C. circuits. How to build power amplifiers, ABC eliminators. Up-to-the-minute information on all new radio developments. It's free. Send for copy today.


KARAS ELECTRIC COMPANY
4031L2 North Rockwell St., Chicago, Ill.
Portland, Oregon, 53 4th St.
San Francisco, 585 Mission St.
Los Angeles, 324 N. San Pedro

Name.....
St. and No.....
City and State.....

4031L2

AERO KITS

You Can Build
Better Than You Can Buy

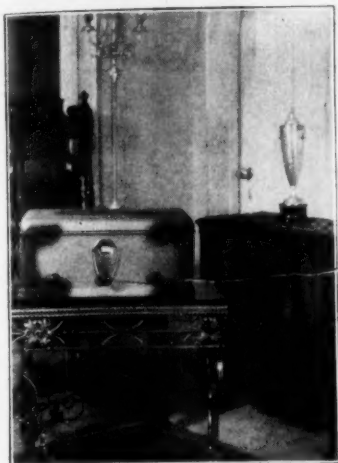

Aero "CHRONOPHASE"

The Aero "CHRONOPHASE" principle in Radio Frequency Amplification is the first outstanding development in broadcast reception since the introduction of the neutrodyne. Now selectivity takes on new meaning, for sets employing this principle can be made so selective that even the side bands of local broadcasting stations can be cut off. Greater distance range, too, is achieved with remarkable smoothness of control. No factory-built set has the new and revolutionary "CHRONOPHASE" principle. It may be had, however

In Three Wonderful Receivers

The 1929 six-tube "Aerodyne," the Aero Seven-Twenty-Nine and the five-tube Aero "CHRONOPHASE" all incorporate the "CHRONOPHASE" circuit. Complete kits for these receivers may be had from your dealer. No expense has been spared to make these kits the finest you can buy. A beautiful two-tone metal cabinet is a part of each kit. Every part needed for the construction of the receiver is included—even wire, soldering lugs and wood screws—so that nothing more need be purchased. Anyone can assemble an Aero receiver in a few hours. Panels are drilled, which insures proper placement of parts and full-size pictorial wiring diagrams eliminate mistakes in wiring. Aero sets can be built for A.C., D.C., or Shield-Grid tubes.

A postcard request brings two valuable booklets introducing the new 1929 line of Aero kits and describing the 64 page Aero Green Book for 1929. Send to

AERO PRODUCTS INCORPORATED

Dept. 588, 4611 E. Ravenswood Ave.
CHICAGO, ILL.



Console Model. A beautiful walnut finished cabinet, furnished in 6-tube and 7-tube push-pull. Equipped with "Peerless" Speaker.

Size 26"x40"x16" deep.

Your Own Label On This Radio

Your Best Business Builder!

There's no business-builder in the world like a good radio in action! And no radio can deliver better than the Premier. Put your private label on it—and get ALL THE BUSINESS THAT IT BUILDS!

Private-label radio brings you longer profits; its flexible price meets any kind of competition or market; it frees you from top-heavy inventories and territorial contracts; you order only what you need. And—private-label radio preserves your trade identity, your most valuable possession.

Material and manufacture—not advertising!—determine the quality and salability of a receiver. Premier Private-Label Radio is equal to any on the market in performance, looks, quality and salability. Table, console and combination models,—furnished standard in 6-tube and 7-tube Push-Pull.

CHASSIS SPECIFICATIONS

All-metal chassis; rigid, strong, stays put. Unconditionally guaranteed. Apparatus 100% shielded. Licensed under U. S. Navy Patents and Hogan Patent No. 1,041,002.

Write for price and full details.
No obligation.

PREMIER ELECTRIC COMPANY

Established 1905—Manufacturers Ever Since
3841 Ravenswood Avenue
CHICAGO, ILLINOIS

Helps You Pass Government Radio Examination


An Excellent Book
"PRACTICAL RADIO
TELEGRAPHY"

380 Pages

\$3.00 SENT TO YOU
POSTPAID

"RADIO"

Pacific Bldg. San Francisco, Calif.

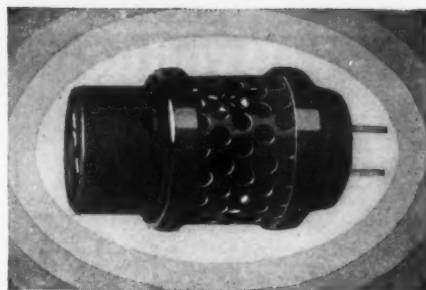

\$2.00 Insures
Your A.C. Tubes

The Vitrohm 507-109 Unit costs \$2.00. Installed on your radio set, it lengthens a. c. tube life by automatically lowering filament voltage.

Attached in a moment—Nothing combustible—Nothing to wear out—Does not get excessively hot.

It consists of a Vitrohm Resistor mounted within a perforated metal cage, a plug, and a receptacle.

Write for free information on this and other Ward Leonard Radio Products.

WARD LEONARD MOUNT
ELECTRIC CO. VERNON
NEW YORK

ANOTHER ACHIEVEMENT



by
Dr. Lee

DeForest

With the same creative enthusiasm that produced the first radio vacuum tube (1906) Dr. DeForest has now developed the perfected Audion.

When you replace your tubes with DeForest Audions you will experience a new enjoyment in clarified reception.

Send today for your free copy of the interesting booklet by the "Father of Radio."

DeForest Radio Co.
JERSEY CITY ~ N.J.


Tell them you saw it in RADIO



Tune More Sharply

Bring your set up to maximum sharpness with X-L Vario Densers

Practically all of the popular high grade circuits now use X-L Products. Perfect reception is always assured because of the accurate values and dependable service these well known products give. Endorsed by leading radio engineers, designers and builders and standard in most quality sets. Broad and positive capacity range that assures exact oscillation control easily obtained with both Model "N" and Model "G" Vario Densers.

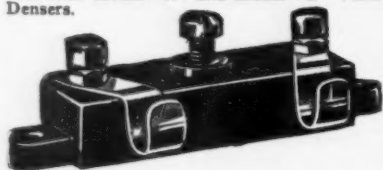

Model "G" Vario Denser

Genuine Bakelite casing, dust and moisture proof. All metal parts phosphor bronze nickel plated. Only the best imported India mica used. Extreme micrometer capacity advance, exceptional accessibility in close quarters. Model "N" has variable capacity adjustable from 1.8 to 20 micro-micro farads. Price each, \$1.00.

Model "G" with grid clips made in three variable capacity ranges, viz: Model G-1, .00002 to .0001 Mfd.; Model G-5, .0001 to .0005 Mfd.; Model G-10, .0005 to .001 Mfd. Price each \$1.50.

New BAKELITE INSULATED

X-L PUSH POST

The most perfect binding post made. Push down with thumb, insert wire, remove pressure, wire is held firmly. Vibration will not loosen but releases instantly when you wish. No chance to forget to tighten. Positive, permanent. Plain or all standard markings. Also made in all-metal design. Price each 15c.

Strip of 7 on black panel with white markings, price \$1.50.



X-L Push Post

Write for interesting and valuable free copy of our new up-to-date book of wiring diagrams showing use of X-L units in all leading circuits.

XL Radio Laboratories

Dept. J, 1224 Belmont Ave., Chicago, Ill.

TECHNICAL BRIEFS

(Continued from Page 38)

with transformers having $\frac{1}{2}$ -in. and $1\frac{1}{2}$ -in. primaries, for 9, 18 and 36 turns each. The screen-grid tube circuit connections for each type are shown in Fig. 3, *a* showing the transformers and *b* the autotransformer.

The $1\frac{1}{2}$ -in. primary type is that generally advocated for use with a shield-grid tube when a tuned impedance is not employed. It will be noticed that there is little gain in amplification when more

and a consequently greater overall amplification. As the number of turns is increased in the portion of the secondary which acts as a primary, the amplification on the higher frequencies is reduced because the two currents in this portion of the coil are in quadrature, and the voltage in the grid of the next tube is consequently lower. This can also be used in a multi-stage amplifier to secure uniform amplification over the entire spectrum without so greatly impairing the selectivity.

The selectivity curves for these three

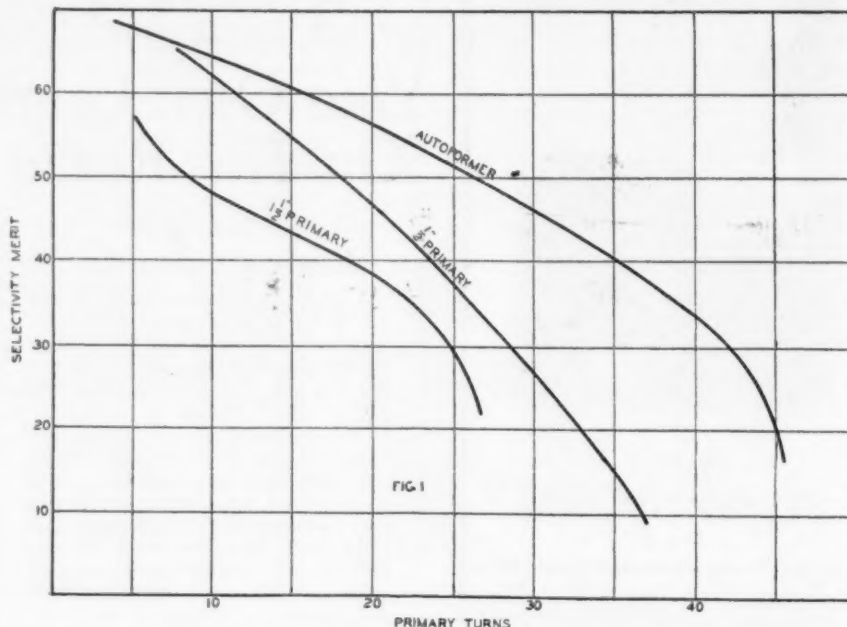


Fig. 4. Selectivity Curves for Three Types of Transformers

than 18 turns are used, thus impairing its possibilities for selectivity.

With the $\frac{1}{2}$ -in. primary a variation in the number of turns changes the point where maximum amplification is secured. Hence with a multi-stage cascade amplifier uniform amplification can be secured over the whole band by adjusting the number of turns in the primary of each transformer, although this may result in sacrificing the selectivity of one or two stages.

As the inductive coupling is much greater with an autotransformer, a few turns will give a high primary impedance

types of transformers, are shown in Fig. 4. The figure of merit considers the inverse ratio of amplification obtained at the mean of frequencies 50 k.c. distant from the oscillator frequency, plotted against a percentage cutoff at seven-tenths of the maximum. A selectivity factor of 50 is fair, 55 is good, and 60 gives an extremely desirable point. It will be noticed that at 350 meters, for example, this selectivity figure can be obtained with the autotransformer circuit with an amplification figure of 5.7, whereas the corresponding $\frac{1}{2}$ -in. primary is secured with an amplification

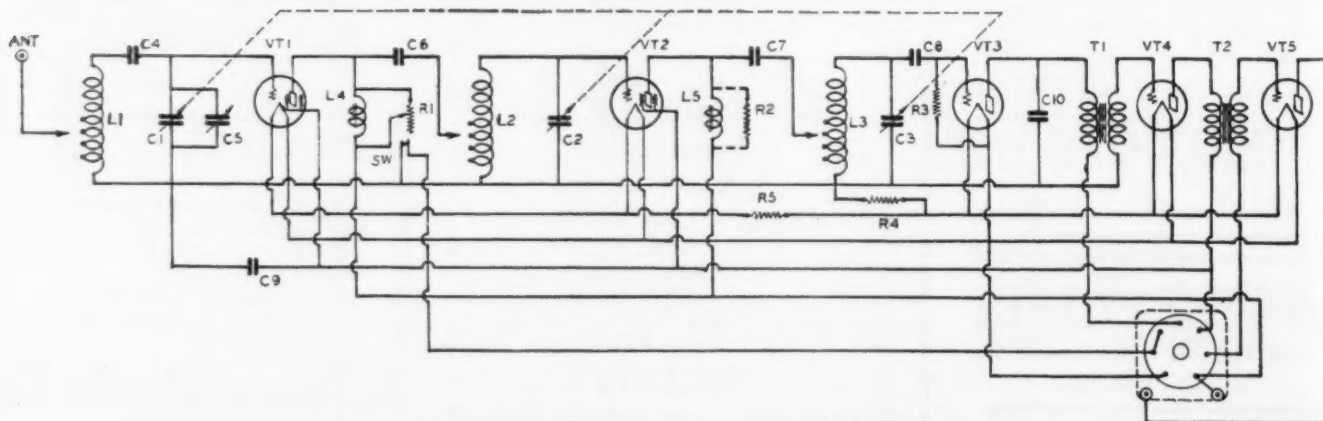


Fig. 6. Chronophase Circuit with Two Screen-Grid R.F. Stages

Philadelphia Your Choice Should Be The HOTEL MAJESTIC BROAD ST AND GIRARD AVE.

400 LARGE ROOMS

Only Hotel in Philadelphia with a
subway entrance from main lobby.

MOST MODERATE RATES!

Single room, running water	\$2.00
For two	\$3.50
Single room, private bath	\$3.00
For two	\$5.00-\$6.00

Garage Connected with Hotel

Wire at our expense for Reservations
JNO. C. GOSSLER, Mgr. Dir.



SPINTITE WRENCHES FREE

With a one year subscription to
"RADIO"

3 Stevens Spintite wrenches for round nuts given free this month with a subscription to "RADIO." Send \$2.50, get "RADIO" for one year, and the wrenches also. We pay the postage. Only a few sets of these wrenches still on hand. Hurry.

Publishers of "RADIO"

Pacific Bldg. San Francisco

Your Tubes STEADY AS THE STARS When AMPERITE-Controlled

Don't let "A" battery current fluctuations spoil your radio reception or ruin your tubes. Install Amperites and automatically keep the filament temperature constant according to tube rating. Entirely unlike fixed resistors. With AMPERITE control tubes last longer and your set sounds better. Panel arrangement improved and wiring simplified. Tuning is easier and volume is increased. A type for every tube—battery or A. C.

\$1.10, with mounting (in U. S. A.) at all dealers.
Radiall Company
50 FRANKLIN ST., NEW YORK



AMPERITE
The "SELF-ADJUSTING" Rheostat

of only 3.6, or about 65 %. In this particular instance the superiority of the autoformer type is outstanding.

Oscillation was frequently encountered, even in connection with the supposedly non-oscillating shield-grid tube, unless some means were taken to prevent it. The best results were obtained by shifting the phase angle of the currents in various stages by the method illustrated in Fig. 5.

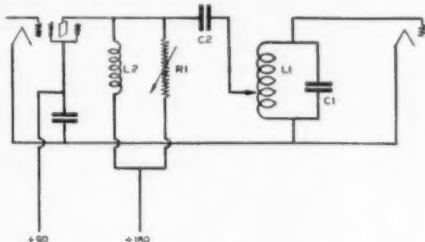


Fig. 5. Chronophase Circuit

An inductance L_2 of comparatively low d.c. resistance was shunted around the resistance R_1 , maintaining a maximum static value of plate voltage at the tube, while offering a very high impedance to r.f. currents. The resistance R_1 can be varied without affecting the static value of the plate voltage and will be found to serve as an oscillation control. If provision is made so that it can be reduced to a low value, so as to effectively short-circuit C_2 , it can also be employed as a volume control.


In a circuit containing two stages of radio-frequency amplification, it will rarely be found necessary to employ more than one such resistance, as sufficient adjustment of the time relation can be obtained to avoid oscillation while still maintaining the satisfactory value of overall amplification. Maximum results, regardless of the type of tube used, can be obtained by varying the proportion of L_1 which is used in the plate circuit of the preceding tube. Little trouble was experienced from inductive coupling between coils.

Shielding always introduces certain losses in the coil, due to linking a portion of the coil's field, and also complicates the mechanical construction of the receiver. It will be seen from the curve that the necessity of shielding is mitigated as far as interstage coupling effects go, while the diameter of the coil is so small that direct pick-up from local stations is reduced to a minimum, as has been demonstrated in practice.

One such receiver using two stages of tuned radio-frequency amplification with shield-grid tubes, employing the "Chronophase" system, has been given an exceedingly thorough tryout. On a 25-ft. aerial located on the shore of Lake Michigan, in the heart of the most congested mass of broadcasting stations in the world, it has been possible to cut through locals and secure good loud speaker reception of stations a thousand miles distant.

Tell them you saw it in RADIO

YEARS Ahead!

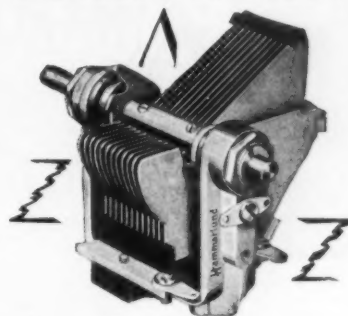

The HAMMARLUND "Midline" Condenser

Condensers come and condensers go, but the Hammarlund "Midline" keeps ahead.

Built with watch-like precision and embodying every feature demanded of a modern tuning instrument, the Hammarlund "Midline" Condenser continues to make radio history.

If you know radio, you know Hammarlund. If you are a beginner, ask any radio engineer his estimate of Hammarlund Products. Follow his advice.

Write for Folder

Hammarlund Manufacturing Co.

424-438 W. 33rd St., New York

For Better Radio
Hammarlund
PRECISION
PRODUCTS

\$1.00 Brings you the next 6 issues of "RADIO"

'B' BATTERY ELIMINATOR

Only **\$5.95**

MONEY-BACK GUARANTEE

No more worry with "B" Batteries! Hook up an R. B. "B" Battery Eliminator and forget battery troubles forever. This wonderful new invention means better reception, sharper tuning. Gives you more real pleasure from your set.

COMPLETELY EQUIPPED— No "Extras" to Buy

Operates perfectly on direct or alternating current giving up to 90 volts current, and using the full wave of the power supply. Simple directions enclosed—anyone can plug it into any kind of set up to six tubes. Constant voltage gives set more power. Costs no more than set of good "B" Batteries. Solidly built in beautifully finished metal case, with genuine Bakelite top.

SEND YOUR ORDER NOW


Don't blame your set because run down "B" Batteries won't let it work right. Order your Eliminator NOW. Write name and address on a piece of paper, plus a dollar bill to it, and mail it TODAY. Pay postman balance (\$4.95 plus a few cents postage) when he delivers your Eliminator. Use it ten days. If not more than satisfied, return it and get your money back.

135-Volt Eliminator Only \$7.95

New style Eliminator that gives amazing performances. Send \$1.00 and pay balance of \$6.95 (plus postage) on delivery. Guaranteed to please—or money back. Be sure to ask for 135-Volt Eliminator.

THE R. B. SPECIALTY CO.
Dept. D-304, 318 Sycamore St., Cincinnati, O.

FREE 3 DAY TRIAL WITH

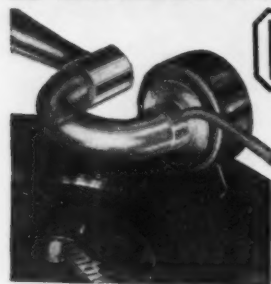

NA-ALD
TRADE MARK
REG. U.S. PAT. OFF.

NEW ELECTRIC PICKUP

With a NA-ALD Electric Pickup and a good radio set or power amplifier you can electrically amplify the music from

phonograph records and get the results of talking machines costing several hundreds of dollars. The new NA-ALD Pickup fits A.C. or battery sets. It is equipped with twin magnets giving a full, rich tone quality on both high and bass notes. Every set owner should have one. You may try a NA-ALD Pickup for three days and if not satisfied return it and get your money refunded.

ALDEN MANUFACTURING CO.
Brockton, Mass. Dept. R1

END RADIO BOTHERS

DO YOU KNOW what's wrong when your radio set isn't working right? Ten to one, you don't. Twenty to one, you would if you had a copy of

Hoff's Radio Trouble Finder

Ever hear of M. M. Hoff, radiotician, of Philadelphia? He was one of the very first "radio bugs" and has been building and studying sets ever since. And now, out of his broad experience, this man has written a book to tell radio owners how to keep their sets working right.

He tells in plain words and illustrations how a set is made, what the parts are called, what are the few usual troubles and how to fix them. Then he lists 103 troubles that sometimes happen and tells how to detect and fix each one.

The book is a regular cyclopedia of radio information—only it's in a language anyone can understand. Read it five minutes and you'll know more about radio than you ever dreamed of.

It will save you many a repair man. It will save you hours of guessing and fussing and fuming. It will help you to keep the tone of your set always sweet and strong. It will keep you from losing many programs. And, best of all—

IT WILL MAKE YOU STOP SWEARING—MUCH TO THE SURPRISE OF YOUR FAMILY— because radio repairs are expensive. Why hire them done when you can easily learn how to keep your set from needing them?


All It Costs Is \$1

Send cash with your order and you get also a Dictionary of Radio Terms and the latest list of Radio Broadcasting Stations with call letters and the new Federal Radio Commission wave lengths. Send your dollar today while the copies last. Six copies for \$4.00.

CHICAGO BARGAIN STORES

426 Quincy Building, Desk 5 Chicago, Ill.

INTERESTED IN TELEVISION?

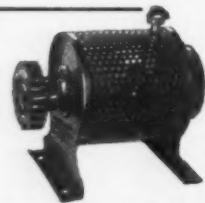

motor from standstill to full speed; pushbutton for quick start and momentary acceleration; 25-500 ohm fixed or variable resistance.

Clarostat Mfg. Co., 285 N. 6th St., Brooklyn, N.Y.

**SPEED CONTROL
CLAROSTAT**

\$1.00

Brings the Next Six
Issues of "RADIO" to
your address

RADIO KIT REVIEWS

(Continued from Page 44)

THORDARSON PHONOGRAPH AMPLIFIER


This two-stage all-electric amplifier using a 210 power tube, converts an old style mechanical phonograph into a modern high quality electrical reproducing machine. In addition to the revolving turntable and electrically recorded records, it requires only a good pick-up unit and the easily assembled equipment listed in this kit to get faithful reproduction of audio frequencies from any good radio speaker.

The amplifier is operated completely from alternating current and is so constructed that it is readily portable. It is exceedingly

furnish to the voltage divider, direct current free from hum.

Filament current for the first audio-frequency tube is supplied by the current flowing through the voltage divider. When the 100-volt field of the dynamic speaker is connected to the terminals marked "Field," about 60 milliamperes will flow through the field windings of the dynamic speaker and will be available for heating the filament of the 199 tube.

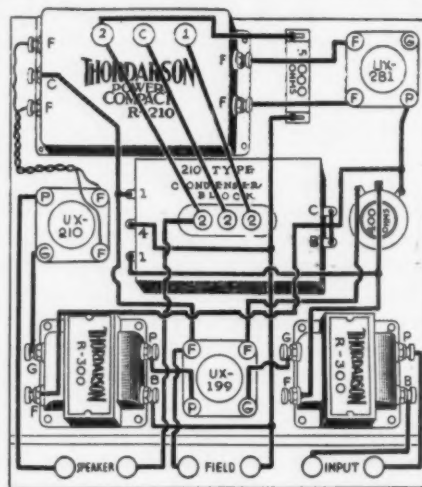The plate voltage applied to the plate of the 210 power tube is 385 volts, secured through the voltage drop of the 5000-ohm resistor and the field of the dynamic speaker.



*Pictorial Wiring Diagram of Thordarson
Phonograph Amplifier*

compact, being 10x10-in. and may be placed in one of the compartments or in the tone chamber of the phonograph so that no unsightly or difficult connections to the radio receiver are necessary.

The power transformers and filter chokes are completely housed in the Thordarson R-210 Power Compact. This unit furnishes power for the high voltage supply to the plate of the 281 rectifier tube, power for the filament of the same tube, as well as power for the filament of the 210 power tube. The rectifier and filter circuits are conventional, and

The grid bias of 25 volts is secured through the voltage drop through the filament of the 199 tube and the 400-ohm potentiometer. The plate potential for the 199 tube is taken from the high voltage side of the power field of the dynamic speaker, about 125 volts. The grid bias for the 199 tube is obtained from the voltage drop between the filament side of the 400-ohm potentiometer and the movable arm. The arm should be adjusted for best results. The undistorted output of the 210 power tube operating under the above conditions is about 1200 milliwatts.


In view of the fact that dynamic speakers have incorporated in their assembly an output transformer, none is needed in the amplifier itself. It is to be noted at this point

LIST OF PARTS

- 1 Thordarson R-210 Power Compact
- 2 Thordarson R-300 Audio Transformers.
- 1 210 Condenser Block (Dubilier, Tobe, Potter, Acme, Aerovox, Fast, Splitdorf).
- 1 Electrad Fixed Resistor, 5000 ohms, Type B.
- 1 Yaxley 400-ohm Potentiometer.
- 3 Benjamin Sockets (Sub-panel).
- 6 Binding Posts, 2 Input, 2 Speaker, 1 Pos., 1 Neg.
- 3 Benjamin Sub-panel Brackets.
- 1 P.C. Bakelite 10" x 10" x 1/4".
- 1 P.C. Bakelite 10" x 2" x 3/16".

TUBES

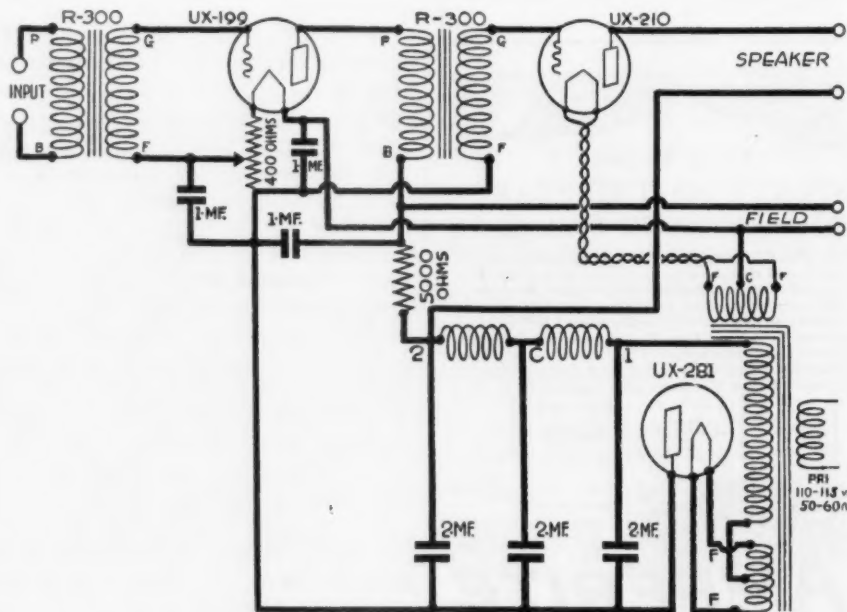- 1 UX-281 Rectifier.
- 1 UX-210 Power Amplifier.
- 1 UX-199 Amplifier.




Circuit Diagram of Thordarson Phonograph Amplifier

Tell them you saw it in RADIO

that the type of dynamic speaker used must be of the high-voltage field type.


If for any reason it is desired to use this amplifier with other than the dynamic type of speaker it will be necessary to use an output transformer, for the current output of the 210 tube is apt to burn out the fine wire windings of the speaker. The primary of this transformer should be connected to the two terminals marked "Speaker" and the loud speaker should be connected directly to the secondary of this transformer. It will also be necessary to compensate for the field current of the dynamic speaker. This may be done easily by inserting a 2500-ohm resistor in place of the field, that is, connect the resistor to the two terminals marked "Field."

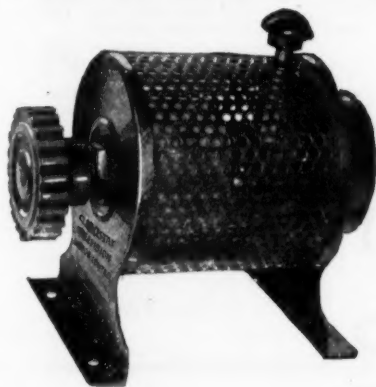The Television Clarostat comprises a special power type clarostat, together with a short-circuiting push-button, contained in a sturdy, ventilated, metal housing with mounting feet. The device has a resistance range of from 25 to 500 ohms, or sufficient for the



required range of speed. It dissipates up to 80 watts, and is capable of controlling either a universal or a condenser type motor, on a.c. or d.c., up to $\frac{1}{8}$ horsepower.

The new REL variable condensers for use in short-wave receivers and wavemeters, as well as low-power transmitters, are ruggedly constructed with heavy brass plates and have a rigid three-point mounting which eliminates vibrations. They can be mounted on a metal panel without necessarily grounding either the stator or rotor plates. The rotor shaft is immersed in a pool of mercury inside the one-piece bearing, thus giving positive contact. The stator plates are shaped so as to prevent an increase in capacity when the rotor plates pass the point at which the stators are joined together. These condensers are made in various capacities, depending upon the number of plates. The three-plate

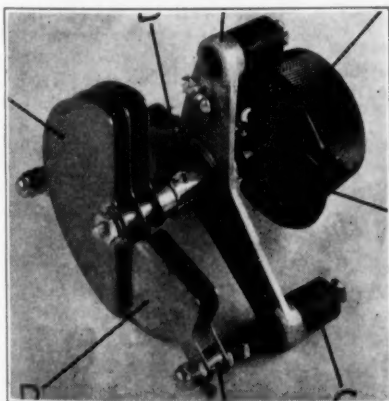

model illustrated has a maximum capacity of 54 mmfd. The capacity of the two-plate model may be regulated by moving the stator plate, thus giving a widespread tuning range.

A CROWNING ACHIEVEMENT IN A-C TUBES

Arcturus has it—a "heater type" Power Amplifier No. 071H!

The whole radio world has been waiting for an "Indirectly Heated Cathode" type '71 tube to eliminate troubles inherent in the "filament type."

Now—you can experience the newest in radio—a revelation in radio reception. Put an Arcturus "heater type" tube in every socket. Note the clear, undistorted volume, the better tone qualities, the quicker reception, the extremely

(An unbiased
view of FACTS)

long life, the immunity to current surge—all the requisites for a

perfect A-C tube.

Nowhere else can you get these advantages except in "heater type" tubes. Leading set manufacturers, recognizing this, are using "heater" tubes throughout their receivers.

You can adapt this greater efficiency to your receiver by using a complete set of Arcturus "all heater type" tubes in every socket. Get a set from your dealer today.

West Coast Distributors

**Universal Agencies, 905 Mission St.
San Francisco, California**

ARCTURUS

A-C LONG LIFE TUBES

Newest Radio Hook-Ups—FREE

Send now for the newest radio hook-up book. Shows how easy it is to build remarkable new A. C. and D. C. receivers of longest range, greatest volume, purest, clearest tone and super-selective. Also shows how to make short-wave receivers and adapters, how to use new screen grid tube in A. C. and D. C. circuits, how to build power amplifiers and ABC eliminators. Latest information on all new radio wrinkles. Send for free copy now.

KARAS ELECTRIC COMPANY
4031L1 North Rockwell St., Chicago, Ill.
Portland, Oregon, 53 4th St.
San Francisco, 585 Mission St.
Los Angeles, 324 N. San Pedro

Name.....
St. and No.....
City and State.....

4031L1

SET BUILDERS Get this Book

Barawik, the first and oldest radio specialty house, offers you unusual service this year. Bigger stocks, quicker shipments, lower prices. Deal with an old established, reliable house. Get honest goods, honest service, honest prices. Barawik service makes you more money. Send now for big new Catalog showing lowest wholesale prices.


BARAWIK CO. 1811 Canal St., CHICAGO, U. S. A.

Mail This Coupon Now for Free Radio Guide

Name.....
Address.....

Tell them you saw it in RADIO

POWER AMPLIFIERS

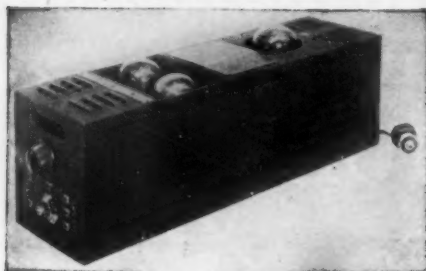

THE PX-2 POWER AMPLIFIER

is a two-stage power amplifier which can be energized from the detector tube of a radio set, providing sufficient volume for homes or small halls—frequently used for demonstrating records or speakers by dealers.

List price (tubes extra) **\$75.00**


Uses the No. 226 in the first stage, the No. 210 in the second and the No. 281 as rectifier—is provided with volume control.

POWERIZER P-4

This is a Powerizer which substitutes and contains 210 for the last stage and is easily and quickly connected to any radio set; specially adapted for use with dynamic speakers; uses a UX-210, UX-281. Furnishes its own A, B and C.

Price, less tubes **\$49.50**

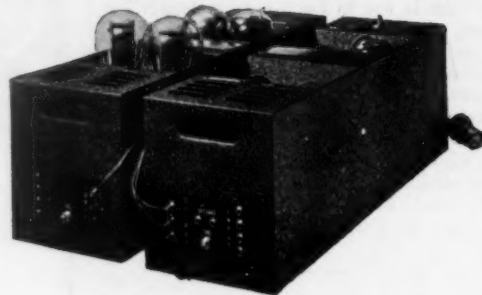The possibilities of making money from power amplification are unlimited. There is a demand in every city. Manufacturers, jobbers and dealers everywhere are converting their radios and radio phonographs into power amplified, A. C. Electrics, with this famous Powerizer Power Amplifier. Power Amplifiers used for demonstrating speakers—for auditorium volume.



POWERIZER PXP-250

is a very powerful three-stage push-pull amplifier. It is unique in that the amount of emerging amplification is unlimited, using our own system of sectional units. Push-pull 250 units may be added at will. Two units are sufficient to fill a house with at least 2,500 people; consists of one-stage UY-227, one-stage push-pull No. 171, and one-stage push-pull No. 250; has a tapped input and output. For tonal quality and power, this is the last word in power amplification. (Tubes necessary—one (1) UY-227, one (1) UX-280, two (2) UX-171, two (2) UX-281, and two (2) UX-250—tubes extra.)

List Price **\$250.00**

All of our units use alloy steel transformers, insuring maximum volume over the entire audible range. We would be very glad to handle any special problem that you may have on amplification.

THE PIONEERS IN POWER AMPLIFICATION HAVE IMPORTANT NEWS FOR YOU

Licensed by Radio Corporation of America and Associated Companies. Write for Bulletin PR-4

RADIO RECEPTOR COMPANY

Makers of the Famous

106 Seventh Avenue

New York City

POWERIZER

REG.



STRENGTH-INBUILT!

BENEATH the attractive exteriors of Aerovox Filter Condensers and Filter Blocks lies a sturdy framework built to withstand the onslaughts of voltage surges and unusual service conditions. A true example of Structural Strength—INBUILT!

Write for the Aerovox Research Worker, a free monthly publication containing many articles of paramount interest to you!

AEROVOX

"Built Better"

68-A Washington Street

Brooklyn, N. Y.

Two radio magazines for the price of **ONE!**

Hundreds and hundreds of readers of "RADIO" have availed themselves of our special money saving offer whereby you subscribe to two radio magazines for the price of one. "CITIZENS' RADIO CALL BOOK" and "RADIO"—both magazines sent to your address for a full year for the

price of a one year subscription to "RADIO"—\$2.50. The next issue of the "CALL BOOK" will be out on November first. Better subscribe now to avoid missing it. "RADIO" will be sent to you for 12 months, starting with our December issue, out on November 25th. Save \$2.50 by subscribing today.

MAIL COUPON NOW!

COUPON

"RADIO,"
433 Pacific Building,
San Francisco, Calif.

Here is \$2.50. Send me "RADIO" and "CITIZENS' RADIO CALL BOOK" for one full year starting with the DECEMBER issue of both magazines.

Name.....

Street and No.....

City and State.....

DEPENDABLE! EVERLASTING!



100 Volt Edison Element,
Non-Destructive Rechargeable
"B" Battery with Charger.....\$12
140 Volt with Chemical Charger.....\$17
180 Volt with Dry Trickle Charger.....\$24

Complete knockdown batteries, all sizes at reduced prices. Detector and intermediate voltages plainly marked. Greater volume and clearer than any other eliminator.

Use this coupon
to receive our interesting booklet.

SEE JAY BATTERY COMPANY
913 Brook Ave., New York, N. Y.

Please mail me at once your FREE illustrated booklet describing your batteries and power units, without any obligation to me.

Name.....
Street & No.....
Town..... State.....



Professional Set Builders and Dealers!

The latest developments of the 1929 season are fully described in our NEW FREE Catalog. Lowest prices on all nationally advertised kits, sets, accessories, cabinets, etc. Get the BEST in RADIO—at the BIGGEST SAVING. Complete stock carried. No shipping delays. Write for Catalog TODAY.

TELEVISION—We have complete information which will prove interesting to SET BUILDERS.

WALTER ROWAN CO.
833 Washington Blvd., Dept. 101
CHICAGO, ILL.

FREE Wholesale Radio Catalog

Set Builders-Dealers! Save Money!
Send for the most complete book of nationally known Parts, Kits, Cabinets, Consoles, Speakers, Power Units, Sets, etc. All at lowest wholesale prices. Quick service on all your needs. Write now, it is FREE—
SETBUILDERS SUPPLY CO.
Dept. 14-3 Rosenberg Bldg. Madison and Market Sts. CHICAGO, ILL.

FERRANTI

Audio Frequency Transformers
Send 15c in coin for copy of the
1929 Year Book.

FERRANTI, INC.
130 West 42nd St., New York, N. Y.

**THE MIRACLE OF
THE RADIO WORLD!**

Newest Guaranteed 7-Tube
1-Dial Console Set—Worth \$200

BUY DIRECT 1929 MODEL



**ALL ELECTRIC RADIO
30 DAYS' FREE TRIAL!**

**A Wonder
Bargain!**

Buy direct
from factory—
\$200
VALUE

Outperforms
sets selling at
2 and 3 times
our low price.
Includes console
shown, made of combination
walnut; A. C.
electric set,
all tubes,
built-in magnetic
speaker and aerial
equipment.



**COMPLETE
Nothing Else to Buy**

Powerful Reception—Amazing Tone!

Remember—30 days free trial. You be the judge! Worth \$200 and looks like! Only one dial to tune—illuminated! Marvelous mellow tone. Selective and gets distance easily. The radio sensation for quality, price and performance. Mail coupon today for our big, money-saving Free Catalog, before you buy any radio or accessories!

Battery Sets

Our low factory prices on the complete line of Diamond Electric and battery operated radios shown in catalog will amaze you!

**Our New FREE
Catalog—Just
Published—Shows
You How To
SAVE HALF!**

Diamond Radio Company
Dept. 226 - 820 S. Clinton St., Chicago, Ill.

MAIL THIS COUPON TODAY!

**Diamond Radio Company, Dept. 226
820 S. Clinton St., Chicago, Ill.**
Please send me your Free Catalog of Diamond radios and details of your 30 Day FREE Trial offer
Name.....
Address.....
City..... State.....

**Back Copies of
"RADIO" Wanted!!**

I will pay 35 cents each for the
following back-numbers of
"RADIO"—

1924—May, Nov., Dec.
1925—Jan., March, Dec.
1926—Feb., March, May
1927—February issue

Only one copy of each issue is wanted

L. G. SCHNELLER
504 Forrest Ave., River Forest, Ill.

Tell them you saw it in RADIO



A Vitrohm 507-109 Unit
installed on your radio
set lengthens the life of
the a.c. tubes by automatically lowering the
filament voltage.

This unit costs only \$2.00
—a small investment if
one set of a.c. tubes is
saved.

Write for free information
on the complete line
of Ward Leonard Radio
Products.

**WARD LEONARD MOUNT
ELECTRIC CO. VERNON
NEW YORK**

INTERESTED IN DX?

It's by no means a lost art. Greater distances than ever before can be covered today—if you know how. Try some of the ingenious stunts described in "The Gateway to Better Radio"—that big, unselfish, understandable manual of 20,000 words and 88 illustrations, which is yours for 25 cents a copy. Get yours today from your dealer or direct from
Clarostat Mfg. Co., 285 N. 6th St., Brooklyn, N. Y.

CLAROSTAT
REG. U. S. PAT. OFF.

**Send For
WESTERN RADIO
New
1929 Catalog**

Dealers and Set Builders

THE NEW 1929 Catalog is crammed full of the FINEST, NEWEST, Nationally known A.C. sets, consoles, cabinets, dynamic speakers, kits, eliminators and accessories at LOWEST PRICES. Largest stock of radio parts. Prompt delivery. Write for our FREE catalog.
Western Radio Mfg. Co.
128 W. Lake St., Dept. R-11
CHICAGO

FREE



**"The Big
Friendly
Radio House"**



Don't Burn Out Tubes

One of the chief troubles in the new A. C. sets using either A. C. tubes or D. C. tubes in series is paralysis or damage to the tubes due to incorrect filament voltage. This invariably can be traced to line voltage, which in some localities varies considerably throughout a twenty-four hour period. In the sets using the new A. C. four and five prong tubes it is very important that the filament voltage is right, as it is sometimes found that a particular filament setting is necessary to eliminate hum.

All of the above troubles call for some definite method of adjustment and this can be best accomplished by a suitable A. C. voltmeter having ranges which cover the trouble expected.

Such an instrument and one used by many service men in their work is the Jewell Pattern 77 triple range portable A. C. voltmeter. It is a very desirable instrument for the set owner as it enables him to operate his set at safe filament voltages at all times. The combination range is 0-3-15-150 volts. The scale is silver etched with black characters, and the movement is mounted in a metal case on a bakelite base.

Every owner of an A. C. operated set should have one. Write for descriptive circular No. 1145.

Jewell Electrical Instrument Company
1650 WALNUT STREET, CHICAGO
"28 Years Making Good Instruments"



Pattern No. 77

FREE RADIO BOOK!

AND NEW SUPPLEMENT C

44 pages chock-full of vital information for set builders and all radio enthusiasts. 16 new easy-to-build circuits—receivers, transmitters, radiophones, short wave. Complete construction data, schematics, photos, etc. Also full information about Aero air-dielectric coils. Write for FREE copy TODAY. Address AERO PRODUCTS, Inc., Dept. 764, 4611 Ravenswood Ave., Chicago, Ill.

SHERMAN SQUARE
HOTEL
70TH ST.
&
B'WAY
NY

CONVENIENT HOMELIKE

QUIET COMFORTABLE

EXCELLENT FOOD
AT MODERATE PRICES

COURTEOUS
SERVICE

SINGLE ROOM \$2.50
AND BATH
FOR TWO \$4.00

REASONABLE RATES

WIRE
AT OUR
EXPENSE

NEW SHIELDED SUPER-10

5 Screen Grid R. F. Amplifiers
4 Stage Power A. F. Amplifier

*A new and Superior Receiver,
representing highest type of effi-
ciency obtainable, in point of
extreme range, selectivity and
quality of reproduction*

Illustrated literature gratis

Complete Constructional Blue Prints
\$2.00, postpaid

NORDEN-HAUCK, INC.

*Builders of Highest Class Radio
Apparatus in the World*

Marine Bldg., Philadelphia, Pa.

Cable Address "NORHAUCK"

RADIOADS

A CLASSIFIED ADVERTISING SECTION READ BY BETTER BUYERS

The rate per word is eight cents net. Remittance must accompany all advertisements. Include name and address when counting words.

Ads for the December Issue Must
Reach Us by November Fifth

MAKE MONEY WITH PATENTS! We offer patents with money-making possibilities; circular free. Floyd Clymer, Denver, Colo. (3T)

IMAGINE AN ORGANIZATION of radio "nuts" with over 3000 clients scattered throughout the world, hundreds of them hams, all of them radiowise—dealers, builders, experimenters. Over \$40,000 stock of high-grade receiving and transmitting parts only, no sets. Spend over \$5,000 yearly on our own experimenting, carry nothing until it passes our tests. 25c will bring prepaid over four pounds, catalog, circuits, data, etc. Weekly data sheets for experimenters and builders (more reliable data than all radio magazines together)—20 weeks, \$1.00, 52 weeks, \$2.50. Full dealer's discounts to licensed hams, and radiowise builders. We carry approved items advertised in "RADIO," Kladag Radio Laboratories. Established 1920, Kent, Ohio. (6T)

WANTED—Men to work with National Radio Service organization. No selling scheme. Radio Doctors, Inc., Dept. R, Essex St., Salem, Mass.

DEFECTIVE AUDIO TRANSFORMERS Reclaimed Using Factory Windings, Original Guarantee—\$0.90. Reclaimed transformers for sale, most makes, \$10.00. Inquiries invited. TRANSFORMER RECLAIMING SERVICE, 9 South Reed Ave., Mobile, Alabama.

CHILLICOTHE WALNUT CABINETS. 7x26 inches and 11 inches deep. Genuine walnut with full length piano hinge. Several of these are in stock. Never used. Originally purchased for editorial photographing. Retail price \$30.00. We will sell these while they last for \$12.50, express charges collect. Eight on hand. Publishers of "RADIO," Pacific Building, San Francisco, Calif.

ELECTRICAL BARGAINS. — New 3/4-HP Westinghouse 110 volt, 60 cycle, 1750 speed alternating motors with pulleys, \$8.75. Variable speed motors for television 110 volt alternating current, \$7.00. Also other sizes motors and generators. Electrical Surplus Co., Dept. 1, 1911 Chicago Ave., Chicago.

FOR SALE.—Latest model Best's Shielded Grid Super without cabinet. Perfect condition. \$100. Address Owner, 1129 Mandana Blvd., Oakland, Cal.

NAVY SURPLUS offered at fraction of original cost. General Electric 24/1500, 24/750, 12/350 volt. Holtz-Cabot 12/500, Westinghouse 10/350. Battery driven also adapted for external drive. 500 and 900 cycle generators. All ball bearing. Literature. Henry Kienzle, 501 East 84th Street, New York. (2T)

KENNEDY TUNER, 200-3600 meters; Magnavox 2-stage amplifier, tubes; Magnavox dynamic horn. Lot \$25.00. Roy Strong, Manteca, Calif.

FOR SALE!—Gerald Best's "Modernized" 45-KC super exactly as described in the editorial columns of October "RADIO." This receiver was built by G. M. Best for use in gathering editorial material for the story, and the publishers of "RADIO" will sell the receiver, as illustrated, for \$75.00. A fine genuine walnut cabinet with piano hinge is included in the price. In perfect condition and accurately matched and balanced. First money order for \$75.00 takes it. Set will be shipped to you express charges collect. PUBLISHERS OF "RADIO," 433 Pacific Bldg., San Francisco, Calif.

BIG PAY.—South American work. American firms pay fare, expenses. South American Service Bureau, 14,600 Alma, Detroit, Mich.


RADIO STATION stamps bought, sold and exchanged. Chas. A. Phildius, 510 East 120th St., New York, N. Y. (4T)

USE THE CLASSIFIED ADS IN "RADIO"

They Bring Results

Mail Your "Ad" Now

AIR-KING

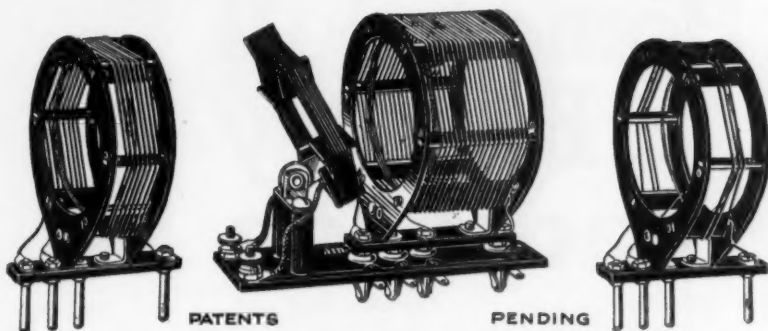

\$12.50

Per Set as
Illustrated

THE ULTIMATE in Precision Short Wave Plug-in Coils

THE Air-King Precision short wave coils have been built scientifically to meet all the exacting requirements of high frequency work, such as extremely low losses, rugged construction and permanency of calibration.

(1) The low loss feature has been obtained by winding the turns "on air," and by using the least possible amount of solid dielectric. The dielectric is all air except at the few places where the wire touches the lateral ribs upon which it is wound. The turns are spaced so that the distributed capacity is very low. This decreases the losses and increases the tuning range of the coils.

(2) Ruggedness in an unusual degree has been secured by riveting the lateral ribs firmly to the sturdy bakelite end pieces. The ribs are mounted edgewise so that they offer the greatest resistance to bending under the stresses set up by the tightly wound wire and so that the least amount of solid material comes in contact with it. The strength is so great that a coil may be dropped on the floor from a distance of several feet without the slightest damage or change in the shape of the coil or in the alignment of the wires. You cannot disturb the coil construction by twisting with your hands, although you exert all your strength. A coil can also be inserted into and taken out of the coil receptacle times without number, and remain unimpaired. This is an important feature in plug-in coils which must be inserted in and removed from the base many times.

(3) Permanency of calibration is also an important feature secured by the rugged construction. The wires cannot shift, for they are firmly held in the slots in the ribs. Hence both the inductance and the distributed capacity of a coil remain fixed. It is thus possible to log a receiver built with these coils with the assurance that the log or calibration chart is valid every time the same coil is inserted and the same tube used.

(4) The coils are designed to tune with a condenser having a maximum capacity of .00014 mfd. When a condenser of this value is used the set of coils will cover the entire short wave band from about 15 meters to 133 meters with suitable overlapping of ranges for the separate coils to prevent any dead spots.

(5) The tickler winding on each coil has been designed so that when a regeneration condenser of .00025 mfd. is used, oscillation control at all settings of the tuning condenser is complete.

(6) The same antenna coil is used for all the tuning coils, therefore, it is mounted on the coil receptacle. So that the required degree of coupling may be obtained for any of the tuning coils, at any setting of the tuning condenser, for any range of frequency, and for any antenna, the antenna or primary coil is mounted on hinges. The primary may be turned as required to given maximum signal strength in any case and is held securely in place by friction.

Price—\$12.50 per Set of 3

WAVELENGTH RANGES OF THESE COILS

The tuning ranges of the three coils of the Air-King kit, when used with a .00014 mfd. tuning condenser, are as follows:

No. 1—Small coil—15 to 33½ meters

No. 2—Intermediate coil—31½ to 68 meters

No. 3—Large coil—57 to 133 meters

These wavelength ranges are engraved on each coil frame. Other coils available in ranges up to the broadcast band and down to 8 meters.

Mfd. by AIR-KING PRODUCTS CO.
216 WALLABOUT ST. BROOKLYN, N.Y., U.S.A.

Order from Offenbach if you live in the West. / / / Order from Factory if you live in the East.

RADIO DEALER'S SUPPLY SERVICE

Wholesale Division of

OFFENBACH ELECTRIC CO.

1452 Market Street,
San Francisco, Calif.

Here is \$5.00. Send me by parcel post at once a set of Air-King Short Wave Plug-in Coils as advertised in NOVEMBER "RADIO." The small balance is to be paid by me C.O.D. upon receipt of shipment. Dealer discounts are allowed if your order is attached to your letterhead.

Name

Street and No.

City and State

AIR-KING PRODUCTS CO.

216 Wallabout Street,
Brooklyn, N. Y.

Send me immediately one set of AIR-KING SHORT WAVE PLUG-IN COILS as advertised in "RADIO." I enclose \$5.00 in part payment. Balance C.O.D. It is understood that the usual discount is to be allowed to me if I am a dealer or jobber.


Name

Street and No.

City and State

Tell them you saw it in RADIO

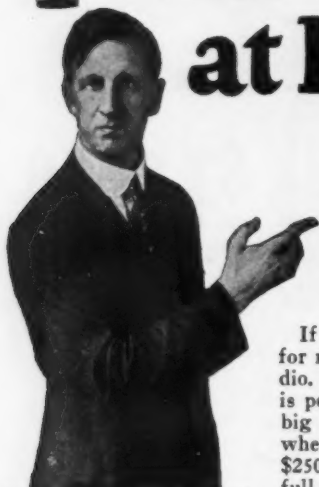I Will Train You at Home to Fill a Big-Pay Radio Job



Here's the PROOF



Made \$185 in Three Weeks Spare Time

"I have met with continued success. For instance, recently I realized a profit of \$185 in three weeks, \$1.50 an hour. I have been making good money almost from the time I enrolled. The N. R. I. has put me on the solid road to success."—Peter J. Dunn, 901 N. Monroe St., Baltimore, Md.

Made \$588 in One Month

"The training I received from you has done me a world of good. Some time ago during one of our busy months I made \$588. I am servicing all makes of Radio receiving sets. My boss is highly pleased with my work since I have been able to handle our entire output of sets here alone."—Herbert Reese, 2215 So. E St., Elwood, Indiana.



Earns Price of Course in One Week Spare Time

"I have been so busy with Radio work that I have not had time to study. The other week, in spare time, I earned enough to pay for my course. I have more work than I can do. Recently I made enough money in one month spare time to pay for a \$375 beautiful console all-electric Radio. When I enrolled I did not know the difference between a rheostat and a coil. Now I am making all kinds of money."—Earle Cummings, 18 Webster St., Haverhill, Mass.

If you are earning a penny less than \$50 a week, send for my book of information on the opportunities in Radio. It's FREE. Clip the coupon NOW. A flood of gold is pouring into this new business, creating hundreds of big pay jobs. Why go along at \$25, \$30 or \$45 a week when the good jobs in Radio pay \$50, \$75 and up to \$250 a week? My book "Rich Rewards in Radio" gives full information on these big jobs and explains how you can quickly become a Radio Expert through my easy, practical home-study training.

Salaries of \$50 to \$250 a week not unusual

Get into this live-wire profession of quick success. Radio needs trained men. The amazing growth of the Radio business has astounded the world. In a few short years three hundred thousand jobs have been created. And the biggest growth of Radio is still to come. That's why salaries of \$50 to \$250 a week are not unusual. Radio simply hasn't got nearly the number of thoroughly trained men it needs. Study Radio and after only a short time land yourself a REAL job with a REAL future.

You Can Learn Quickly and Easily in Spare Time

Hundreds of N.R.I. trained men are today making big money—holding down big jobs—in the Radio field. Men just like you—their only advantage is training. You, too, can become a Radio Expert just as they did by our new practical methods. Our tested, clear training makes it easy for you to learn. You can stay home, hold your job, and learn quickly in your spare time. Lack of education or experience is no drawback. You can read and write. That's enough.

Many Earn \$15, \$20, \$30 Weekly on the Side While Learning

My Radio course is the famous course "that pays for itself." I teach you to begin making money almost the day you enroll. My new practical method makes this possible. I give you SIX BIG OUTFITS of Radio parts with my course. You are taught to build practically every type of receiving set known. M. E. Sullivan, 412 73rd Street, Brooklyn, N. Y., writes: "I made \$720 while studying." Earle Cummings, 18 Webster Street, Haverhill, Mass., "I made \$375 in one month." G. W. Page, 1807 21st Ave., Nashville, Tenn., "I picked up \$935 in my spare time while studying."

Your Money Back if Not Satisfied


I'll give you just the training you need to get into the Radio business. My course fits you for all lines—manufacturing, selling, servicing sets, in business for yourself, operating on board ship or in a broadcasting station—and many others. I back up my training with a signed agreement to refund every penny of your money if, after completion, you are not satisfied with the course I give you.

ACT NOW—64-page Book is FREE

Send for this big book of Radio information. It won't cost you a penny. It has put hundreds of fellows on the road to bigger pay and success. Get it. Investigate. See what Radio has to offer you, and how my Employment Department helps you get into Radio after you graduate. Clip or tear out the coupon and mail it RIGHT NOW.



J. E. SMITH, President,
Dept. 33-R,
National Radio Institute
Washington, D. C.

**RADIO
NEEDS
TRAINED
MEN!**

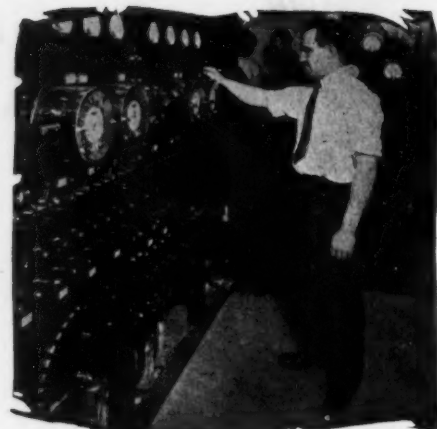

**You can build
100 circuits with
the six big outfits
of Radio parts
I give you**

3 of the 100 you can build

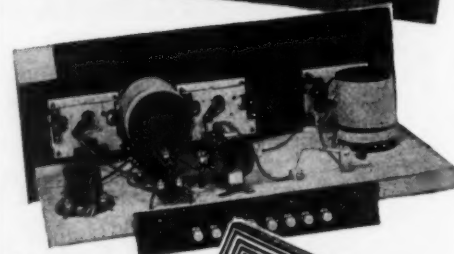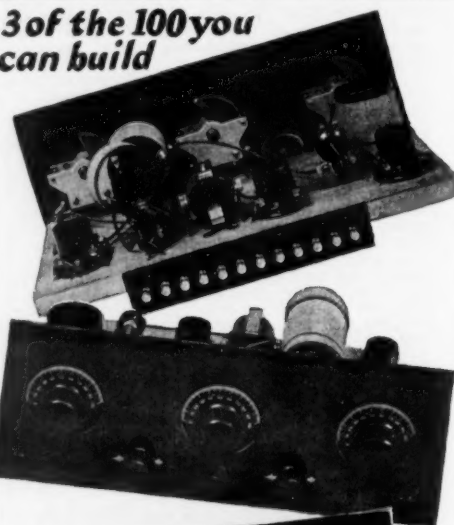

**Find out quick
about this
practical way
to big pay**



Mail This FREE COUPON Today

J. E. SMITH, President,
Dept. 33-R, National Radio Institute,
Washington, D. C.
Dear Mr. Smith: Kindly send me your big book
"Rich Rewards in Radio," giving information on
the big-money opportunities in Radio and your
practical method of teaching with six big outfits.
I understand this book is free, and that this places
me under no obligation whatever.

Name..... Age.....
Address.....
City..... State.....
Occupation.....

Employment Service to all Graduates
Originators of Radio Home Study Training

TOBE



TOBE Tobe Type 250 B-Block



TOBE B BLOCKS—Model 760



TOBE VACUUM TIPON LEAKS



TOBE TOBE 1300 Line Hi-Voltage SURGPROOF Condensers




TOBE TOBE A-Condenser



TOBE TINYTOBE Condensers

A manufacturer can have no greater faith in his products than to guarantee their faithful operation and with such guarantee TOBE products are sold.

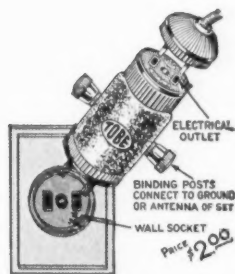

TOBE 4-PURPOSE LIGHT SOCKET AERIAL

The test of the manufacturer's faith in his products is how long will he guarantee them. Tobe apparatus is unconditionally guaranteed for one year.



TOBE FILTER CONDENSERS




TOBE TOBE A-Filter



Radio Interference Filter No. 1



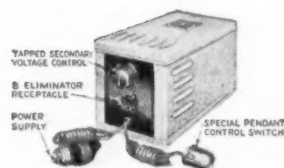TOBE 5 WATT VERITAS FITS ALL STANDARD MOUNTS



TOBE The New Tobe A Supply



TOBE 1000 Volt & 2000 Volt Transmitting Condenser



TOBE TOBE By-Pass Filter Condenser New Model

TOBE DEUTSCHMANN CO.

CANTON, MASS.

NEW YORK

CANTON, MASS.

CHICAGO

THE MECHANICAL MASTERPIECE

NEW 1929

Browning-Drake

EIGHT IN LINE

Eight tubes in line—aluminum construction throughout—all power equipment an integral part of chassis—this year's masterpiece of mechanical precision.



Special Browning-Drake circuit, famous for tone quality and distance—cabinet of selected walnut with hand-rubbed Duco finish. List \$135.00.

In radio sets, as in most everything else, you get about what you pay for. The cheapest is never the best.

Your customers are willing to pay a little more and get a Browning-Drake.

Refinements, which make for beauty, power, and tone quality, are obtained through precision assembly, rather than mass production. Among those who appreciate and require the best, Browning-Drake is the outstanding choice.

Quality never fails to satisfy.

BROWNING
TRADE MARK
DRAKE

Press of
THE JAMES H. BARRY COMPANY
SAN FRANCISCO, U. S. A.